

# **CMOS ANALOG IC DESIGN**

## **QUESTION BANK**

### **M.TECH**

### **(I YEAR – I SEM)**

### **(2023-24)**

**Department of Electronics and Communication Engineering**



**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY**  
**(Autonomous Institution - UGC, Govt. of India)**

Recognized under 2(f) and 12 (B) of UGC ACT 1956

(Affiliated to JNTUH, Hyderabad, Approved by AICTE - Accredited by NBA & NAAC – 'A' Grade - ISO 9001:2015 Certified)  
Maisammaguda, Dhulapally (Post Via. Kompally), Secunderabad – 500100, Telangana State, India



Code No: **R22D6803****MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY**

(Autonomous Institution – UGC, Govt. of India)

**M.Tech I Year I Semester Supplementary Examinations, August 2023****CMOS Analog IC Design****(VLSI&ES)**

<b>Roll No</b>									
----------------	--	--	--	--	--	--	--	--	--

**Time: 3 hours****Max. Marks: 60****Note:** This question paper contains two parts A and B

Part A is compulsory which carries 10 marks and Answer all questions.

Part B Consists of 5 SECTIONS (One SECTION for each UNIT). Answer **FIVE** Questions, Choosing ONE Question from each SECTION and each Question carries 10 marks.

\*\*\*\*

**PART-A (10 MARKS)****(Write all answers of this PART at one place)**

- |          |          |   |             |
|----------|----------|---|-------------|
| <b>1</b> | <b>A</b> | Define threshold voltage? Give the expression for it?                         | <b>[1M]</b> |
|          | <b>B</b> | Draw the small signal model for NMOS MOSFET with all considerations           | <b>[1M]</b> |
|          | <b>C</b> | Draw the circuit diagram for Wilson current mirror?                           | <b>[1M]</b> |
|          | <b>D</b> | What is the value of output resistance when MOSFET is in degeneration?        | <b>[1M]</b> |
|          | <b>E</b> | What is Current amplifier?  | <b>[1M]</b> |
|          | <b>F</b> | Draw the single ended differential amplifier circuit diagram?                 | <b>[1M]</b> |
|          | <b>G</b> | List out the op-amp operation parameters.                                     | <b>[1M]</b> |
|          | <b>H</b> | Explain about OTA?  | <b>[1M]</b> |
|          | <b>I</b> | Sketch the transfer characteristic and model for comparator with finite gain? | <b>[1M]</b> |
|          | <b>J</b> | Differentiate the Two-stage comparator and Discrete time Comparator           | <b>[1M]</b> |

**PART-B( 50 MARKS)****SECTION-I**

- |          |          |  |             |
|----------|----------|--|-------------|
| <b>2</b> | <b>A</b> | Derive the I-V relationship of the MOSFET in all the possible regions.     | <b>[6M]</b> |
|          | <b>B</b> | Suggest a region of operation for the same if one wants to design a switch | <b>[4M]</b> |
|          |          | <b>OR</b>  |             |

- |          |          |  |             |
|----------|----------|--|-------------|
| <b>3</b> | <b>A</b> | Explain about subthreshold conduction?                   | <b>[5M]</b> |
|          | <b>B</b> | Discuss the various short channel effects in MOS devices | <b>[5M]</b> |

**SECTION-II**

- |          |          |  |             |
|----------|----------|--|-------------|
| <b>4</b> | <b>A</b> | Draw and explain about simple current mirror with beat helper. | <b>[5M]</b> |
|          | <b>B</b> | Explain about cascode current mirrors.                         | <b>[5M]</b> |
|          |          | <b>OR</b>  |             |

- |          |          |  |             |
|----------|----------|--|-------------|
| <b>5</b> | <b>A</b> | Discuss about the charge injection errors in MOS switch.               | <b>[5M]</b> |
|          | <b>B</b> | Draw the circuit diagram of High swing cascode current mirror circuit? | <b>[5M]</b> |

**SECTION-III**

- |          |          |  |             |
|----------|----------|--|-------------|
| <b>6</b> | <b>A</b> | Derive the voltage gain for telescopic op amp?   | <b>[5M]</b> |
|          | <b>B</b> | Discuss the principle of current feedback op amp | <b>[5M]</b> |
|          |          | <b>OR</b>  |             |

- |          |          |  |             |
|----------|----------|--|-------------|
| <b>7</b> | <b>A</b> | Discuss the disadvantages of cascode amplifier under low voltage condition | <b>[5M]</b> |
|----------|----------|--|-------------|

- and hence discuss the folded cascode structure to address the same
- B Explain the various architectures of high gain amplifiers. [5M]
- SECTION-IV**
- 8 A Explain about PSRS of two stage op amp [5M]  
 B Explain what is meant by dominant pole compensation in operational amplifiers [5M]
- OR
- 9 Explain about single and two stage op amp with neat circuit diagrams [10M]
- SECTION-V**
- 10 A Explain the auto zeroing concept of improving the performance of a comparator. [5M]  
 B Discuss the dynamic characteristics of a Comparator? [5M]
- OR
- 11 A Give the principle of comparators and characterize the same? [5M]  
 B Explain about Switched capacitor comparators? [5M]
- \*\*\*

**Code No: R20D6803****MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****M.Tech I Year I Semester Supplementary Examinations, August 2023****CMOS Analog IC Design****(VLSI&ES)**

<b>Roll No</b>									
----------------	--	--	--	--	--	--	--	--	--

**Time: 3 hours****Max. Marks:****70**

**Note:** This question paper Consists of 5 Sections. Answer **FIVE** Questions, Choosing ONE Question from each SECTION and each Question carries 14 marks.

\*\*\*

**SECTION-I**

- 1    A    Design the Physical structure of an n-channel and a p-channel transistor in a p-well technology. [7M]  
       B    Define the threshold voltages in MOS transistor and derive the threshold voltage equation. [7M]

OR

- 2    A    Define latch up and explain two prevention methods. What are the advantages of latch up? [7M]  
       B    Design the small-signal model for the MOS transistor. [7M]

**SECTION-II**

- 3    A    Illustrate the hierarchy of analog circuits for the operational amplifier. [7M]  
       B    Derive the active resistor equation  $r_{ds}$  for the MOS diode resistor. [7M]

OR

- 4    A    Design current sinks and source characteristics. [7M]  
       B    Draw the I-V characteristics of ideal current and voltage references. [7M]

**SECTION-III**

- 5    A    Compare Active PMOS load inverter and Current source load inverter. [7M]  
       B    Design the noise calculations in a current-source load inverter. [7M]

OR

- 6    A    Design the CMOS differential amplifier using a current-mirror load. [7M]  
       B    Calculate the minimum output voltage for the simple Cascode Amplifier. [7M]

**SECTION-IV**

- 7    A    Design of CMOS Op-Amps and simplified inverting voltage amplifier using an op-amp. [7M]  
       B    Give the design procedure for the Two-stage CMOS op-amp. [7M]

OR

- 8            Design the power-supply rejection ratio of two-stage op amps. [14M]

**SECTION-V**

- 9    A    Design the two-stage, open-loop comparators and its performances. [7M]  
       B    Design the clamped push-pull output comparators. [7M]

OR

- 10            Calculate the Propagation delay time of a two-stage open-loop comparator. [14M]

Code No: R18D6808

**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY**

(Autonomous Institution – UGC, Govt. of India)

**M.Tech I Year I Semester Supplementary Examinations, August 2023****CMOS Analog Integrated Circuit Design**

(VLSI&amp;ES)

Roll No									
---------	--	--	--	--	--	--	--	--	--



**Time: 3 hours****Max. Marks: 70**

**Note:** This question paper Consists of 5 Sections. Answer **FIVE** Questions, Choosing ONE Question from each SECTION and each Question carries 14 marks.

\*\*\*

  **SECTION-I**

- 1 A Explain the operation of a MOS transistor and derive the mathematical model (drain current equation) in all operating regions [7M]
- B Determine the operating region and  $I_D$  of each of the following MOSFETs. [7M]  
Assume  $V_{THn} = 0.4$ ,  $V_{THp} = -0.4$ ,  $\mu_n C_{ox} = 200 \mu A/V^2$ ,  $\mu_p C_{ox} = 100 \mu A/V^2$   
 $W/L = 10 \mu m / 0.5 \mu m$ .  $\lambda = 0$ ,  $\gamma = 0$



OR

- 2 A What are the different capacitor components compatible with fabrication steps used to build MOS device. Mention the range of values and matching accuracy. [7M]
- B Draw the small signal model of a MOSFET and derive the small signal parameters [7M]

**SECTION-II**

- 3 A Derive (using small signal analysis) the on-channel resistance of a [7M]  
(i) Diode connected MOSFET in saturation region  
(ii) MOSFET in linear region
- B With neat sketches, compare basic current sink and cascode current sink in terms of voltage overhead and output resistance. [7M]

OR

- 4 A Design a basic NMOS current mirror for a output current of 0.75mA [7M]  
from a reference current of 0.5mA and a voltage overhead of 0.3V.  
Assume  $V_{THn} = 0.4$ ,  $\mu_n C_{ox} = 200 \mu A/V^2$
- B What is an ideal voltage/current reference and mention their [7M]  
performance characteristics? Describe the general principle of a  
bandgap reference circuit

**SECTION-III**

- 5 A Draw the circuit diagram of an current source load interver, plot the [7M]  
voltage transfer function and derive its small signal voltage gain

- B Give a neat sketch of CMOS differential amplifier with active current mirror load and derive the voltage gain, slew rate and voltage transfer curve [7M]
- OR
- 6 A What are the advantages of cascading?? Provide a circuit implementation of a cascode amplifier (with current mirror biasing) and derive its voltage gain [7M]
- B Write short notes on high gain amplifier architectures [7M]
- SECTION-IV**
- 7 A What is the need for frequency compensation in an opamp? Describe the miller compensation of a two stage op-amp [7M]
- B Design a two-stage opamp for the below specifications [7M]  
 $A_v=3000V/V$ ,  $V_{dd}=2.5V$ ,  $V_{ss} = -2.5V$ ,  $GB=10MHz$ ,  $CL=10pF$ ,  $SR > 20V/\mu s$ ,  $V_{out,range}=\pm 2V$ ,  $ICMR=-1V$  to  $2V$ ,  $P_{diss}=2mW$ . Assume appropriate material and device parameters
- OR
- 8 A Provide a neat sketch of nMOS input PMOS cascode folded cascode opamp and derive the output voltage swing, output resistance and small signal voltage gain [7M]
- B Write short notes on measurement/simulation of gain, bandwidth, CMRR and PSRR of an opamp [7M]
- SECTION-V**
- 9 A Describe the model of a comparator with finite gain. Define the static and dynamic characteristics of a comparator [7M]
- B With a neat sketch, describe the methods to increase the capacitive drive of a two-stage open loop comparator [7M]
- OR
- 10 A Draw a neat sketch of two-stage open loop comparator and derive its  $V_{OH}$ , small signal gain, frequency response and slew rate [7M]
- B What is the need for comparator with hysteresis? Provide a neat sketch of comparator with hysteresis and plot input/output waveforms with and without hysteresis [7M]

**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****M.Tech I Year I Semester Supplementary Examinations, November 2022****CMOS Analog IC Design****(VLSI&ES)**

<b>Roll No</b>										
----------------	--	--	--	--	--	--	--	--	--	--

**Time: 3 hours****Max. Marks: 70**Answer Any **Five** Questions

All Questions carries equal marks.

\*\*\*

- |          |   |   |              |
|----------|---|---|--------------|
| <b>1</b> | A | Discuss the Passive Components of the MOS transistor?   | <b>[7M]</b>  |
|          | B | Explain sub threshold MOS model?  | <b>[7M]</b>  |
| <b>2</b> | A | Explain the CMOS device Modelling?  | <b>[7M]</b>  |
|          | B | Draw the small-signal model for the MOS transistor. Briefly explain each component in that?         | <b>[7M]</b>  |
| <b>3</b> | A | Explain the given simplest forms of the current mirror, the MOS version of the current mirror?      | <b>[7M]</b>  |
|          | B | Explain the Bipolar simple current mirror with degeneration helper with necessary equations?        | <b>[7M]</b>  |
| <b>4</b> |   | What is the Current Mirror? Explain the general properties of current mirrors with a block Diagram? | <b>[14M]</b> |
| <b>5</b> | A | Design a CMOS current mirror load differential amplifier?   | <b>[7M]</b>  |
|          | B | Explain the slew rate and noise for a p-channel differential amplifier with necessary equations?    | <b>[7M]</b>  |
| <b>6</b> | A | Explain about cascade amplifier?  | <b>[7M]</b>  |
|          | B | Explain about the design of CMOS opamps?  | <b>[7M]</b>  |
| <b>7</b> | A | Explain about the Cascode Op-amps?  | <b>[7M]</b>  |

- B Explain the design of Two-stage op-amps? [7M]
- 8 A Compare the dynamic latch with the NMOS and PMOS latches. What are the advantages and disadvantages of the two latches? [7M]
- B Explain the different types of Open-loop comparator? [7M]

.....



**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****M.Tech I Year I Semester Regular/Supplementary Examinations, June 2022**  
**CMOS Analog IC Design****(VLSI&ES)**

<b>Roll No</b>										
----------------	--	--	--	--	--	--	--	--	--	--

**Time: 3 hours****Max. Marks: 70**Answer Any **Five** Questions

All Questions carries equal marks.

\*\*\*

- |          |          |  |             |
|----------|----------|--|-------------|
| <b>1</b> | <b>A</b> | Explain the Large-signal model for the MOS Transistor?   | <b>[7M]</b> |
|          | <b>B</b> | Explain about computer simulation model?   | <b>[7M]</b> |
| <b>2</b> | <b>A</b> | Draw the small-signal model for the MOS transistor. Briefly explain each component in that?  | <b>[7M]</b> |
|          | <b>B</b> | Choose values of $V_{GS} = 1, 2, 3, 4$ and $5V$ , assume that the channel modulation parameter is zero. Sketch to scale the output characteristics of an enhancement n-channel device if $V_T = 0.7V$ and $I_D = 500\mu A$ when $V_{GS} = 5V$ in saturation. | <b>[7M]</b> |
| <b>3</b> | <b>A</b> | Explain the simplest forms of the current mirror and the Bipolar version of the current mirror?  | <b>[7M]</b> |
|          | <b>B</b> | Explain in detail the MOS cascode current mirror with necessary equations?   | <b>[7M]</b> |
| <b>4</b> | <b>A</b> | Explain the difference between cascode current mirror and Wilson current mirror?   | <b>[7M]</b> |
|          | <b>B</b> | Write a short notes on current sinks and sources?  | <b>[7M]</b> |

- 5**      A      Briefly explain the differential amplifiers. With necessary equation give the large-signal analysis of CMOS differential amplifiers?      **[7M]**
- B      Derive the expression for power-supply rejection ratio of Two-stage op-amps?      **[7M]**
- 
- 6**      A      Explain about current amplifier?      **[7M]**
- B      Explain the concept of push-pull inverter with a neat diagram. Derive the small signal voltage gain and find the zero in plane?      **[7M]**
- 
- 7**      A      Explain about the design of Two-stage op-amps?      **[7M]**
- B      Explain the compensation of Op-amps?      **[7M]**
- 
- 8**      A      Differentiate the Two-stage comparator and Discrete-time Comparator?      **[7M]**
- B      With neat sketch and necessary equations explain the Design aspect of a two stage open loop comparator for slewing response?      **[7M]**

\*\*\*\*\*

**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY**

**(Autonomous Institution – UGC, Govt. of India)**

**M.Tech I Year I Semester Supplementary Examinations, November 2022**  
**CMOS Analog Integrated Circuit Design**

**(VLSI&ES)**

<b>Roll No</b>										
----------------	--	--	--	--	--	--	--	--	--	--

**Time: 3 hours**

**Max. Marks: 70**

Answer Any **Five** Questions

All Questions carries equal marks.

\*\*\*

- 1** Explain about the computer simulation models. **[14M]**
  
- 2** Explain the Large-signal model for the MOS Transistor. **[14M]**
  
- 3** Discuss about current sinks and sources. **[14M]**
  
- 4** Explain the difference between cascade current mirror and Wilson current mirror. **[14M]**
  
- 5** Explain about the current amplifier. **[14M]**
  
- 6** Explain about the output amplifier. **[14M]**

**7** Explain about the design of CMOS op-amps. **[14M]**

**8** How to improve the performance of Open loop comparator. **[14M]**

\*\*\*\*\*

Code No: R20D6803

**R20**

**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY**

**(Autonomous Institution – UGC, Govt. of India)**

**M.Tech I Year I Semester Regular Examinations, July 2021**

**CMOS Analog IC Design**

**(VLSI&ES)**

<b>Roll No</b>										
----------------	--	--	--	--	--	--	--	--	--	--

**Time: 3 hours**

**Max. Marks: 70**

Answer Any **Five** Questions

All Questions carries equal marks.

\*\*\*

- 1 Find the Threshold voltage and Body factor of an n-channel [14M]  
transistor with an  $n^+$  silicon gate if  $t_{ox} = 200 \text{ \AA}$ ,  $N_A = 3 \times 10^{16} \text{ cm}^{-3}$ , gate doping  $N_D = 4 \times 10^{19} \text{ cm}^{-3}$ , and if the number of positively charged ions at Gate-Silicon interface per area is  $10^{10} \text{ cm}^{-2}$ .
- 2 Interpret the simple MOS large signal model using mathematical [14M]  
models.
- 3 Model the Voltage reference circuits using voltage division of [14M]  
Resistor and Active device implementation.
- 4 What is current mirror circuit and discusses its operation using [14M]  
various blocks

- 5 What is Active load inverter? Develop small signal model for the Active load inverter. [14M]
- 6 Develop CMOS differential Amplifier and obtain the Differential transconductance of the amplifier. [14M]
- 7 Draw the block diagram of a general two stage Op-Amp and explain the functionality each block. [14M]
- 8 Identify model of an Ideal comparator, comparator with finite gain and comparator with input-offset voltage. [14M]

\*\*\*\*\*

**R20**

Code No: R20D6803

**MALLA REDDY COLLEGE OF ENGINEERING &  
TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****M.Tech I Year I Semester Supplementary Examination  
CMOS Analog IC Design****(VLSI&ES)**

<b>Roll No</b>										
----------------	--	--	--	--	--	--	--	--	--	--

**Time: 3 hours****Max. Marks: 70**

**Note:** This question paper Consists of 5 Sections. Answer **FIVE** Questions, Choosing ONE Question from each SECTION and each Question carries 14 marks.

**\*\*\*****SECTION-I**

- 1** Develop the small signal model of MOS transistor and derive the equation for its transconductance. **[14M]**

**OR**

- 2** For an n-channel MOSFET with an  $n^+$  silicon gate if  $t_{ox} = 200 \text{ \AA}$ ,  $N_A = 3 \times 10^{15} \text{ cm}^{-3}$ , gate doping  $N_D = 4 \times 10^{18} \text{ cm}^{-3}$ , and if the number of positively charged ions at Gate-Silicon interface per area is  $10^{10} \text{ cm}^{-2}$ . Find the  $V_t$  and  $\gamma$  of the transistor. **[14M]**

**SECTION-II**

- 3** What is Standard Cascode current circuit and discusses its operation using output characteristics. **[14M]**

**OR**

- 4 What happens when Gate and Drain of MOS transistor are tied together? Show its I-V characteristics and its small signal model. [14M]

**SECTION-III**

- 5 Identify the circuit models for Active load, current source and Push-pull inverters. [14M]

OR

- 6 Develop CMOS differential Amplifier using current mirror load and obtain the Differential transconductance of the amplifier. [14M]

**SECTION-IV**

- 7 List the design procedure parameters of two stage CMOS Op-Amp. [14M]

OR

- 8 Derive the method for calculating Power-Supply Rejection Ratio and its model. [14M]

**SECTION-V**

- 9 Build the circuit model and frequency response of two stage comparator. [14M]

OR

- 10 Find the propagation delay time of open-loop comparator that has a dominant pole at  $10^3$  rad/s, DC gain of  $10^4$ , slew rate  $1 \text{ V}/\mu\text{s}$ , and a binary output voltage swing of  $1 \text{ V}$  for an applied input voltage  $10 \text{ mV}$ . [14M]

\*\*\*\*\*



**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****M.Tech I Year I Semester Supplementary Examinations, December  
CMOS Analog Integrated Circuit Design****(VLSI&ES)**

<b>Roll No</b>										
----------------	--	--	--	--	--	--	--	--	--	--

**Time: 3 hours  
70****Max. Marks:**

**Note:** This question paper Consists of 5 Sections. Answer **FIVE** Questions, Choosing ONE Question from each SECTION and each Question carries 14 marks.

\*\*\*

**SECTION-I**

- 1 a).Discuss about the Passive Components of the MOS transistor. **[7M]**  
b).Explain about the computer simulation models. **[7M]**

OR

- 2 a).Compare NMOS and CMOS technologies with an example. **[7M]**  
b).Explain sub threshold MOS model. **[7M]**

**SECTION-II**

- 3 a).Write a short note on current sinks and sources. **[7M]**  
b).Explain the difference between cascade current mirror and Wilson current mirror. **[7M]**

OR

- 4 a).Explain in details the MOS cascode current mirror with necessary equations. **[7M]**  
b).Illustrate the Bipolar version of current mirror with necessary equations. **[7M]**

**SECTION-III**

- 5 a).Explain the concept of push-pull inverter with neat diagram. **[7M]**

b).Derive the small signal voltage gain and find the zero in plane. [7M]

OR

6 a).Name the different output amplifiers and explain any one in detailed. [7M]

[7M]

b).Illustrate the Architectures of High Gain Amplifiers.

#### **SECTION-IV**

7 a).Explain about the design of Two-stage op-amps. [7M]

b).Demonstrate the Cascode Op-amps. [7M]

OR

8 a).Derive the expression for power-supply rejection ratio of Two-stage op-amps. [7M]

[7M]

b).Write a short note on design aspects of Op-Amp.

#### **SECTION-V**

9 a).Explain about the different types of Open loop comparator [7M]

b).Discuss various types of open loop comparators [7M]

OR

10 Elaborate the Performance improvement of Open-Loop Comparators. [14M]

\*\*\*\*\*

**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****M.Tech I Year I Semester Supplementary Examinations, February/March 2021****CMOS Analog Integrated Circuit Design****(VLSI&ES)**

<b>Roll No</b>										
----------------	--	--	--	--	--	--	--	--	--	--

**Time: 2 hours 30 min****Max. Marks:****70**Answer Any **Five** Questions

All Questions carries equal marks.

\*\*\*\*

- 1 a). Draw the small-signal model for the MOS transistor. Briefly explain each component in that. **[7M]**  
**[7M]**
- b). Explain about the CMOS device Modelling.
- 2 a). Choose values of  $V_{GS} = 1, 2, 3, 4$  and  $5V$ , assume that the channel modulation parameter is zero. Sketch to scale the output characteristics of an enhancement n-channel device if  $V_T = 0.7V$  and  $I_D = 500\mu A$  when  $V_{GS} = 5V$  in saturation. **[7M]**  
**[7M]**
- b). Explain the Large-signal model for the MOS Transistor.
- 3 a). What is Current sink. Explain the general properties of current sink with block diagram? **[7M]**  
**[7M]**
- b). Explain in detailed about MOS switch and MOS Diode. **[7M]**
- 4 a). Write a short note on MOS switch model. **[7M]**  
**[7M]**
- b). Explain about the Bipolar simple current mirror with degeneration helper with necessary equations. **[7M]**

- 5 a).Briefly explain the differential amplifiers. With necessary equation give the large signal analysis of CMOS differential amplifiers. [7M]  
b).Design a CMOS current mirror load differential amplifier. [7M]
- 6 Explain about a) Current Amplifier b) Cascode Amplifier. [14M]
- 7 With neat sketch explain the following [7M]  
a) Characteristics of Op-Amp b) Classification of Op-Amp [7M]
- 8 Explain the following terms with neat sketch. [7M]  
a) Switched capacitor comparators b) Regenerative comparators. [7M]

\*\*\*\*\*

**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****M.Tech I Year - I Semester Regular/Supplementary Examinations,  
January-2020****CMOS Analog Integrated Circuit Design****(VLSI&ES)**

<b>Roll No</b>										
----------------	--	--	--	--	--	--	--	--	--	--

**Time: 3 hours  
70****Max. Marks:**

**Note:** This question paper Consists of 5 Sections. Answer **FIVE** Questions, Choosing ONE Question from each SECTION and each Question carries 14 marks.

\*\*\*

**SECTION-I**

- 1** Analyze the Simple MOS Small-Signal Model with the associated parameters in detail. **[14M]**

OR

- 2** a) Illustrate the formation of MOS transistor using n-well technology and threshold voltage. **[7M]**  
b) Describe the importance of Sub-threshold MOS Model with relevant diagram **[7M]**

**SECTION-II**

- 3** a) Draw the model for a non ideal switch and explain its parameters in detail **[6M]**  
b) Draw and explain about a simple current mirror with Beta helper. **[8M]**

OR

- 4** a) Describe the concept of increasing the output resistance in current sink and the factor by which it is increased? **[7M]**  
b) Differentiate between Wilson current mirror and cascode Wilson current mirror **[7M]**

### **SECTION-III**

- 5** Illustrate the design of Cascode Amplifiers. **[14M]**

OR

- 6** Design a CMOS differential amplifier with current mirror load **[14M]**

### **SECTION-IV**

- 7** a) With a schematic explain about operational-amplifier with its equivalent circuit **[4M]**

- b) Define and explain the following terms **[10M]**

i) Common-Mode Input Range

ii) Common-Mode Rejection Ratio

OR

- 8** a) Briefly explain the Miller compensating networks in op-Amps. **[7M]**

- b) Design the two stage CMOS op-amp to meet the important specifications **[7M]**

### **SECTION-V**

- 9** Describe the following **[7M]**

- (a) Auto zeroing technique (b) Comparator using hysteresis **[7M]**

OR

- 10** a) Discuss the Characterization of Comparator **[7M]**

- b) Explain the types of discrete time Comparator. **[7M]**

\*\*\*\*\*

**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****M.Tech I-Year - I Semester Supplementary Examinations, Dec-18/Jan-19****CMOS Analog Integrated Circuit Design  
(VLSI&ES)**

<b>Roll No</b>										
----------------	--	--	--	--	--	--	--	--	--	--

**Time: 3 hours****Max. Marks: 70**

**Note:** This question paper Consists of 5 Sections. Answer **FIVE** Questions, Choosing ONE Question from each SECTION and each Question carries 14 marks.

\*\*\*\*\*

			Marks	CO	Blooms Level
--	--	--	-------	----	--------------

**SECTION-I**

<b>Q.1.</b>	a)	Draw the physical structure of n channel and p channel MOS transistor using well technology and highlight the importance points?	[7M]	CO1	2
	b)	Explain the importance of BSIM3 model addresses threshold voltage reduction	[7M]	CO1	2
		<b>OR</b>			
<b>Q.2.</b>	a)	Explain the small signal model for the MOS transistor	[7M]	CO2	2
	b)	Explain about CMOS device model?	[7M]		

**SECTION-II**

<b>Q.3.</b>	a)	Explain the the feedback through effects by using a dummy transistor?	[7M]	CO3	2
	b)	Draw the circuit diagram of standard cascode current sink and how its reduces the errors in V or I	[7M]		
		<b>OR</b>			
<b>Q.4.</b>	a)	What do you mean by band gap reference and list the principle involved?	[7M]	CO2	4
	b)	Explain 2 Input NOR gate with depletion NMOS loads. Calculate output high voltage and output low voltage?	[7M]		

**SECTION-III**

<b>Q.5.</b>	a)	Draw the circuit diagram of output amplifier using push pull inverting amplifier and comment on	[7M]	CO3	2
-------------	----	---	------	-----	---

		it?			
	b)	Explain the noise model of a p channel differential amplifier ?	[7M]	CO3	2
		<b>OR</b>			
<b>Q.6.</b>	a)	Explain the design relationships for the differential amplifier?	[7M]	CO3	2
	b)	Draw the circuit diagram of differential mode and common mode circuits using CMOS and explain?	[7M]	CO3	3

#### **SECTION-IV**

<b>Q.7.</b>		What is compensation of Op-amp? Explain the operation of Miller compensation	[14M]	CO4	4
		<b>OR</b>			
<b>Q.8.</b>	a)	Explain the design procedure for the 2 stage CMOS opamp? [7M]	[7M]	CO4	3
	b)	Explain folded cascode op amp? [7M]	[7M]		

#### **SECTION-V**

<b>Q.9.</b>	a)	Explain regenerative comparators? [7M]	[7M]	CO5	4
	b)	Draw the switched capacitor comparator and highlight four important points	[7M]		
		<b>OR</b>			
<b>Q.10.</b>	a)	How to improve the performance of an open loop high gain comparator by auto zeroing?	[7M]	CO5	5
	b)	Explain clamped push pull output comparator	[7M]		



**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****M.Tech I Year I Semester Supplementary Examinations, October/November 2020****CMOS Analog Integrated Circuit Design****(VLSI&ES)**

<b>Roll No</b>										
----------------	--	--	--	--	--	--	--	--	--	--

**Time: 2 hours****Max. Marks: 70**Answer Any **Four** Questions

All Questions carries equal marks.

\*\*\*

- 1 Write a brief note on various passive components that are available in CMOS technologies with relevant layout diagrams
- 2 Analyze the Simple MOS Large-Signal Model with the associated parameters in detail.
- 3 Illustrate the MOS switch operation and various models with application
- 4 Explain the concept of current sink and Design a current sink of  $250\mu\text{A}$  and a  $V_{\text{MIN}}$  of  $0.5\text{V}$  using self biased high-swing cascade current source.
- 5 Illustrate the various types of CMOS inverting Amplifiers and small signal model demonstrating the parasitic capacitances
- 6
  - a) Design a differential Input Current Amplifier
  - b) Briefly give a overview of High Gain Amplifiers Architectures
- 7 Describe the miller compensation of a two stage op amp.

\*\*\*\*\*

**R15**Code No: **R15D6805****MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****M.Tech I-Year - I Semester Supplementary Examinations, Dec-18/Jan-19****CMOS Analog Integrated Circuit Design  
(VLSI&ES)**

<b>Roll No</b>										
----------------	--	--	--	--	--	--	--	--	--	--

**Time: 3 hours****Max. Marks: 75**

**Note:** This question paper Consists of 5 Sections. Answer **FIVE** Questions, Choosing ONE Question from each SECTION and each Question carries 15 marks.

\*\*\*\*\*

			Marks	CO	Blooms Level
--	--	--	-------	----	--------------

**SECTION-I**

<b>Q.1.</b>	a)	Explain about MOS large- signal analysis of CMOS Device Modeling	[10M]	CO1	2
	b)	Explain sub-threshold MOS model Parameters.	[5M]	CO1	2
		<b>OR</b>			
<b>Q.2.</b>	a)	Discuss about the passive components of the MOS transistor.	[7M]	CO2	2
	b)	Write about computer simulation models for MOS transistor	[8M]	CO2	2

**SECTION-II**

<b>Q.3.</b>	a)	Explain the working of current mirror with beta helper	[10M]	CO2	2
	b)	Explain the operation of MOS Diode	[5M]	CO2	1
		<b>OR</b>			
<b>Q.4.</b>		Discuss the Cascode current Mirror and Wilson Current Mirror	[15M]	CO2	2

**SECTION-III**

<b>Q.5.</b>	a)	Explain about working of differential amplifier	<b>[10M]</b>	<b>CO3</b>	<b>3</b>
	b)	Explain the operation of CMOS inverter	<b>[5M]</b>	<b>CO3</b>	<b>3</b>
		<b>OR</b>			
<b>Q.6.</b>		Discuss the principle of High Gain Amplifiers Architectures	<b>[15M]</b>	<b>CO3</b>	<b>1</b>

**SECTION-IV**

<b>Q.7.</b>		Discuss the concept of op amp compensation and give the necessary expressions.	<b>[15M]</b>	<b>CO4</b>	<b>2</b>
		<b>OR</b>			
<b>Q.8.</b>	a)	Explain the Design of Two-Stage Op Amps	<b>[10M]</b>	<b>CO4</b>	<b>6</b>
	b)	What are the various measurements of op amp?	<b>[5M]</b>	<b>CO4</b>	<b>5</b>

**SECTION-V**

<b>Q.9.</b>	a)	Explain the Discrete-Time Comparators.	<b>[7M]</b>	<b>CO4</b>	<b>2</b>
	b)	What is a comparator and list the important characteristics of a comparator	<b>[8M]</b>	<b>CO4</b>	<b>2</b>
		<b>OR</b>			
<b>Q.10.</b>		What are the various forms of improving the slew-rate of a 2-stage op amp and obtain the expression for slew rate of CMOS op amp	<b>[15M]</b>	<b>CO5</b>	<b>2</b>