

ECAD & VLSI DESIGN LABORATORY MANUAL FOR IV B.TECH ECE-I SEMESTER



MALLA REDDY COLLEGE OF ENGINEERING AND TECHNOLOGY
(An Autonomous Institution-UGC, Govt. Of India)
Department Of Electronics & Communication Engg.
Sponsored by CMR Educational Society
(Affiliated to JNTU, Hyderabad)
Maisammguda, Dhulapally
Secunderabad-500100

CONTENTS

CYCLE-I

S.NO.	EXPERIMENT NAME	PAGE NO.
1	Full Adder	1
2	Design Of Ripple Carry ADDER	4
3	Design Of Carry Save Adder	7
4	Design Of Carry Select Adder	10
5	BCD Adder Realization	14
6	Design of a 4 to 1 multiplexer	18
7	Array Multiplier Realization	22
8	Ripple Counters Realization-(Mod -10 & Mod-12)	27
9	Ring Counter Realization	38
10	Pseudo Random Binary Sequence Generator	41
11	Design of Accumulator	44

CYCLE-II

1	CMOS INVERTER	49
2	NAND GATE	53
3	NOR Gate	57
4	XOR GATE	60
5	CMOS 1-Bit Full Adder	64
6	Common Source Amplifier	67
7	Differential Amplifier	71

Experiment 1: Full Adder

Aim:

Realize the full adder using Verilog.

Software Required : QuestaSim Simulator

Theory:

A combinational circuit that performs the addition of three bits is called a half-adder. This circuit needs three binary inputs and produces two binary outputs. One of the input variables designates the augend and other designates the addend. Mostly, the third input represents the carry from the previous lower significant position. The output variables produce the sum and the carry.

The simplified Boolean functions of the two outputs can be obtained as

$$\text{below: Sum } S = x \oplus y \oplus z$$

$$\text{Carry } C = xy + xz + yz$$

Where x, y & z are the two input variables.

Program:

//Gate-level description of Full Adder using two Half Adder

//Description of Half Adder

module halfadder(s,co,x,y);

input x,y;

output s,co;

//Instantiate primitive

gates xor (s,x,y);

and (co,x,y);

endmodule

//Description of Full Adder

module fulladder(s,co,x,y,ci);

input x,y,ci;

output s,co;

wire s1,d1,d2; **//Outputs of first XOR and AND gates**

//Instantiate Half Adder halfadder ha_1(s1,d1,x,y); halfadder

ha_2(s,d2,s1,ci);

or or_gate(co,d2,d1);

endmodule


//Stimulus for testing Full Adder module simulation;

```


reg x,y,ci; wire s,co;
//Instantiate Full Adder fulladder fa_test(s,co,x,y,ci); initial
begin
x=1'b0; y=1'b0; ci=1'b0;
#100 x=1'b0; y=1'b0; ci=1'b1; #100 x=1'b0; y=1'b1; ci=1'b0; #100 x=1'b0;
y=1'b1; ci=1'b1; #100 x=1'b1; y=1'b0; ci=1'b0; #100 x=1'b1; y=1'b0; ci=1'b1;
#100 x=1'b1; y=1'b1; ci=1'b0; #100 x=1'b1; y=1'b1; ci=1'b1; end
endmodule


```

Logic Diagram:

 

Expected Output Waveform:

 

 Simulation Output Waveform:**Result:**

Thus the logic circuit for the Full adder is designed in Verilog HDL and the output is verified.

Experiment 2: Design Of Ripple Carry ADDER Using Verilog HDL

Aim: To Design Ripple Carry Adder using Verilog HDL

Software Required : QuestaSim Simulator

Theory:

The n -bit adder built from n one-bit full adders is known as ripple carry adder because of the carry is computed. The addition is not complete until $n-1^{th}$ adder has computed its S_{n-1} output; that results depends upon c_i input, n and so on down the line, so the critical delay path goes from the 0-bit inputs up through c_i 's to the $n-1$ bit. (We can find the critical path through the n -bit adder without knowing the exact logic in the full adder because the delay through the n -bit carry chain is so much longer than the delay from a and b to s). The ripple-carry adder is area efficient and easy to design but it is when n is large. It can also be called as cascaded full adder.

The simplified Boolean functions of the two outputs can be obtained as below:

$$\text{Sum } s_i = a_i \text{ xor } b_i \text{ xor } c_i$$


$$\text{Carry } c_{i+1} = a_i b_i + b_i c_i + a_i c_i$$

Where x , y & z are the two input variables.

Procedure:

1. The full-adder circuit is designed and the Boolean function is found out.
2. The Verilog Module Source for the circuit is written.
3. It is implemented in Model Sim and Simulated.
4. Signals are provided and Output Waveforms are viewed.

Circuit diagram:

 


Ripple carry adder using verilog code:


```

module ripplecarryadder(s,cout,a,b,cin); output[7:0]s;
    output cout; input[7:0]a,b; input cin;
    wire c1,c2,c3,c4,c5,c6,c7; fulladd fa0(s[0],c1,a[0],b[0],cin); fulladd
    fa1(s[1],c2,a[1],b[1],c1); fulladd fa2(s[2],c3,a[2],b[2],c2); fulladd
    fa3(s[3],c4,a[3],b[3],c3); fulladd fa4(s[4],c5,a[4],b[4],c4); fulladd
    fa5(s[5],c6,a[5],b[5],c5); fulladd fa6(s[6],c7,a[6],b[6],c6); fulladd
    fa7(s[7],cout,a[7],b[7],c7);
endmodule

module fulladd(s,cout,a,b,cin); output s,cout;
    input a,b,cin;
    wire s1,c1,c2;
    xor(s1,a,b);
    xor(s,s1,cin);
    and(c1,a,b);
    and(c2,s1,cin);
    xor(cout,c2,c1);
endmodule

```

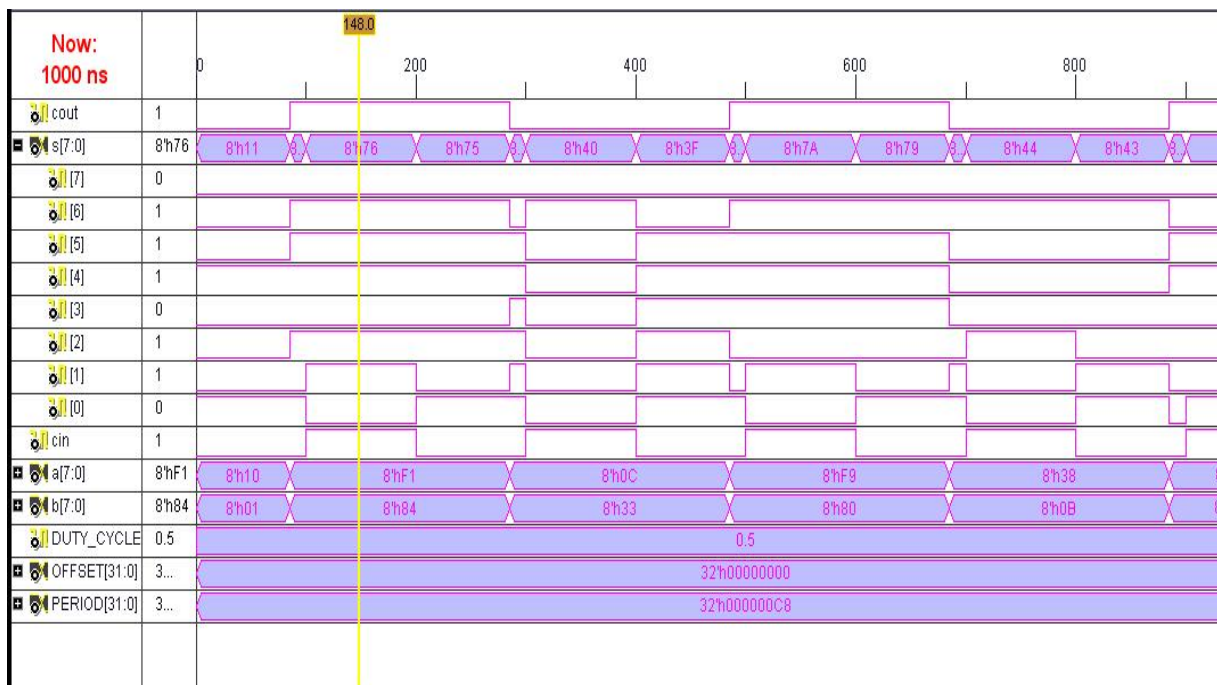Waveform of ripple carry adder:

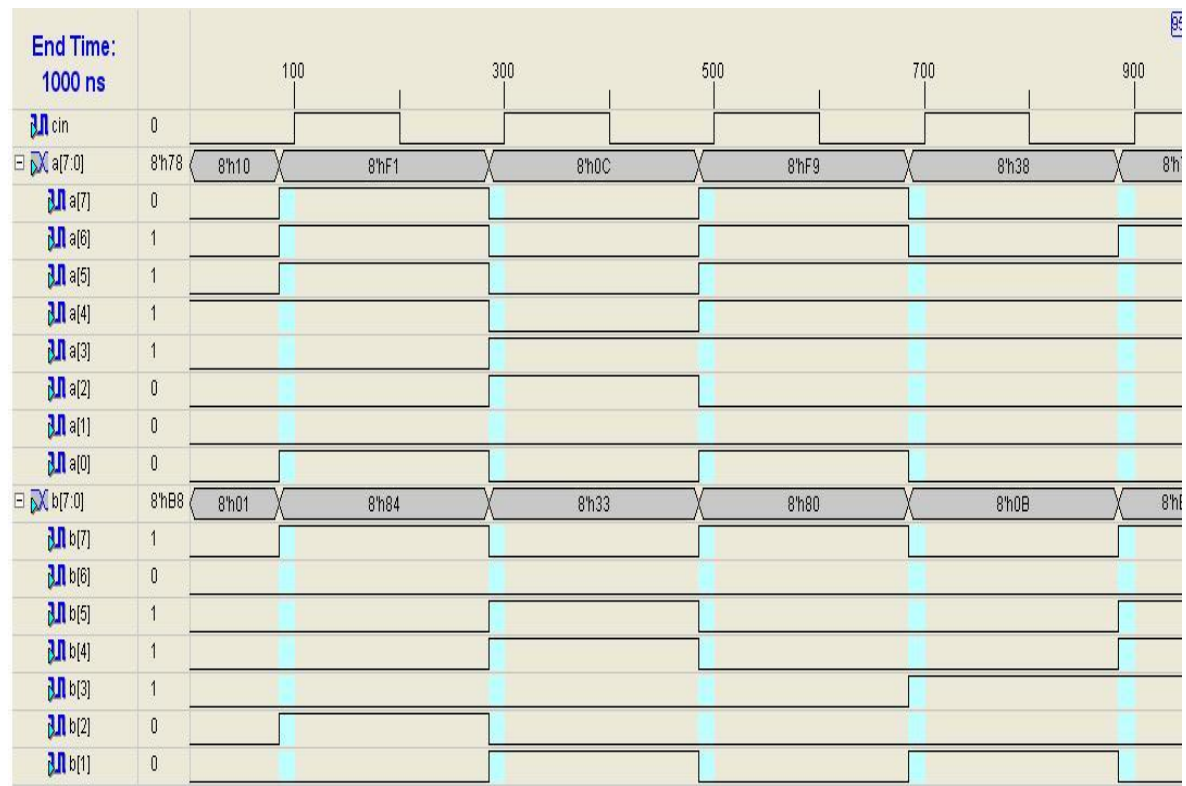Test bench wave form of Ripple carry adder:**RESULT:**

Thus the logic circuit for the Ripple carry adder is designed in Verilog HDL and the output is verified.

Experiment 3: Design Of Carry Save Adder Using Verilog HDL

Aim:

To design Carry Save Adder using Verilog HDL

Software Required : QuestaSim Simulator

Theory:

Carry save adders are suitable when three or more operands are to be added, as in some multiplication schemes. In this adder a separate sum and carry bit is generated for partial results, except when the last operand is added. For example, when three numbers are added, the first two are added using a carry save adder. The partial result is two numbers corresponding to the sum and the carry. The last operand is added using a second carry save adder stage. The results become the sum and carry numbers. Thus a carry save adder reduces the number of operands by one for each adder stage. Finally the sum and carry are added using an adder with carry propagation- for example carry look ahead adder.

Procedure:

1. The carry save adder is designed.
2. The Verilog program source code for the circuit is written.
3. It is implemented in Model Sim and Simulated.
4. Signals are provided and Output Waveforms are viewed.

Carry save adder using Verilog:

```
module  
  carrysaveadder(  
    d,a,b,e); output  
    [4:0]d;  
    input e;  
    input [3:0]a,b;
```


```
wire s1,s2,s3,c0,c1,c2,c3,c4,c5,c6,c7;
```



```
fulladder
a1(d[0],c7,a[0],b[0],
,e); fulladder
a2(s3,c6,a[1],b[1],e
);
```

```
fulladder a3(s2,c5,a[2],b[2],e); fulladder a4(s1,c4,a[3],b[3],e); fulladder
a5(d[1],c3,c7,s3,e); fulladder a6(d[2],c2,c6,c3,s2); fulladder
a7(d[3],c1,c5,s1,c2); fulladder a8(d[4],c0,c4,c1,e); endmodule
```

```
module fulladder(s,c, x,y,z); output s,c;
input x,y,z; xor (s,x,y,z);
assign c = ((x & y )|(y & z)|( z & x)) ; endmodule
```

Logic Diagram:

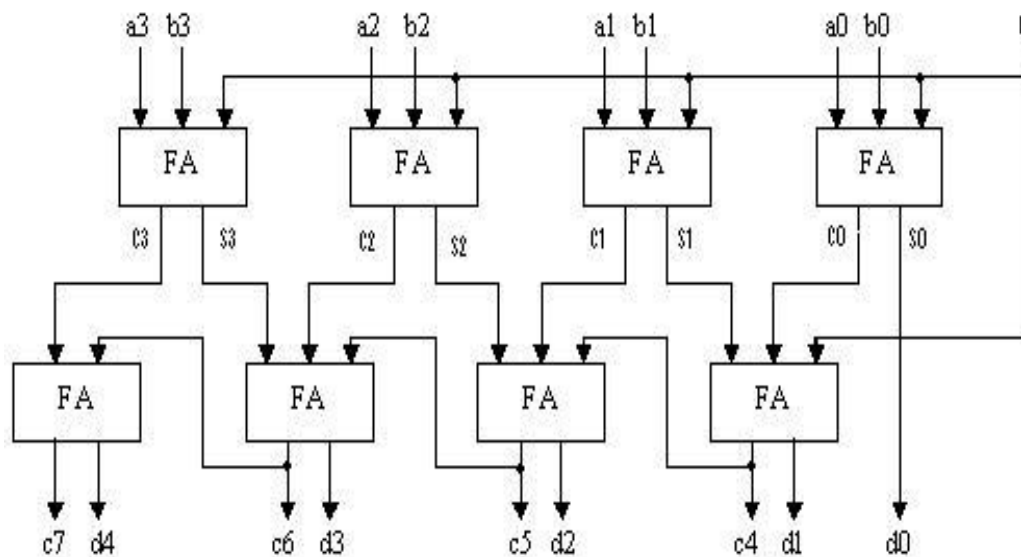

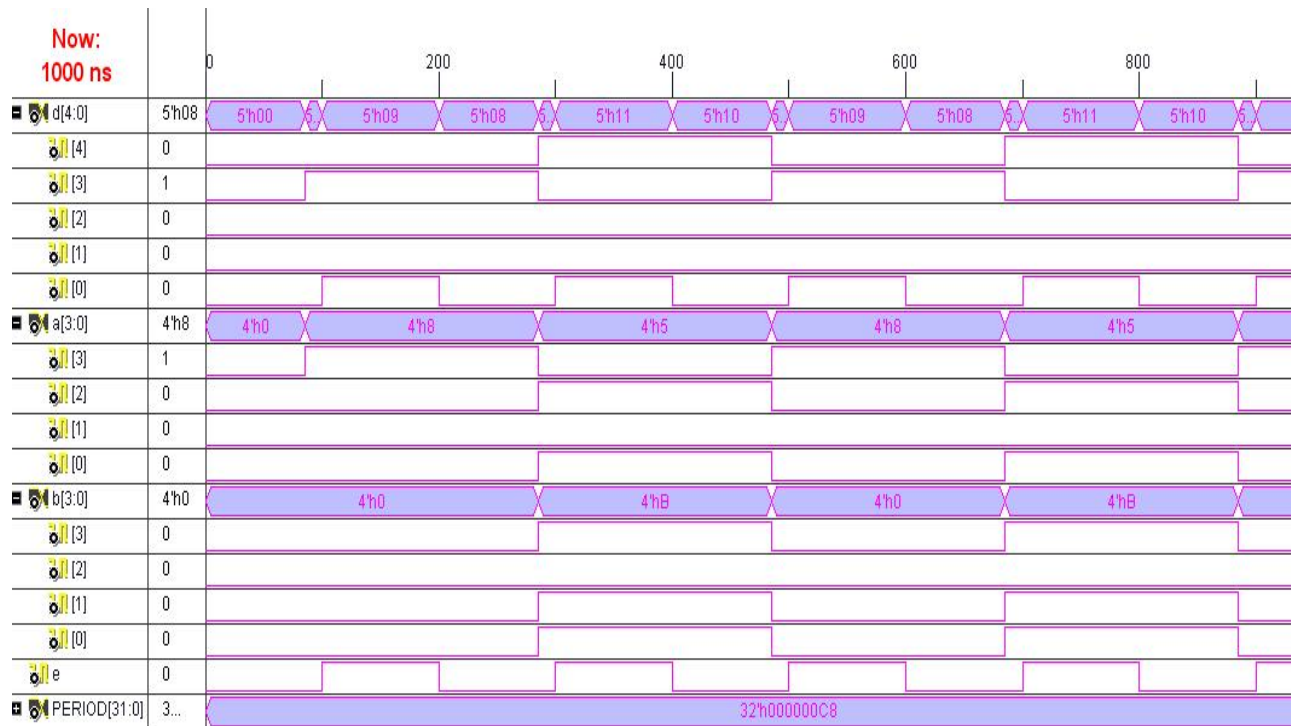 Waveform carry save adder:**Test bench waveform carry-save adder:****RESULT:**

Thus the logic circuit for the carry save adder is designed in Verilog HDL and the output is verified.

Experiment 4: Design Of Carry Select Adder Using Verilog HDL

Aim: To design a Carry Select Adder using Verilog HDL

Software Required : QuestaSim Simulator

Theory:

Carry-select adders use multiple narrow adders to create fast wide adders. A carry-select adder provides two separate adders for the upper words, one for each possibility. A MUX is then used to select the valid result. Consider an 8-bit adder that is split into two 4-bit groups. The lower-order bits are fed into the 4-bit adder 1 to produce the sum bits and a carry-out bit. The higher order bits are used as input to one 4-bit adder and $V_{11} V_{10} V_9 V_8$ are used as input of the another 4-bit adder. Adder U0 calculates the sum with a carry-in of $C3=0$. While U1 does the same only it has a carry-in value of $C3=1$. Both sets of results are used as inputs to an array of 2:1 MUXes. The carry bit from the adder L is used as the MUX select signal. If $=0$ then the results of U0 are sent to the output, while a value of $=1$ selects the results of U1 for $S_{11} S_{10} S_9 S_8$. The carry-out bit is also selected by the MUX array.

Procedure:

1. The carry-select adder circuit is designed and the Boolean function is found out.
2. The Verilog Module Source for the circuit is written.
3. It is implemented in Model Sim and Simulated.
4. Signals are provided and Output Waveforms are viewed.

carry-select adder using verilog:

```


module project2(s,m,x,y,z);
output [0:3]s;
output [1:5]m;
input [0:11]x;
input [0:11]y;
input z;
wire c0,c1,c2,c3,c4,c5,c6,c7,c8,c9,c10,c11,s4,s5,s6,s7,s8,s9,s10,s11;



fulladder f1(s[0],c0,x[0],y[0],z);
fulladder f2(s[1],c1,x[1],y[1],c0);
fulladder f3(s[2],c2,x[2],y[2],c1);
fulladder f4(s[3],c3,x[3],y[3],c2);
fulladder f5(s4,c4,x[4],y[4],c3);
fulladder f6(s5,c5,x[5],y[5],c4);
fulladder f7(s6,c6,x[6],y[6],c5);
fulladder f8(s7,c7,x[7],y[7],c6);
fulladder f9(s8,c8,x[8],y[8],~c3);
fulladder f10(s9,c9,x[9],y[9],c8);
fulladder f11(s10,c10,x[10],y[10],c9);
fulladder f12(s11,c11,x[11],y[11],c10);

muxer mu1(m[1],s4,s8,c3);
muxer mu2(m[2],s5,s9,c3);
muxer mu3(m[3],s6,s10,c3);
muxer mu4(m[4],s7,s11,c3);
muxer mu5(m[5],c7,c11,c3);
endmodule

module fulladder (s,c,x,y,z); output s,c;
input x,y,z; xor (s,x,y,z);
assign c = ((x & y) | (y & z) | (z & x));
endmodule
module muxer (m,s1,s2,c);
output m;
input s1,s2,c;
wire f,g,h; not (f,c);
and (g,s1,c); and (h,s2,f);
or (m,g,h);
endmodule

```

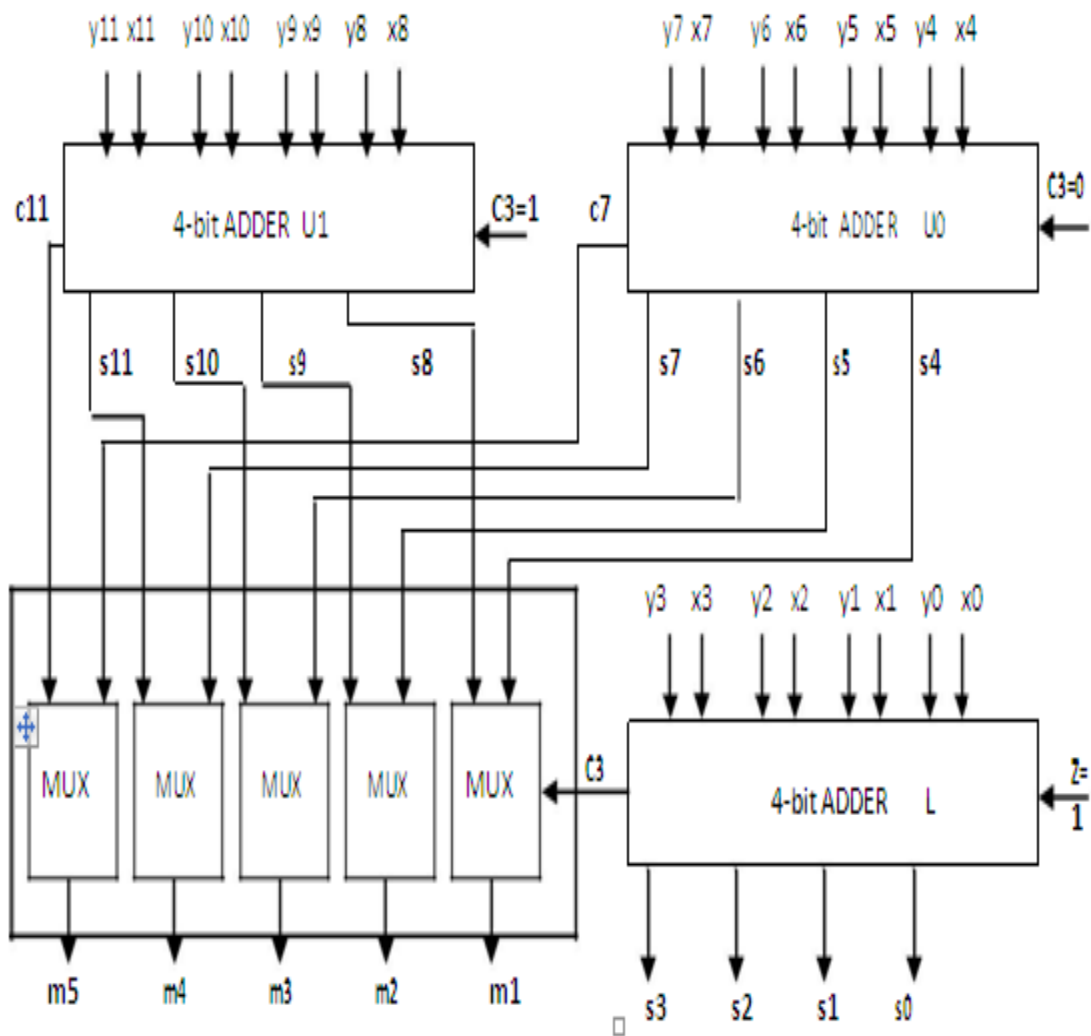Logic Diagram:

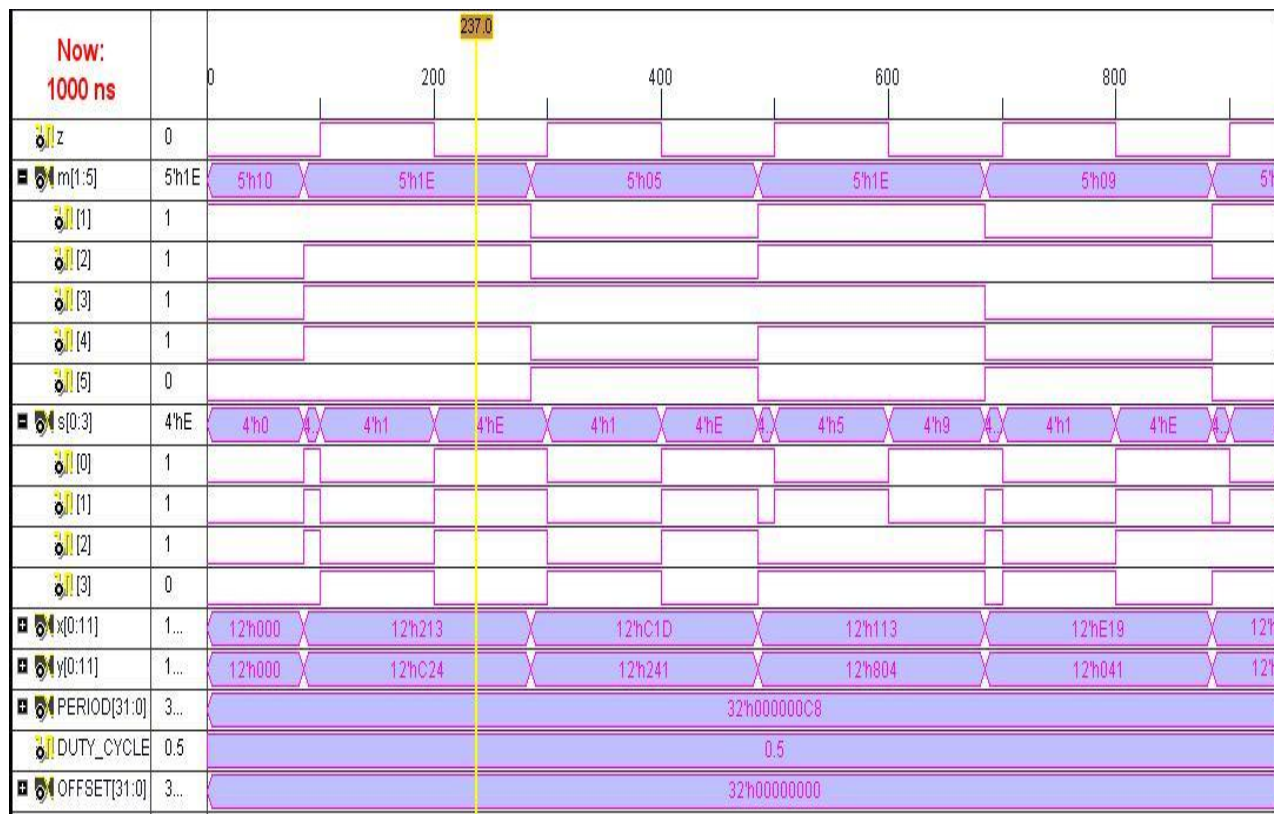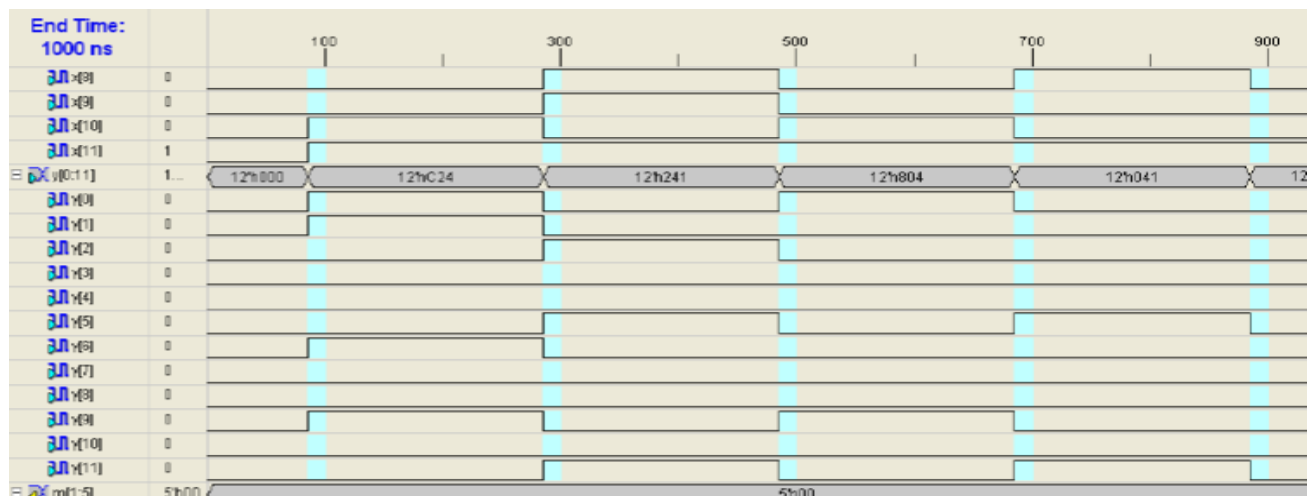Waveform of carry-select adder:**Test bench waveform of carry-select adder:****RESULT:**

Thus the logic circuit for the carry select adder is designed in Verilog HDL and the output is verified.

Experiment 5: BCD Adder Realization In Verilog HDL**Aim:**

To design a BCD adder circuit using Verilog HDL

Software Required: QuestaSim Simulator

Theory:

A BCD adder is the circuit that adds two BCD digits in parallel and produces a sum digit also in BCD. The input digit does not exceed 9, the output sum cannot be greater than 9+9+1=19, the 1 in the sum being an input carry. Suppose we apply two decimal digits, together with the input carry, are first added in the top 4-bit binary adder to produce the binary sum. When the output carry is equal to zero, nothing is added in the binary sum. When it is equal to one, binary 0110 is added to binary sum through the bottom 4-bit binary adder. Output generated from bottom binary adder can be ignored.

The output carry can be expressed in Boolean function

$$k = c_4 + s_3s_2 + s_3s_1$$

Procedure:

1. The BCD adder circuit is designed and the Boolean function is found out.
2. The VHDL program source code for the circuit is written.
3. It is implemented in Model Sim and Simulated.
4. Signals are provided and Output Waveforms are viewed.

Bcd adder using Verilog :

```

module
bcdadder(s,k,a,b,c,d,e);
output [4:7] s;
inout k;
input [0:3]a,b;
input c,d,e;
wire c1,c2,c3,c4,s0,s1,s2,s3,e1,e2,e3,e4;

fulladder f1(s0,c1,a[0],b[0],c);
fulladder f2(s1,c2,a[1],b[1],c1);
fulladder f3(s2,c3,a[2],b[2],c2);
fulladder f4(s3,c4,a[3],b[3],c3);


```



```
assign k=((s3 & s2) | (s3 & s1)| c4);
```

```
fulladder f5(s[4],e1,s0,d,e);
fulladder f6(s[5],e2,s1,k,e1);
fulladder f7(s[6],e3,s2,k,e2);
fulladder f8(s[7],e4,s3,d,e3);
endmodule
```


```
module fulladder(s,ca,a,b,c); output
s,ca;
input a,b,c;
xor(s,a,b,c);
assign ca=((a & b)|(b & c)| (c & a));
endmodule
```

Logic Diagram:

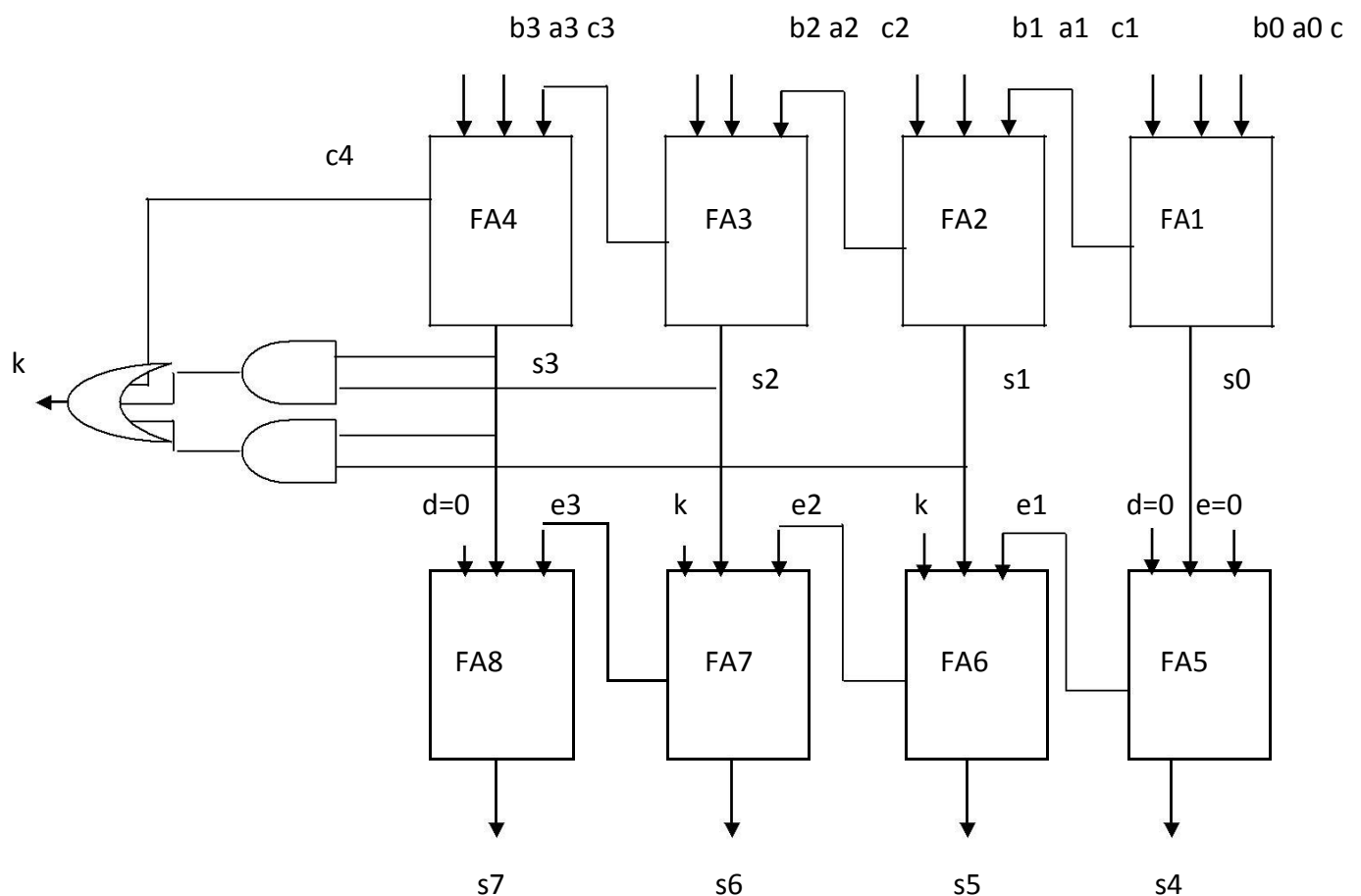

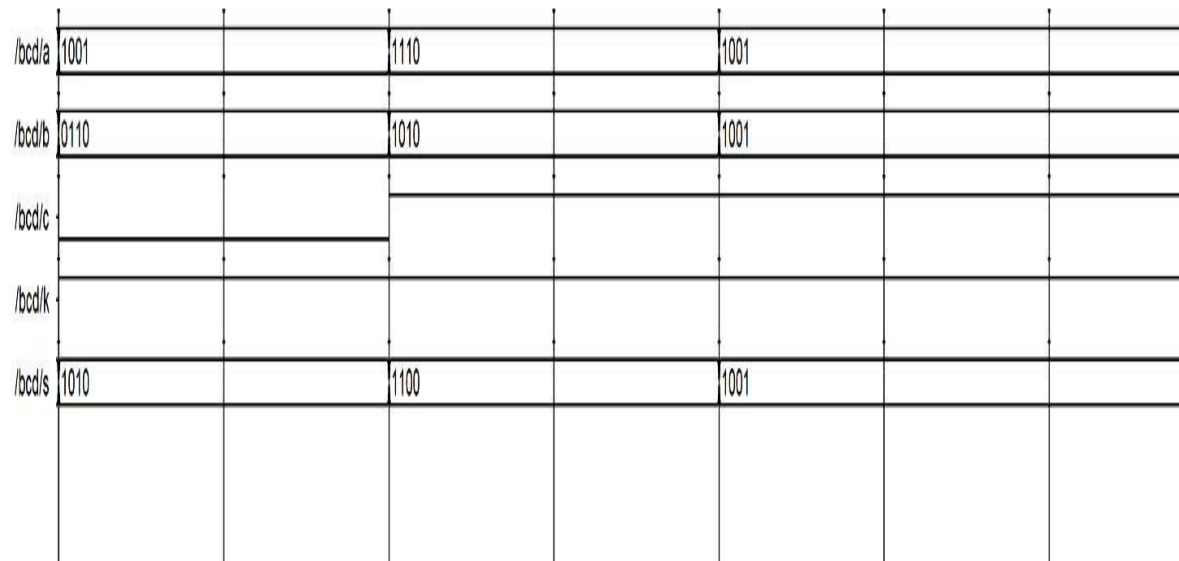 Waveform:**Simulation output:**

Simulation output of BCD Adder

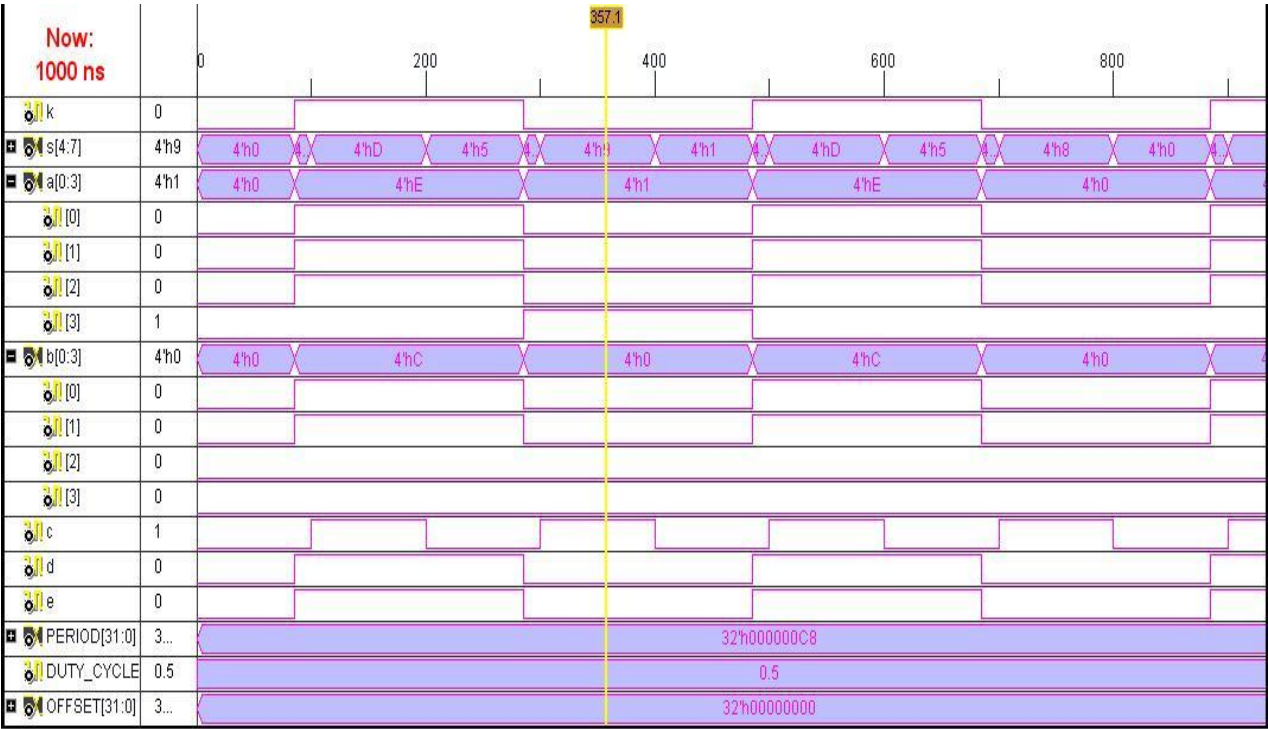

Result: The BCD adder circuit using Verilog HDL has been simulated.

Experiment 6: Design of Multiplexers

Aim: Design a 4 to 1 multiplexer circuit in Verilog.

Software Required: QuestaSim Simulator

Theory:

A digital multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line. Multiplexing means transmitting a large number of information units over a smaller number of channels or lines. The selection of a particular input line is controlled by a set of selection lines. Normally, there are 2^n input lines and n selection lines whose bit combinations determine which input is selected. A multiplexer is also called a data selector, since it selects one of many inputs and steers the binary information to the output lines. Multiplexer ICs may have an enable input to control the operation of the unit. When the enable input is in a given binary state (the disable state), the outputs are disabled, and when it is in the other state (the enable state), the circuit functions as normal multiplexer. The enable input (sometimes called strobe) can be used to expand two or more multiplexer ICs to digital multiplexers with a larger number of inputs.


The size of the multiplexer is specified by the number 2^n of its input lines and the single output line. In general, a 2^n – to – 1 line multiplexer is constructed from an n – to 2^n decoder by adding to it 2^n input lines, one to each AND gate. The outputs of the AND gates are applied to a single OR gate to provide the 1 – line output.

Procedure:

1. The multiplexer circuit is designed and the Boolean function is found out.
2. The Verilog Module Source for the circuit is written.
3. It is implemented in Model Sim and Simulated.
4. Signals are provided and Output Waveforms are viewed.

Truth table:

INPUT		OUTPUT
s[1]	s[0]	y
0	0	D[0]
0	1	D[1]
1	0	D[2]
1	1	D[3]

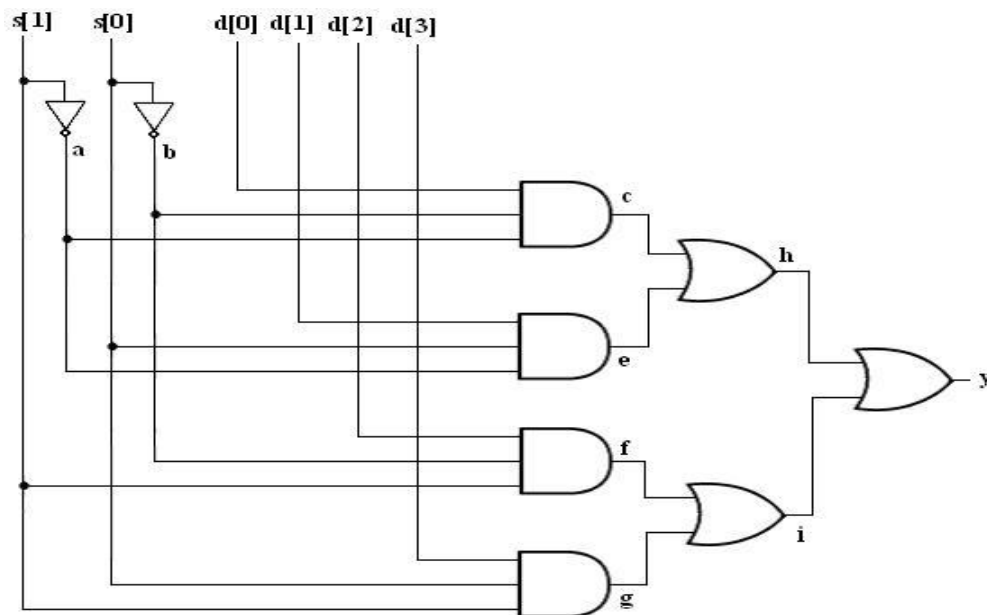Logic Diagram:**4 to 1 Multiplexer:****Multiplexer using verilog code:** module multiplexer(y,d,s); output y;

input [3:0] d; input [1:0] s; wire a,b,c,e,f,g,h,i;

//Instantiate Primitive gates not (a,s[1]);

not (b,s[0]); and (c,d[0],b,a);

and (e,d[1],s[0],a); and (f,d[2],b,s[1]);

and (g,d[3],s[0],s[1]); or (h,c,e);

or (i,f,g); or (y,h,i); endmodule

//Stimulus for testing 4 to 1 Multiplexer

module simulation;

reg [3:0]d; reg [1:0]s; wire y;

//Instantiate the 4 to 1 Multiplexer multiplexer mux_t(y,d,s);

initial begin

```


s=2'b00;d[0]=1'b1;d[1]= 1'b0;d[2]= 1'b0;d[3]= 1'b0; #100
s=2'b00;d[0]= 1'b0;d[1]= 1'b1;d[2]= 1'b1;d[3]= 1'b1; #100
s=2'b01;d[0]= 1'b0;d[1]= 1'b1;d[2]= 1'b0;d[3]= 1'b0; #100
s=2'b01;d[0]= 1'b1;d[1]= 1'b0;d[2]= 1'b1;d[3]= 1'b1; #100
s=2'b10;d[0]= 1'b0;d[1]= 1'b0;d[2]= 1'b1;d[3]= 1'b0; #100

```


```

s=2'b10;d[0]= 1'b1;d[1]= 1'b1;d[2]= 1'b0;d[3]= 1'b1; #100
s=2'b11;d[0]= 1'b0;d[1]= 1'b0;d[2]= 1'b0;d[3]= 1'b1; #100
s=2'b11;d[0]= 1'b1;d[1]= 1'b1;d[2]= 1'b1;d[3]= 1'b0; end
endmodule


```

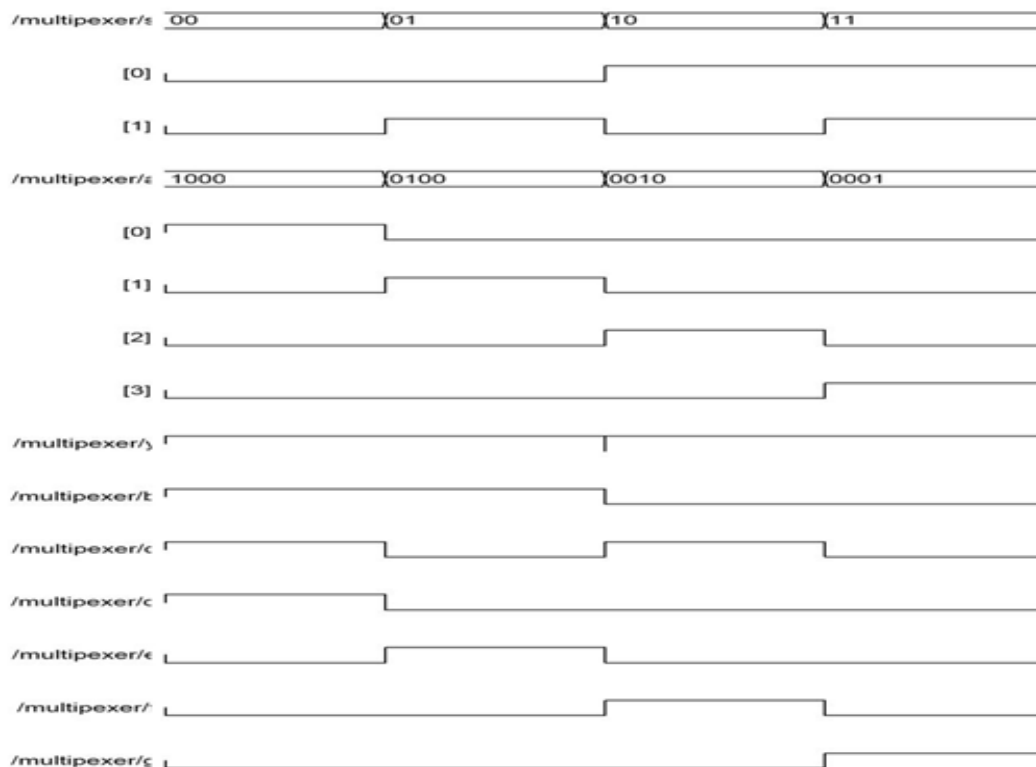Waveform:

Waveform of multiplexers

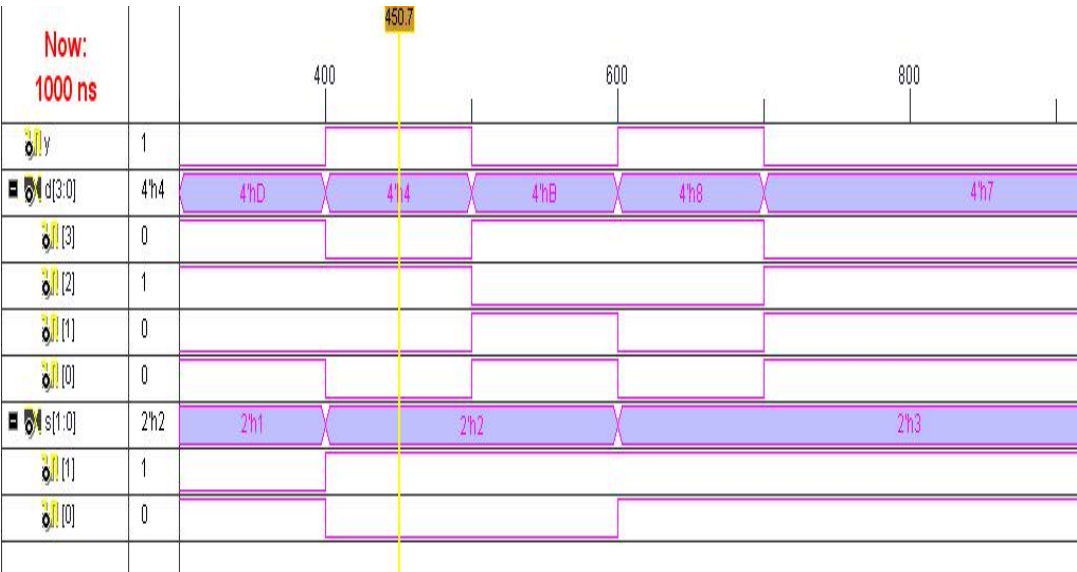

Test bench waveform of multiplexers:

 

RESULT:

Thus the multiplexer is designed in Verilog HDL and the output is verified.

Experiment 7: Array Multiplier Realization In Verilog Hdl

Aim:

To design an array multiplier circuit for 4 inputs and 8 outputs using VHDL.

Software Required: QuestaSim Simulator

Theory:

Binary multiplication can be accomplished by several approaches. The approach presented here is realized entirely with combinational circuits. Such a circuit is called an **array multiplier**. The term array is used to describe the multiplier because the multiplier is organized as an array structure. Each row, called a *partial product*, is formed by a bit-by-bit multiplication of each operand. For example, a partial product is formed when each bit of operand 'a' is multiplied by b0, resulting in a3b0, a2b0, a1b0, a0b0. The binary multiplication table is identical to the AND truth table. Each product bit {o(x)}, is formed by adding partial product columns. The product equations, including the carry-in {c(x)}, from column c(x-1), are (the plus sign indicates addition not OR). Each product term, p(x), is formed by AND gates and collection of product terms needed for the multiplier. By adding appropriate p term outputs, the multiplier output equations are realized, as shown in figure.

4X 4 Array Multiplier:

				a3	a2	a1	a0
				b3	b2	b1	b0
			a3b0	a2b0	a1b0	a0b0	
		a3b1	a2b1	a1b1	a0b1		
	a3b2	a2b2	a1b2	a0b2			
a3b3	a2b3	a1b3	a0b3				
<hr/>							
o7	o6	o5	o4	o3	o2	o1	

a0b0 = p0	a1b2 = p8
a1b0 = p1	a0b3 = p9
a0b1 = p2	a3b1 = p10
a2b0 = p3	a2b2 = p11

$a_1b_1 = p_4$ $a_1b_3 = p_{12}$
 $a_0b_2 = p_5$ $a_3b_2 = p_{13}$
 $a_3b_0 = p_6$ $a_2b_3 = p_{14}$
 $a_2b_1 = p_7$ $a_3b_3 = p_{15}$

Truth Table:

A	B	A X B
0	0	0
0	1	0
1	0	0
1	1	1

Program:

```

module mmmm(m,a,b);

input [3:0]a; input [3:0]b; output [7:0]m; wire [15:0]p; wire
[12:1]s; wire [12:1]c;

and(p[0],a[0],b[0]);
and(p[1],a[1],b[0]);
and(p[2],a[0],b[1]);
and(p[3],a[2],b[0]);
and(p[4],a[1],b[1]);
and(p[5],a[0],b[2]);
and(p[6],a[3],b[0]);
and(p[7],a[2],b[1]);
and(p[8],a[1],b[2]);

and(p[9],a[0],b[3]);

```

```

and(p[10],a[3],b[1]);
and(p[11],a[2],b[2]);
and(p[12],a[1],b[3]);
and(p[13],a[3],b[2]);
and(p[14],a[2],b[3]);
and(p[15],a[3],b[3]);

half ha1(s[1],c[1],p[1],p[2]); half ha2(s[2],c[2],p[4],p[3]); half ha3(s[3],c[3],p[7],p[6]);

full fa4(s[4],c[4],p[11],p[10],c[3]); full fa5(s[5],c[5],p[14],p[13],c[4]); full
fa6(s[6],c[6],p[5],s[2],c[1]); full fa7(s[7],c[7],p[8],s[3],c[2]); full
fa8(s[8],c[8],p[12],s[4],c[7]); full fa9(s[9],c[9],p[9],s[7],c[6]);

half ha10(s[10],c[10],s[8],c[9]);
full fa11(s[11],c[11],s[5],c[8],c[10]); full fa12(s[12],c[12],p[15],s[5],c[11]);


buf(m[0],p[0]);
buf(m[1],s[1]);
buf(m[2],s[6]);
buf(m[3],s[9]);
buf(m[4],s[10]);
buf(m[5],s[11]);
buf(m[6],s[12]);
buf(m[7],c[12]);


endmodule

module half(s,co,x,y); input x,y;
output s,co;
//Instantiate primitive gates xor (s,x,y);
and (co,x,y); endmodule

//Description of Full Adder module full(s,co,x,y,ci); input x,y,ci;
output s,co;
wire s1,d1,d2; //Outputs of first XOR and AND gates //Instantiate Half Adder
half ha_1(s1,d1,x,y); half ha_2(s,d2,s1,ci); or or_gate(co,d2,d1);
endmodule

```

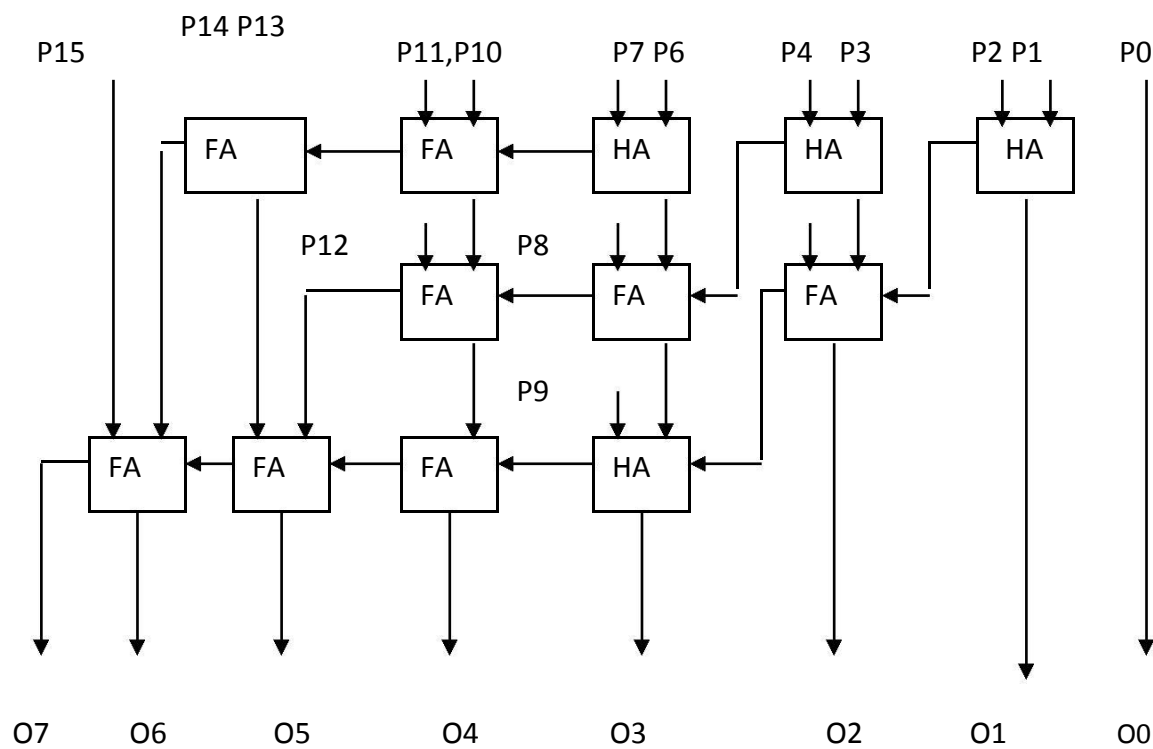Logic Diagram:

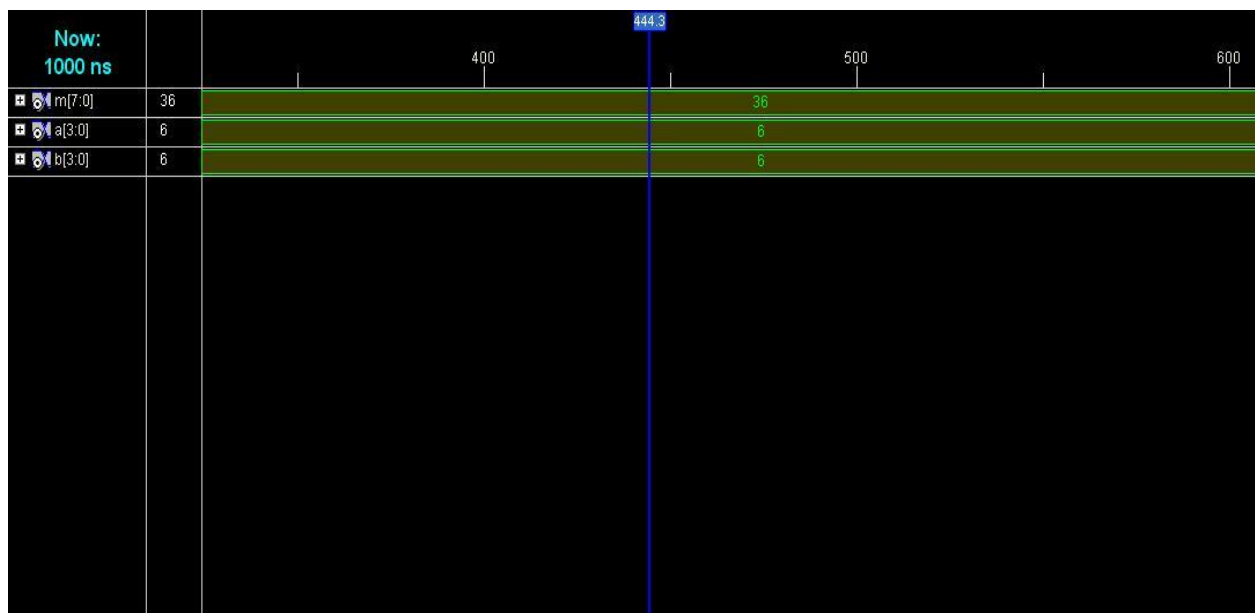Wave Form:**RESULT:**

Thus an array multiplier circuit for 4 inputs and 8 outputs using VHDL is designed and the output is verified.

Experiment 8: Ripple Counter Realization In Verilog HDL

Aim:

To realize an asynchronous ripple counter in Verilog

Software Required: QuestaSim Simulator

Theory:

In a ripple counter, the flip-flop output transition serves as a source for triggering other flip-flops. In other words, the Clock Pulse inputs of all flip-flops (except the first) are triggered not by the incoming pulses, but rather by the transition that occurs in other flip-flops. A binary ripple counter consists of a series connection of complementing flip-flops (JK or T type), with the output of each flip-flop connected to the Clock Pulse input of the next higher-order flip-flop. The flip-flop holding the LSB receives the incoming count pulses. All J and K inputs are equal to 1. The small circle in the Clock Pulse /Count Pulse indicates that the flip-flop complements during a negative-going transition or when the output to which it is connected goes from 1 to 0. The flip-flops change one at a time in rapid succession, and the signal propagates through the counter in a ripple fashion. A binary counter with reverse count is called a binary down-counter. In binary down-counter, the binary count is decremented by 1 with every input count pulse.

Procedure:

1. The 4 bit asynchronous ripple counter circuit is designed.
2. The Verilog Module Source for the circuit is written.
3. It is implemented in Model Sim and Simulated.
4. Signals are provided and Output Waveforms are viewed.

//Structural description of Ripple Counter

```
module ripplecounter(A0,A1,A2,A3,COUNT,RESET);
output A0,A1,A2,A3;
input COUNT,RESET;
//Instantiate Flip-Flop
FF F0(A0,COUNT,RESET); FF
F1(A1,A0,RESET);
FF F2(A2,A1,RESET);
FF F3(A3,A2,RESET);
endmodule
```

//Description of Flip-Flop

```

module FF(Q,CLK,RESET); output Q;
input CLK,RESET; reg Q;
always @(negedge CLK or negedge RESET) if(~RESET)
Q=1'b0; else
Q=(~Q); endmodule

```

//Stimulus for testing Ripple Counter

```

module simulation; reg COUNT;
reg RESET;
wire A0,A1,A2,A3;


```

//Instantiate Ripple Counter

```



ripplecounter rc_t(A0,A1,A2,A3,COUNT,RESET); always
#5 COUNT=~COUNT; initial
begin
COUNT=1'b0;
RESET=1'b0; #10 RESET=1'b1; end
endmodule

```

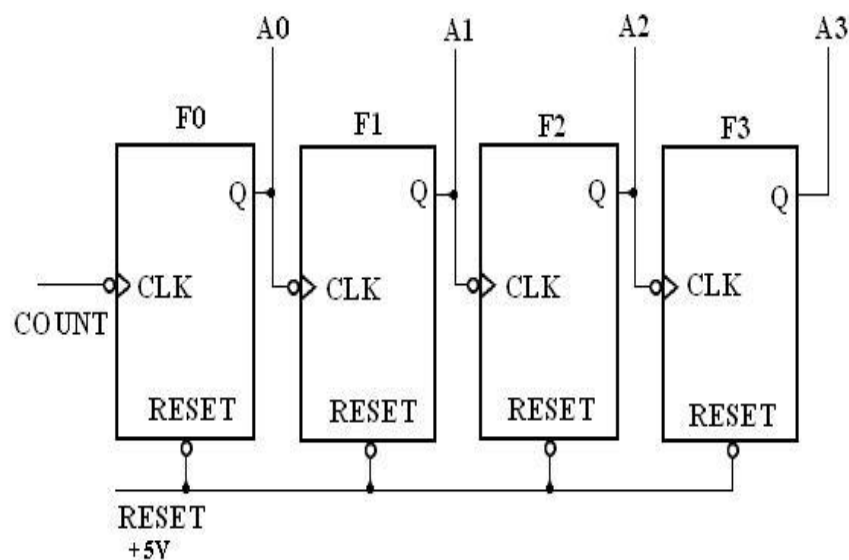LOGIC DIAGRAM:**4-Bit Ripple Counter:**


TRUTH TABLE:

COUNT	A0	A1	A2	A3
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	1	0	0
4	0	0	1	0
5	1	0	1	0
6	0	1	1	0
7	1	1	1	0
8	0	0	0	1
9	1	0	0	1
10	0	1	0	1
11	1	1	0	1
12	0	0	1	1
13	1	0	1	1
14	0	1	1	1
15	1	1	1	1

  Waveform of ripple counter:**Testbench waveform of ripple counter:**

LOGIC DIAGRAM:

MOD-10 Ripple Counter:

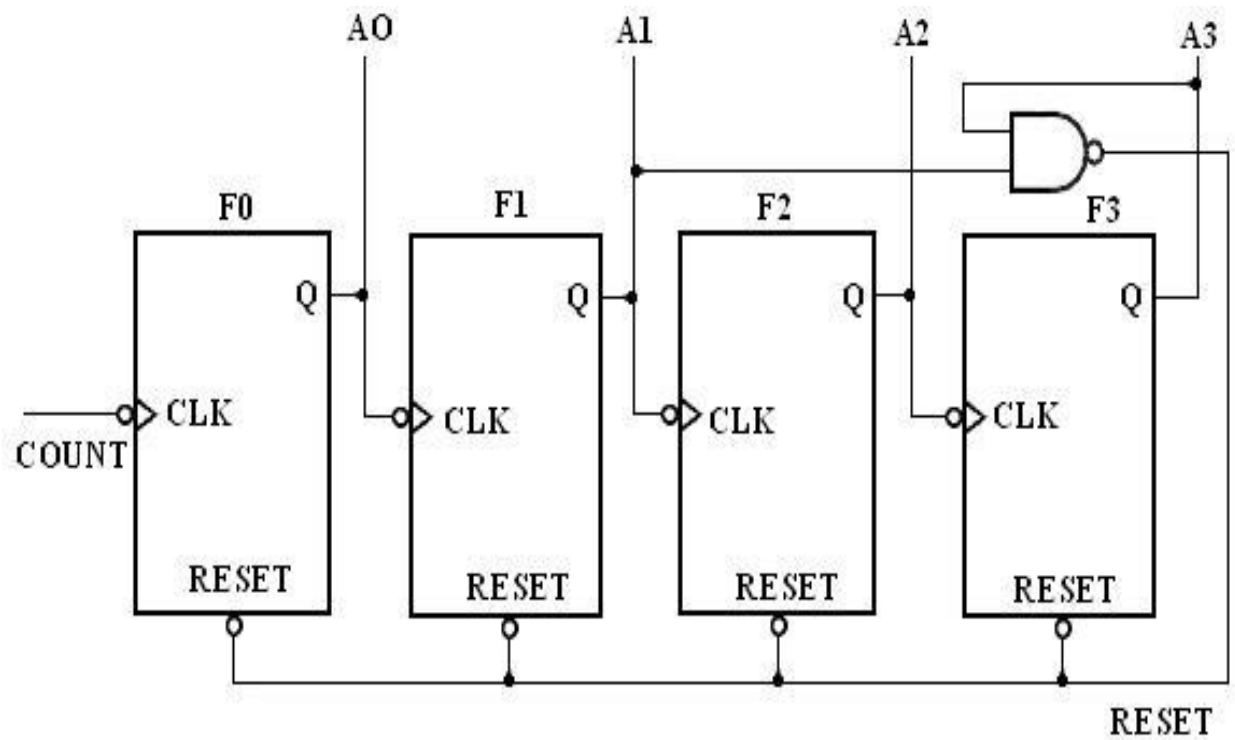

TRUTH TABLE:

COUNT	A0	A1	A2	A3
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	1	0	0
4	0	0	1	0
5	1	0	1	0
6	0	1	1	0
7	1	1	1	0
8	0	0	0	1
9	1	0	0	1
10	0	0	0	0

```

//Structural description of MOD10 Counter
module MOD10(A0,A1,A2,A3,COUNT); output
A0,A1,A2,A3;
input COUNT;
wire RESET;
//Instantiate Flip-Flop
FF F0(A0,COUNT,RESET); FF
F1(A1,A0,RESET);
FF F2(A2,A1,RESET);
FF F3(A3,A2,RESET);
//Instantiate Primitive gate
nand (RESET,A1,A3);
endmodule

```

```

//Description of Flip-Flop
module FF(Q,CLK,RESET);
output Q;

```

```


input CLK,RESET;
reg Q=1'b0;
always @(negedge CLK or negedge RESET)
if(~RESET)
Q=1'b0;
else
Q=(~Q);
endmodule

//Stimulus for testing MOD10 Counter module simulation;
reg COUNT;
wire A0,A1,A2,A3;
//Instantiate MOD10 Counter
MOD10 MOD10_TEST(A0,A1,A2,A3,COUNT); always
#10 COUNT=~COUNT; initial
begin
COUNT=1'b0; end


Endmodule

```

Waveform of mod 10 Counter:

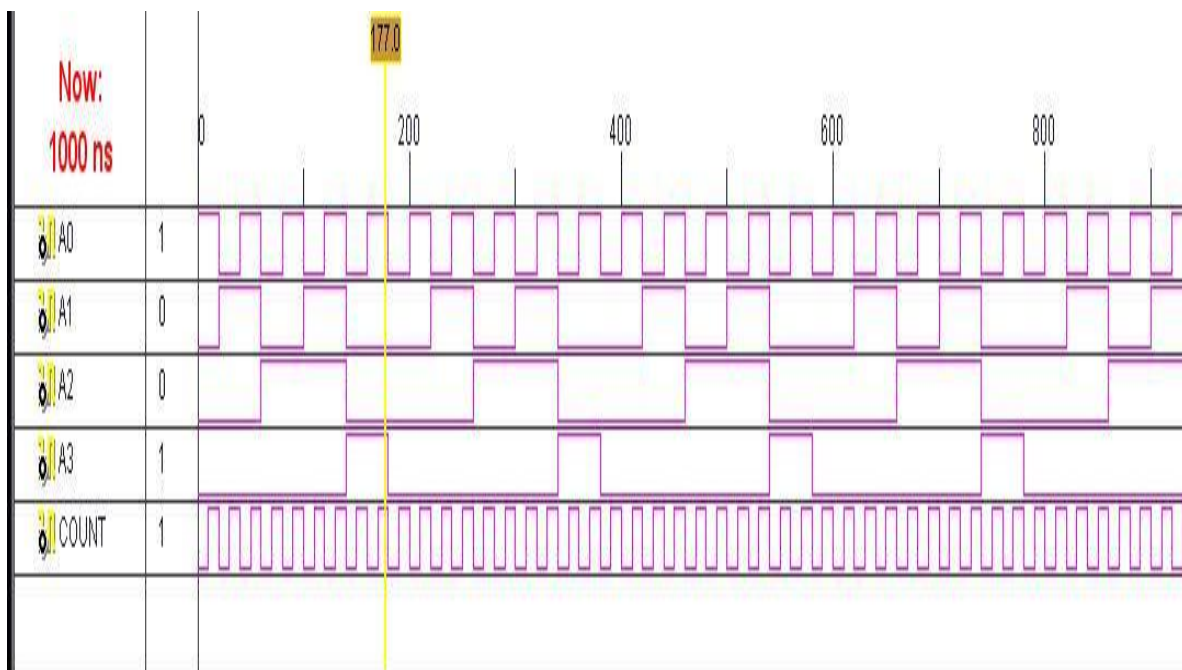


Testbench waveform of mod 10:

 

LOGIC DIAGRAM:

MOD-12 Ripple Counter:

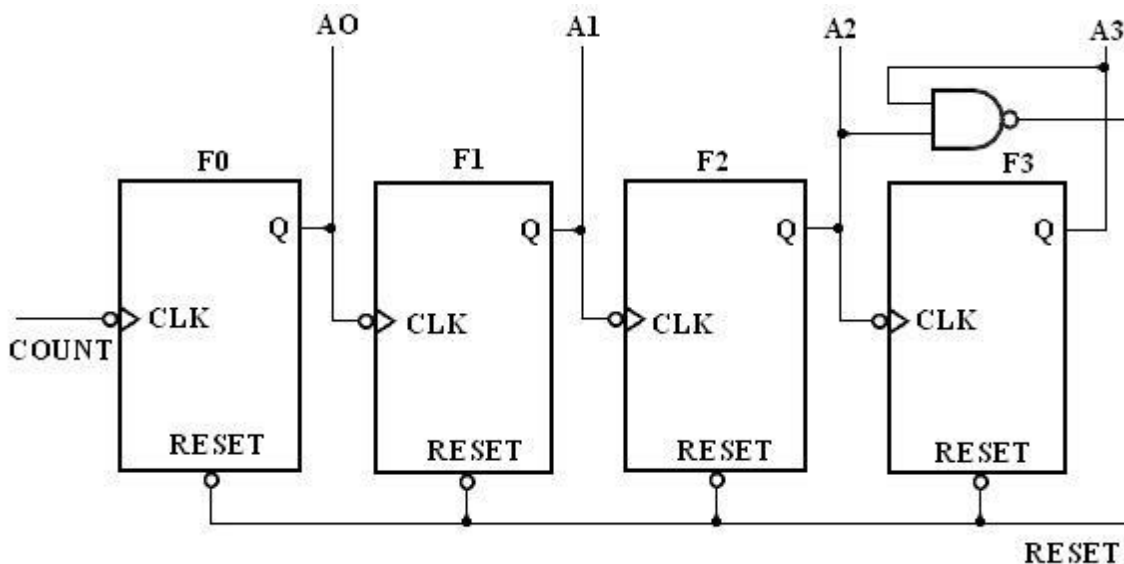

TRUTH TABLE:

COUNT	A0	A1	A2	A3
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	1	0	0
4	0	0	1	0
5	1	0	1	0
6	0	1	1	0
7	1	1	1	0
8	0	0	0	1
9	1	0	0	1
10	0	1	0	1
11	1	1	0	1
12	0	0	0	0

//Structural description of MOD12 Counter


```
module MOD12(A0,A1,A2,A3,COUNT); output A0,A1,A2,A3;
input COUNT; wire RESET;
//Instantiate Flip-Flop
FF F0(A0,COUNT,RESET); FF F1(A1,A0,RESET);
FF F2(A2,A1,RESET);
FF F3(A3,A2,RESET);
//Instantiate Primitive gates nand (RESET,A2,A3); endmodule
```

//Description of Flip-Flop

```
module FF(Q,CLK,RESET); output Q;
input CLK,RESET; reg Q=1'b0;
always @(negedge CLK or negedge RESET) if(~RESET)
Q=1'b0; else
Q=(~Q); endmodule
```

//Stimulus for testing MOD12 Counter

```
module simulation; reg COUNT;
wire A0,A1,A2,A3;
//Instantiate MOD12 Counter
MOD12 MOD12_TEST(A0,A1,A2,A3,COUNT); always
#10 COUNT=~COUNT; initial
begin
COUNT=1'b0; end endmodule
```

 Waveform of mod 12 counter :**Testbench waveform of mod 12 counter:****RESULT:**

Thus the ripple counter is designed in Verilog HDL and the output is verified.

Experiment 9: Ring Counter Realization In Verilog HDL

AIM:

To realize a ring counter in Verilog and VHDL.

Software Required: QuestaSim Simulator

Theory:


A ring counter is a circular shift register with only one flip-flop being set at any particular time; all others are cleared. The single bit is shifted from one flip-flop to the other to produce the sequence of timing signals.

Procedure:


1. The 4 bit ring counter circuit is designed.
2. The Verilog Module Source for the circuit is written.
3. It is implemented in Model Sim and Simulated.
4. Signals are provided and Output Waveforms are viewed.



Binary Ring Counter Design in Verilog

```
module my_ringcntvlog (q,clk,reset);
output [0 : 3]q;
input clk,reset;
reg [0 : 3] q;
always @ (negedge clk or reset)
begin
    if (~reset)
        q = 4'b 1000;
    else if (reset)
        begin
            q[0] <= q[3];
            q[1] <= q[0];
            q[2] <= q[1];
            q[3] <= q[2];
        end
    end
end
endmodule
```

 Logic Diagram:**Truth Table:**

Input		Output		
Clk	Reset	Qa	Qb	Qc
1	1	1	0	0
1	0	0	1	0
1	0	0	0	1
1	0	1	0	0
1	0	0	1	0

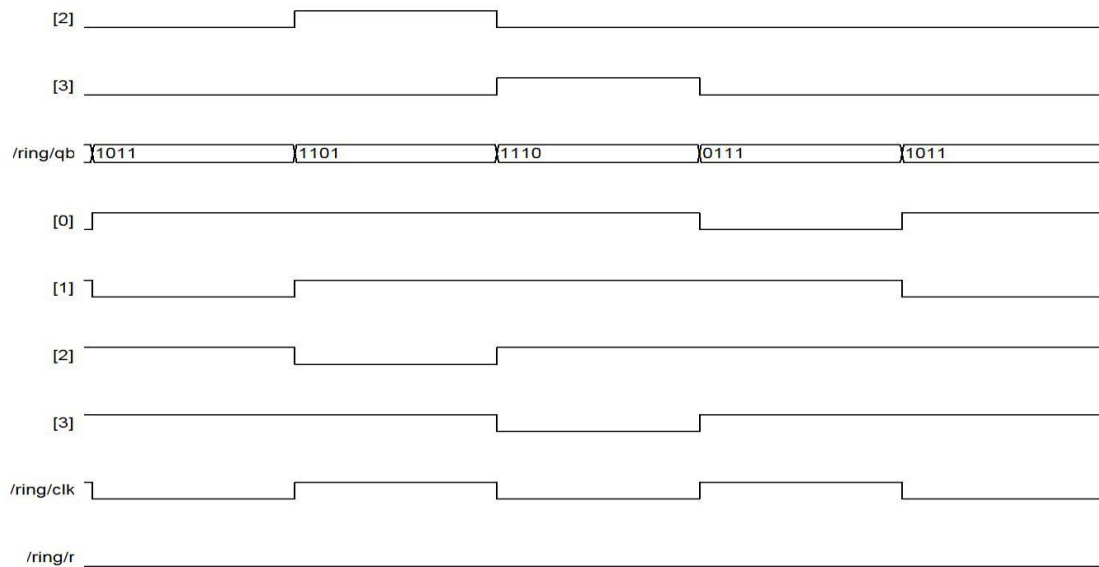Waveforms

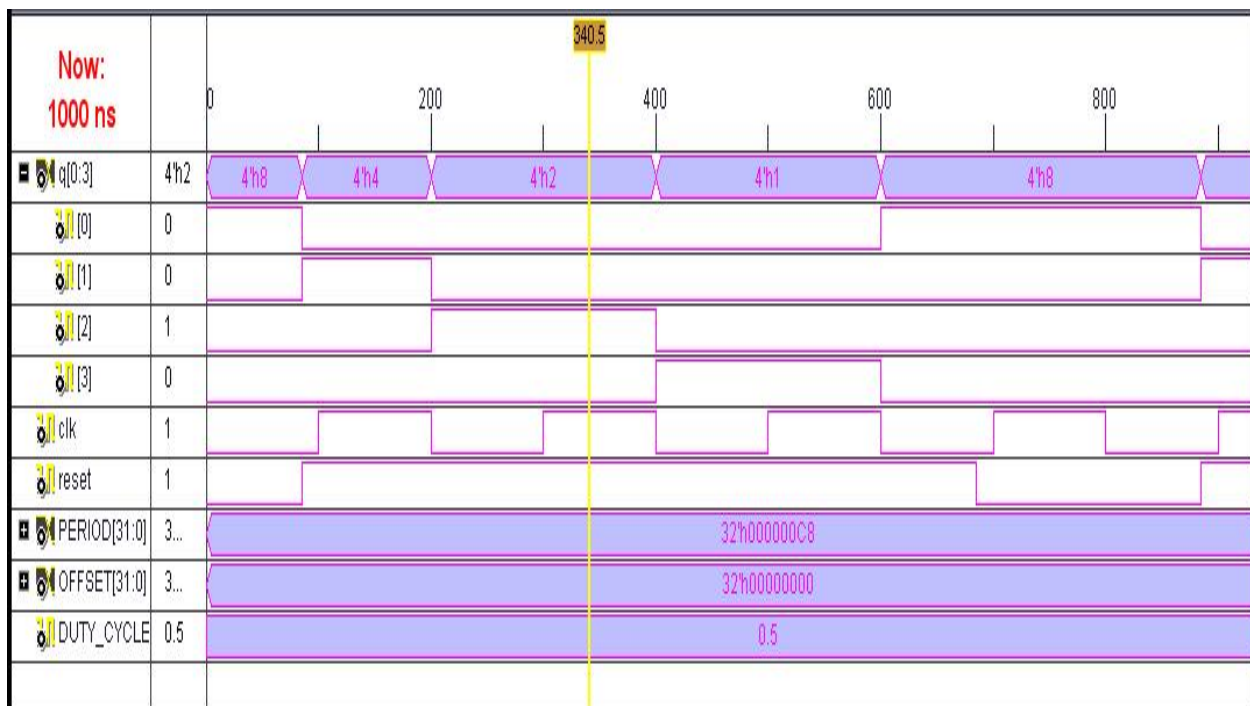 Waveform of ring counter:**Test bench waveform of ring counter:****RESULT:**

Thus the ring counter is designed in Verilog HDL and the output is verified.

Experiment 10: Pseudo Random Binary Sequence Generator


Aim:

Realize the Pseudo random binary sequence generator in Verilog HDL

Theory:

Random numbers for polynomial equations are generated by using the shift register circuit. The random number generator is nothing but the Linear Feedback Shift Register(LFSR). The shift registers are very helpful and versatile modules that facilitate the design of many sequential circuits whose design may otherwise appear very complex. In its simplest form, a shift register consists of a series of flip-flops having identical interconnection between two adjacent flip-flops. Two such registers are shift right registers and the shift left registers. In the shift right register, the bits stored in the flip-flops shift to the right when shift pulse is active. Like that, for a shift left register, the bits stored in the flip-flops shift left when shift pulse is active. In the shift registers, specific patterns are shifted through the register. There are applications where instead of specific patterns, random patterns are more important. Shift registers can also be built to generate such patterns, which are pseudorandom in nature. Called Linear Feedback Shift Registers (LFSR's), these are very useful for encoding and decoding the error control codes. LFSRs used as generators of pseudorandom sequences have proved externally useful in the area of testing of VLSI chips.

Circuit diagram:

 

```

module psrno(y,clk);
  output y;

  input clk;
  wire [1:0]q;
  wire a;

  dff df1(q[0],a,clk);
  dff df2(q[1],q[0],clk);
  dff df3(y,q[1],clk);
  xor x1(a,y,q[1]);
endmodule

```


```


module dff(q,d,clk);
  output q;

  input d,clk;
  reg q=0;
  always @(posedge clk)
  begin
    q = d;
  end
endmodule

```

Waveform of prbs:

 

 Testbench waveform of prbs :**RESULT:**

Thus the pseudo random binary generator is designed in Verilog HDL and the output is verified.

Experiment 11: Design of Accumulator

Aim:

Realize the accumulator in Verilog HDL

Software Required: QuestaSim Simulator

Theory:

An accumulator differs from a counter in the nature of the operands of the add and subtract operation:

- In a counter, the destination and first operand is a signal or variable and the other operand is a constant equal to 1: $A \leq A + 1$.

- In an accumulator, the destination and first operand is a signal or variable, and the second operand is either:

- ◆ A signal or variable: $A \leq A + B$

- ◆ A constant not equal to 1: $A \leq A + \text{Constant}$

An inferred accumulator can be up, down or updown. For an updown accumulator, the accumulated data may differ between the up and down mode:

...

if updown = '1' then $a \leq a + b$;

else

$a \leq a - c$;

Program:

```
module accum (C, CLR, D, Q); input C, CLR;
```

```
input [3:0] D; output [3:0]
```

```
Q; reg [3:0] tmp;
```

```
always @(posedge C or posedge CLR) begin
```

```
    if (CLR)
```


```
        tmp = 4'b0000;
```

```
    else
```


```
        tmp = tmp + D; end
```



```
assign Q = tmp; endmodule
```

Logic Diagram:

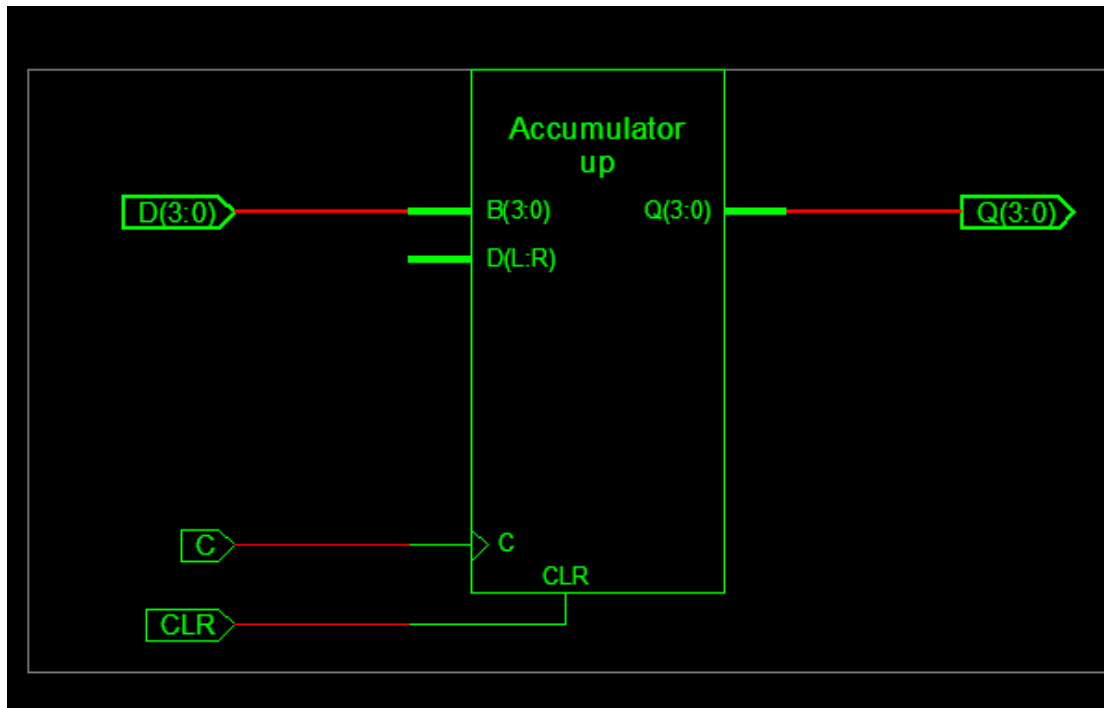


Circuit diagram:

 

  Wave form of accumulator :**Testbench waveform of accumulator:****RESULT:**

Thus the logic circuit for the Accumulator is designed in Verilog HDL and the output is verified.

CYCLE-II

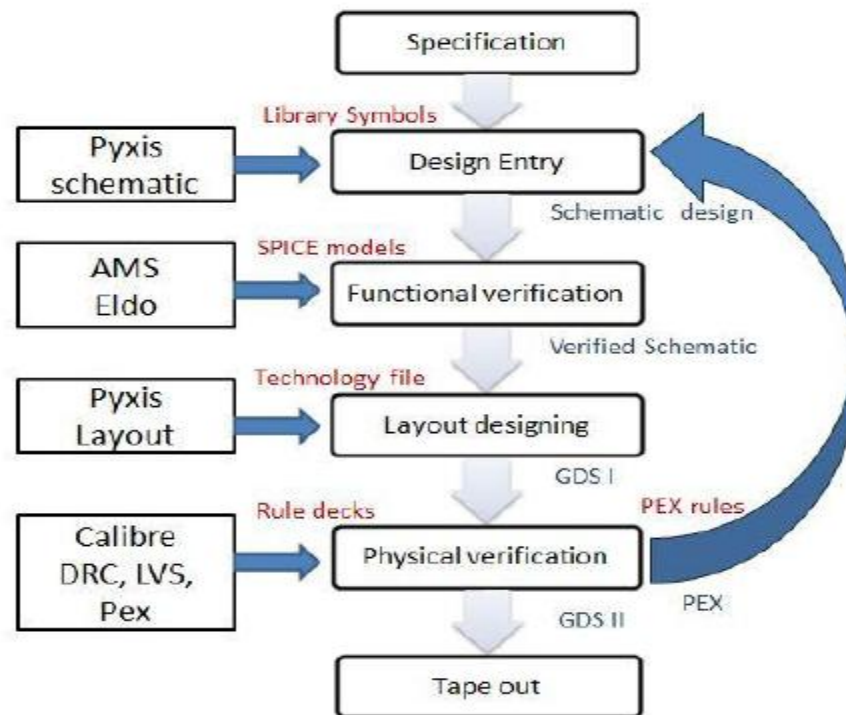

Pyxis Schematic: Pyxis Schematic interacts seamlessly with other solutions in the Pyxis Custom IC Design Platform to create, develop, simulate, verify, optimize and implement even the most challenging full custom analog and mixed-signal IC designs quickly and accurately—the first time. As a designer, you enjoy a consistent look and feel in single environment, whether creating schematics, block diagrams, symbols, or HDL representations. Additionally, Mentor’s foundry partners provide certified design kits for use with Pyxis Custom IC Design Platform solutions.

Pyxis Layout: Pyxis Layout supports an extensive set of editing functions for efficient, accurate polygon editing. This gives the design engineer full control of circuit density and performance, while improving productivity by as much as 5X. Hierarchy and advanced window management allows multiple views of the same cell and provides the capability to edit both views. Additionally, design engineers can create matched analog layouts quickly by editing using a half-cell methodology. **Calibre:** Debugging the error results of physical and circuit verification is costly, both in time and resources. **Calibre RVE** provides fast, flexible, easy-to-use graphical debugging capabilities that minimize your turnaround time and get you to “tapeout-clean” on schedule. Better yet, Calibre RVE easily integrates into all popular layout environments, so no matter which design environment you use, Calibre RVE provides the debugging technology you need for fast, accurate error resolution.

Experiment I: Design and Implementation of an Inverter

AIM: To design and Implementation of an Inverter


TOOLS: Mentor Graphics: Pyxis Schematic, Pyxis Layout, Eldo, Ezwave, Calibre

Theory:

The inverter is universally accepted as the most basic logic gate doing a Boolean operation on a single input variable. Fig.1 depicts the symbol, truth table and a general structure of a CMOS inverter. As shown, the simple structure consists of a combination of a pMOS transistor at the top and a nMOS transistor at the bottom. CMOS is also sometimes referred to as **complementary-symmetry metal-oxide-semiconductor**. The words "complementary-symmetry" refer to the fact that the typical digital design style with CMOS uses complementary and symmetrical pairs of p-type and n-type metal oxide semiconductor field effect transistors (MOSFETs) for logic functions. Two important characteristics of CMOS devices are high noise immunity and low static power consumption. Significant power is only drawn while the transistors in the CMOS device are switching between on and off states. Consequently, CMOS devices do not produce as much waste heat as other forms of logic, for example transistor-transistor logic (TTL) or NMOS logic, which uses all n-channel devices without p-channel devices.


Schematic



Capture:

 


Procedure:

1. Connect the Circuit as shown in the circuit diagram using Pyxis Schematic tool
2. Enter into Simulation mode.
3. Setup the Analysis and library.
4. Setup the required analysis.
5. Probe the required Voltages
6. Run the simulation.
7. Observe the waveforms in EZ wave.
8. Draw the layout using Pysis Layout.
9. Perform Routing using IRoute
10. Perform DRC, LVS, PEX.

 Schematic Symbol:

 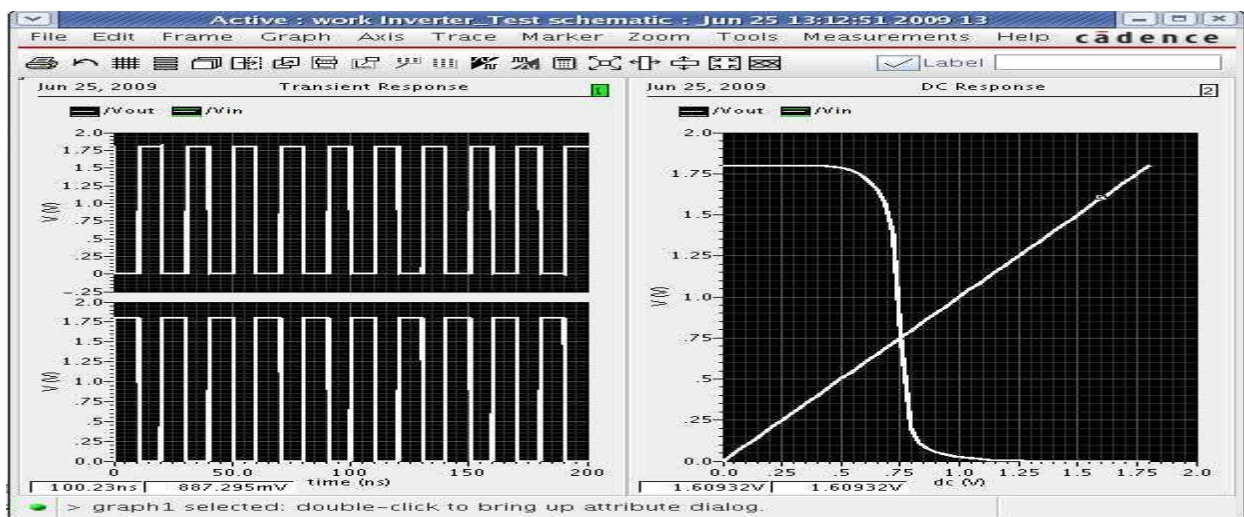Testing the Schematic:**Simulation Output:****Input Vs Output****Transient and DC****Characteristics:**

 
Layout of the Inverter:

Experiment II: NAND GATE

Aim: To create a library and build a schematic of a NAND GATE, to create a symbol for the Inverter, To build an Inverter Test circuit using your Inverter, To set up and run simulations on the Inverter_Test design.


EDA Tool: Mentor Graphics

Schematic :

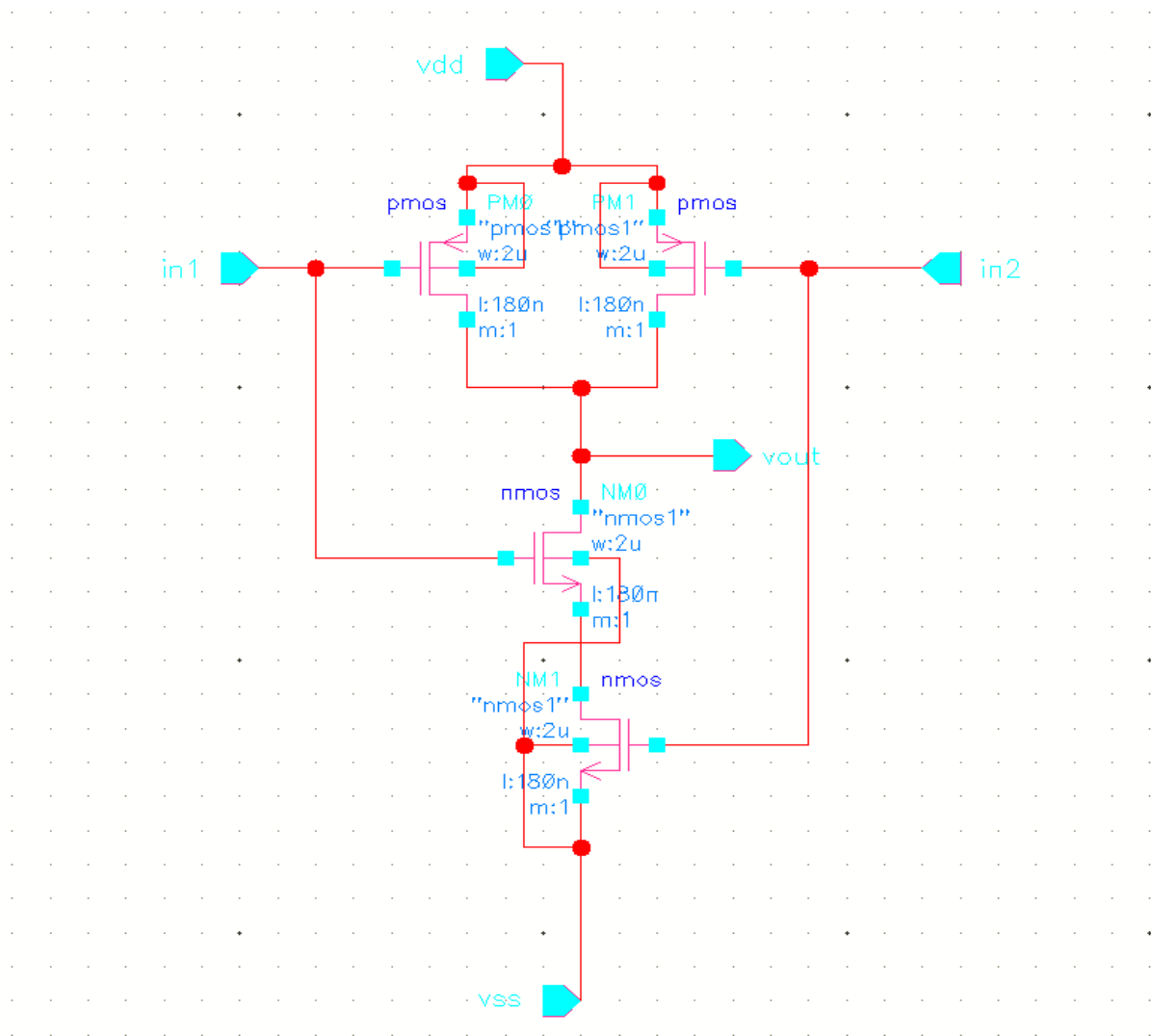


PROCEDURE:


1. Connect the Circuit as shown in the circuit diagram using Pyxis schematic.
2. Create a simulation schematic for simulation.
3. Add necessary nets in outputs to view waveforms.
4. Run the Simulation and observe results in EZwave.
5. Draw the Layout for the circuit using Pyxis Layout.
7. Run the physical verification (DRC, LVS, PEX) using Calibre tool .
8. Run the post layout simulation by adding the .dspf file generated in PEX.
9. Observe the post layout results.

 
Symbol Creation:

Building the NAND Test Design

 

Creating a layout view of NAND gate

 

 
Simulation Output:


EXPERIMENT NO III: NOR Gate

AIM: To design and simulate the CMOS NOR gate



TOOLS: Mentor Graphics: Pyxis Schematic, Pyxis Layout, Eldo, Ezwave, Calibre

CIRCUIT DIAGRAM:

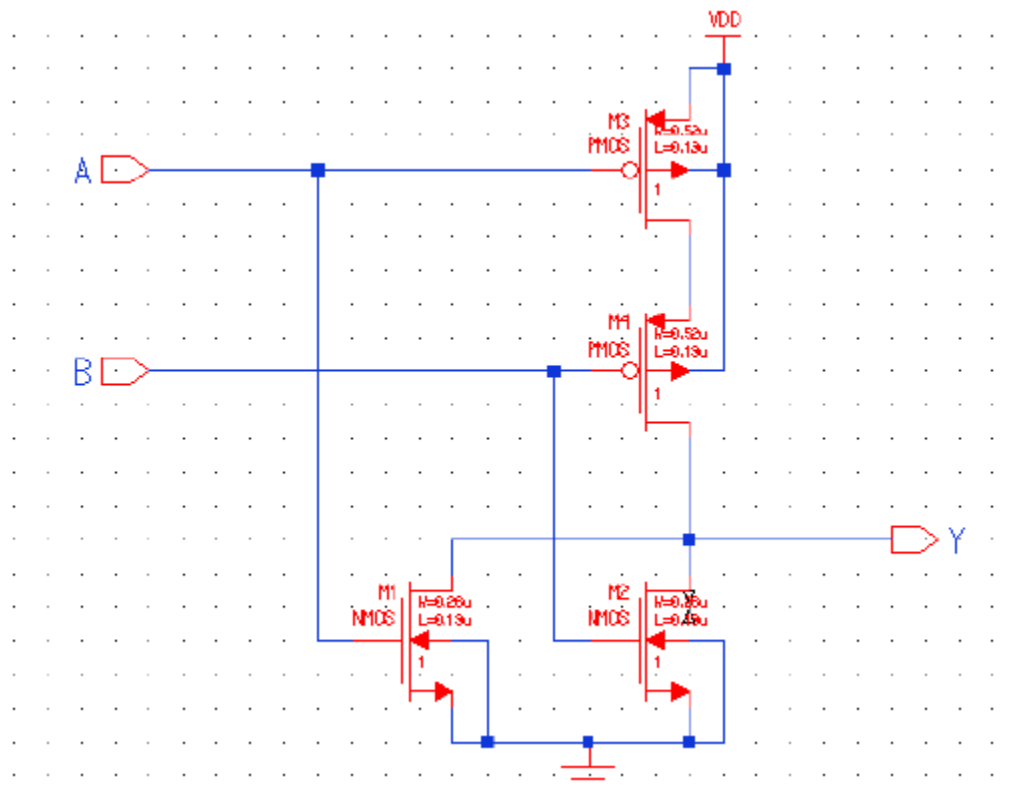

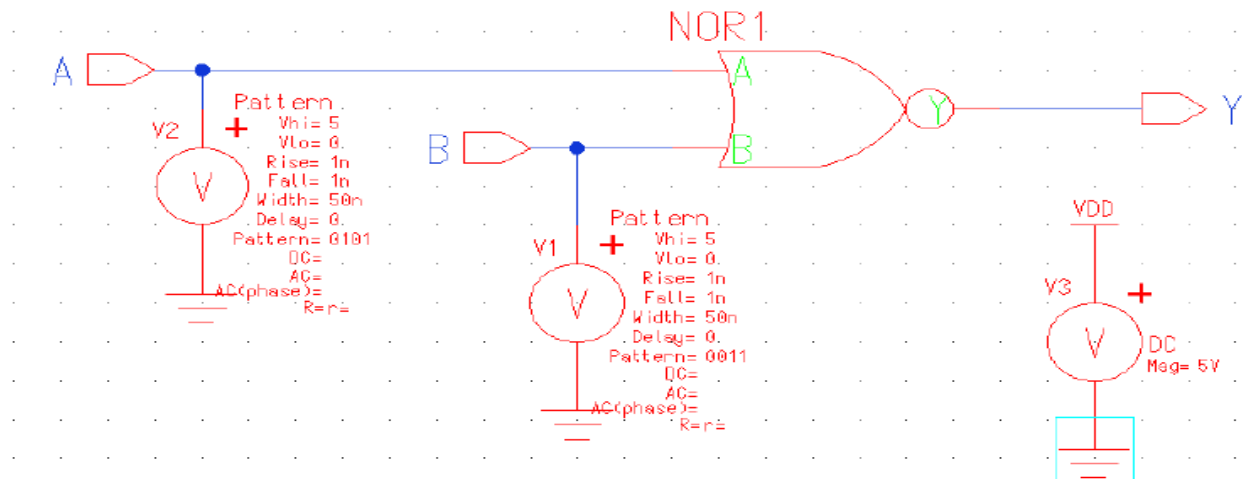SIMULATION CIRCUIT:**PROCEDURE:**


1. Connect the Circuit as shown in the circuit diagram using Pyxis schematic.
2. Create a simulation schematic for simulation.
3. Add necessary nets in outputs to view waveforms.
4. Run the Simulation and observe results in EZwave.
5. Draw the Layout for the circuit using Pyxis Layout.
7. Run the physical verification (DRC, LVS, PEX) using Calibre tool .
8. Run the post layout simulation by adding the .dspf file generated in PEX.
9. Observe the post layout results.

  Simulation Output:**Layout:**

EXPERIMENT NO IV: XOR GATE


Aim: To create a library and build a schematic of an XOR gate, to create a symbol for the XOR, To build an Inverter Test circuit using your XOR, To set up and run simulations on the XOR_Test design.

EDA Tools: Pyxis Schematic, Pyxis Layout, Eldo, Ezwave, Calibre

 
**PROCEDURE:**

1. Connect the Circuit as shown in the circuit diagram using Pyxis schematic.
2. Create a simulation schematic for simulation.
3. Add necessary nets in outputs to view waveforms.
4. Run the Simulation and observe results in EZwave.
5. Draw the Layout for the circuit using Pyxis Layout.
7. Run the physical verification (DRC, LVS, PEX) using Calibre tool .
8. Run the post layout simulation by adding the .dspf file generated in PEX.
9. Observe the post layout results.

Symbol Creation

 


Building the XOR Gate Test Design

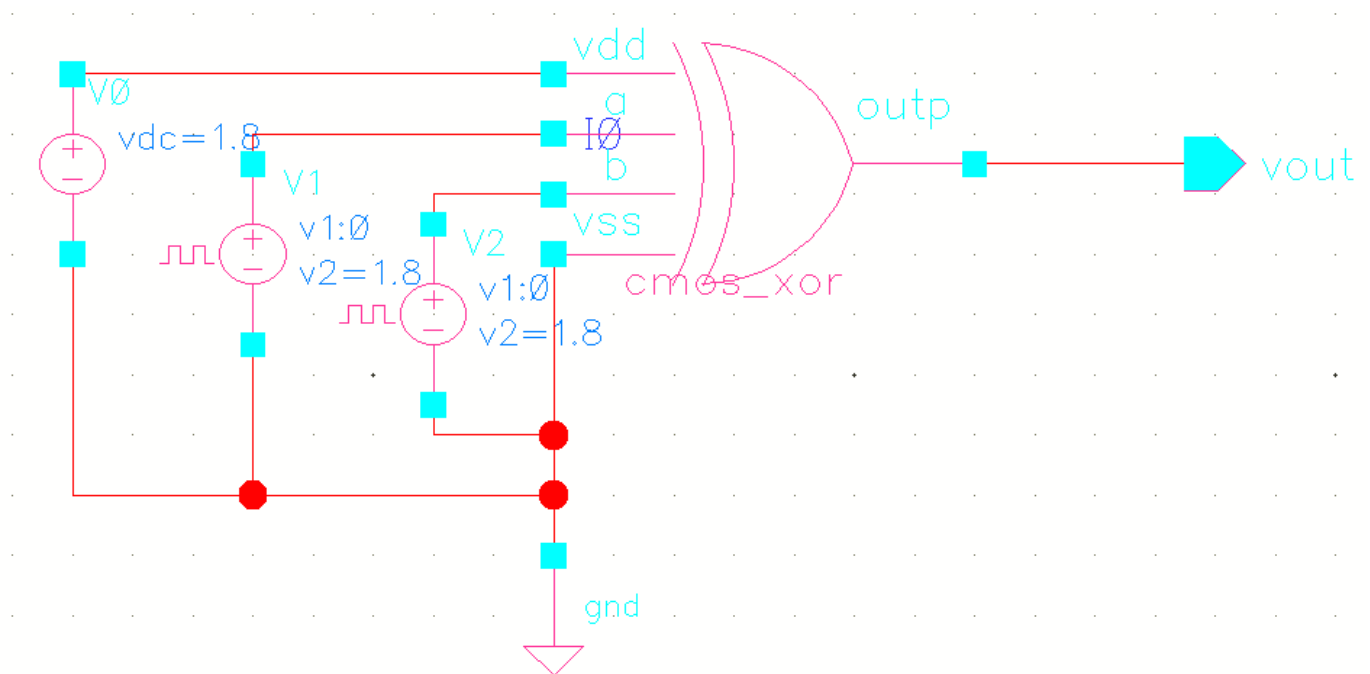


PROCEDURE:

1. Connect the Circuit as shown in the circuit diagram using Pyxis schematic.
2. Create a simulation schematic for simulation.
3. Add necessary nets in outputs to view waveforms.
4. Run the Simulation and observe results in EZwave.
5. Draw the Layout for the circuit using Pyxis Layout.
7. Run the physical verification (DRC, LVS, PEX) using Calibre tool .
8. Run the post layout simulation by adding the .dspf file generated in PEX.
9. Observe the post layout results

 Simulation output:


Layout:

 



EXPERIMENT NO V: CMOS 1-Bit Full Adder


AIM: To design and simulate the CMOS 1 Bit Full Adder.

TOOLS: Pyxis Schematic, Pyxis Layout, Eldo, Ezwave, Calibre.

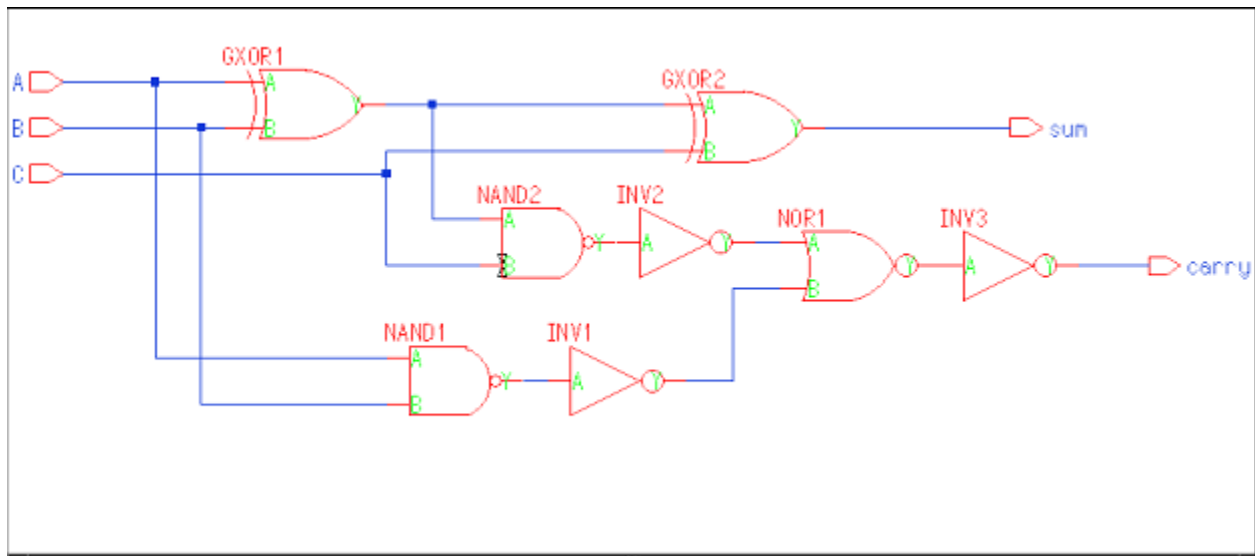Schematic Diagram:**PROCEDURE:**

1. Connect the Circuit as shown in the circuit diagram using Pyxis schematic.
2. Create a simulation schematic for simulation.
3. Add necessary nets in outputs to view waveforms.
4. Run the Simulation and observe results in EZwave.
5. Draw the Layout for the circuit using Pyxis Layout.
7. Run the physical verification (DRC, LVS, PEX) using Calibre tool .
8. Run the post layout simulation by adding the .dspf file generated in PEX.
9. Observe the post layout results

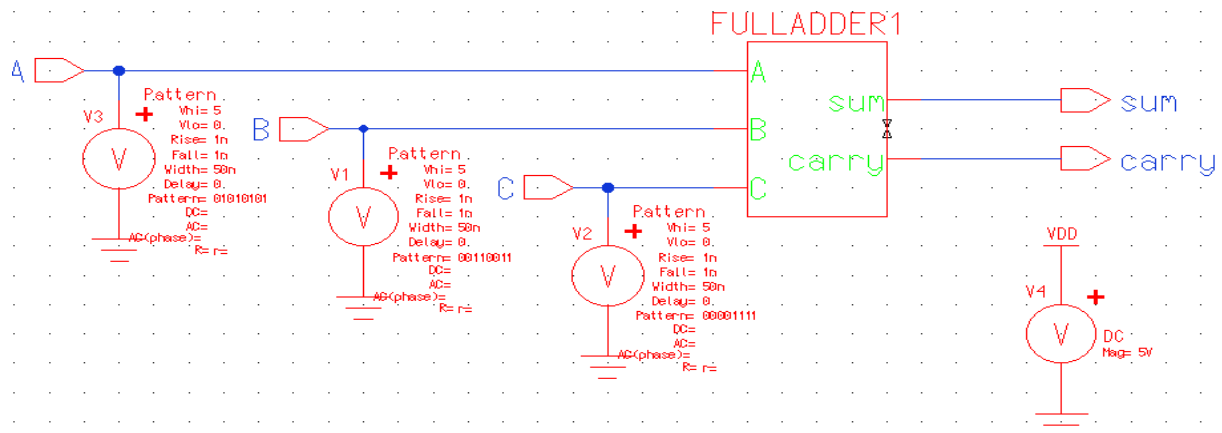 Testing the Full Adder:**Layout:**

 
Simulation Output:


EXPERIMENT NO VI: Common Source Amplifier

AIM: To design and simulate the Common Source Amplifier.



TOOLS: Pyxis Schematic, Pyxis Layout, Eldo, Ezwave, Calibre.

Circuit Diagram:

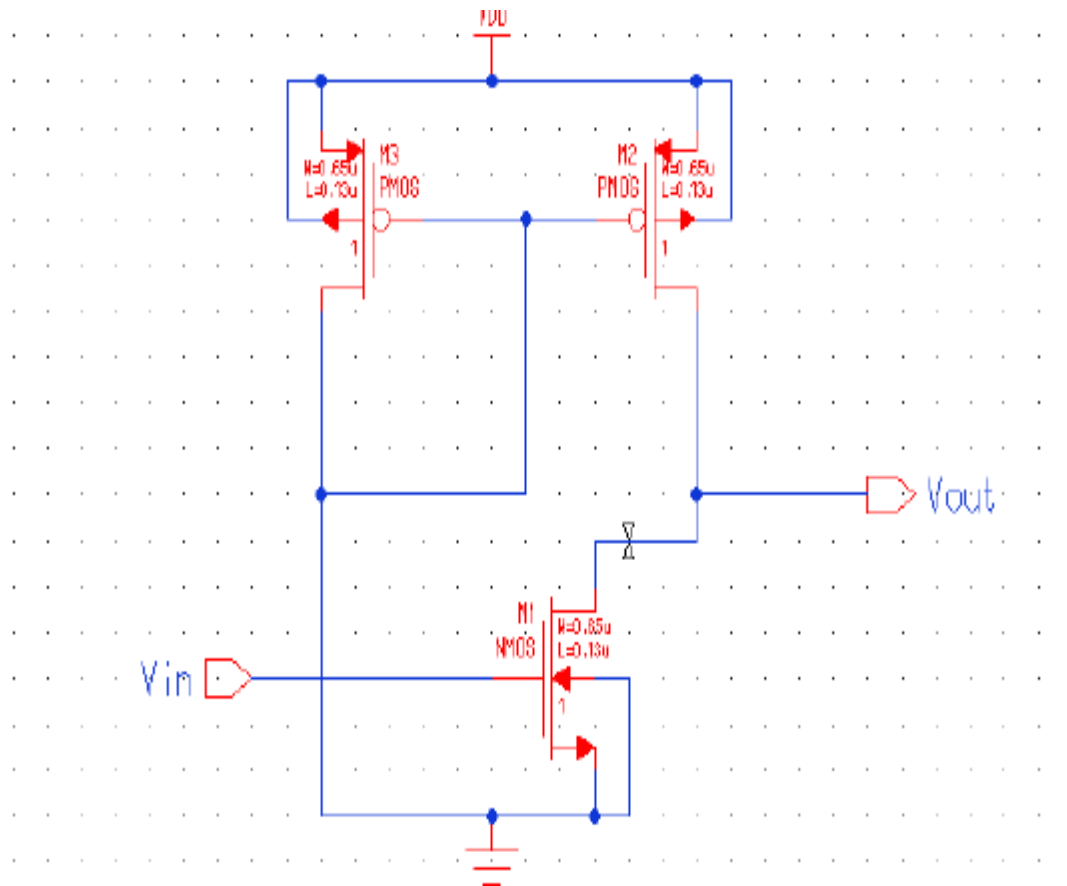


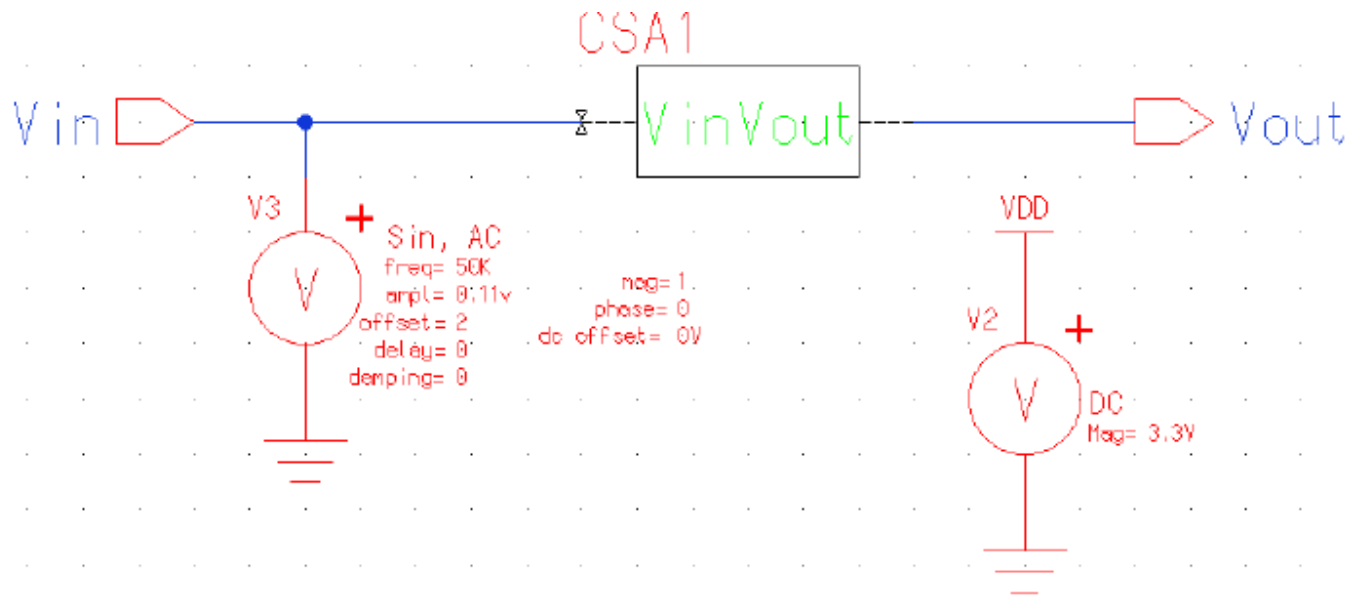Simulation Circuit:**PROCEDURE:**

1. Connect the Circuit as shown in the circuit diagram using Pyxis schematic.
2. Create a simulation schematic for simulation.
3. Add necessary nets in outputs to view waveforms.
4. Run the Simulation and observe results in EZwave.
5. Draw the Layout for the circuit using Pyxis Layout.
7. Run the physical verification (DRC, LVS, PEX) using Calibre tool .
8. Run the post layout simulation by adding the .dspf file generated in PEX.
9. Observe the post layout results.

  AC Analysis:**Transient Analysis result:**

Layout:

 



EXPERIMENT NO VII: Differential Amplifier

AIM: To design and simulate the Differential Amplifier.


TOOLS: Pyxis Schematic, Pyxis Layout, Eldo, Ezwave, Calibre.

CIRCUIT DIAGRAM:

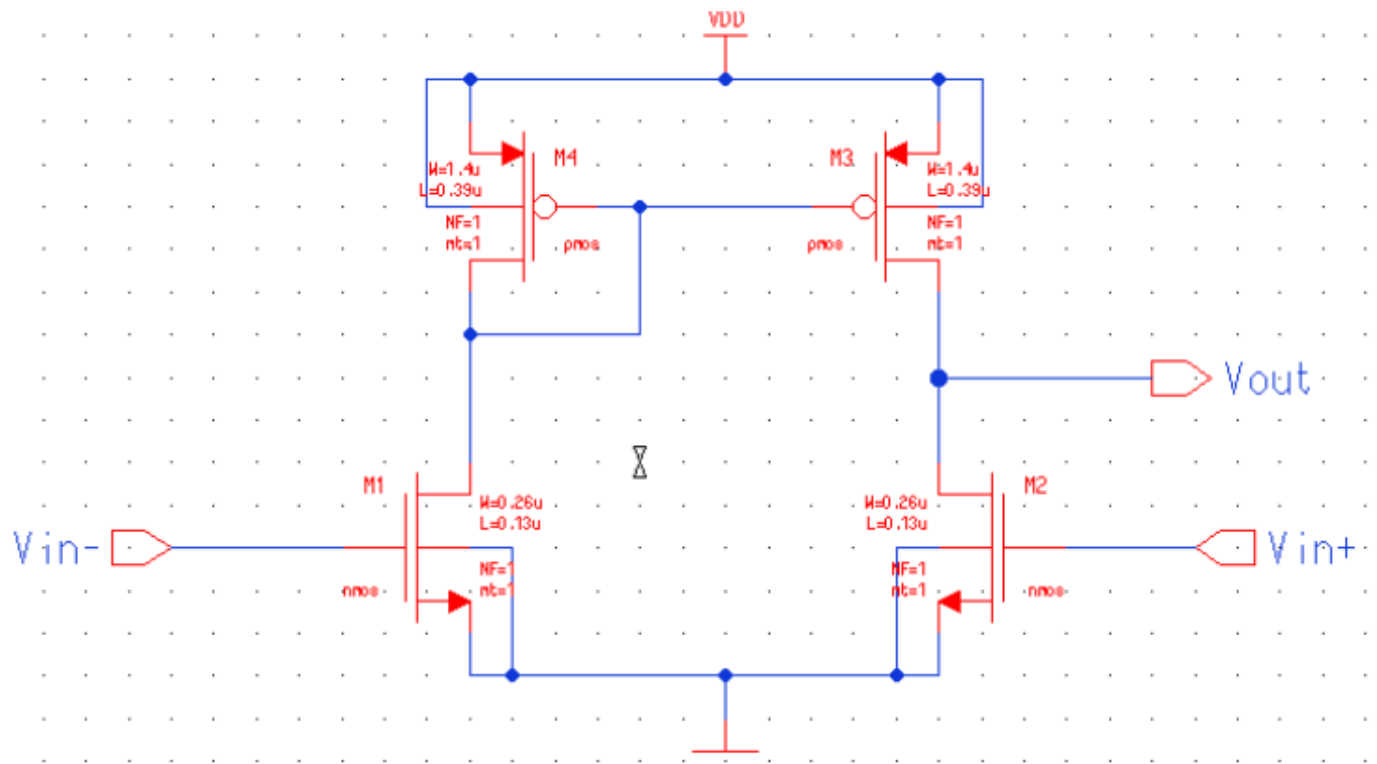

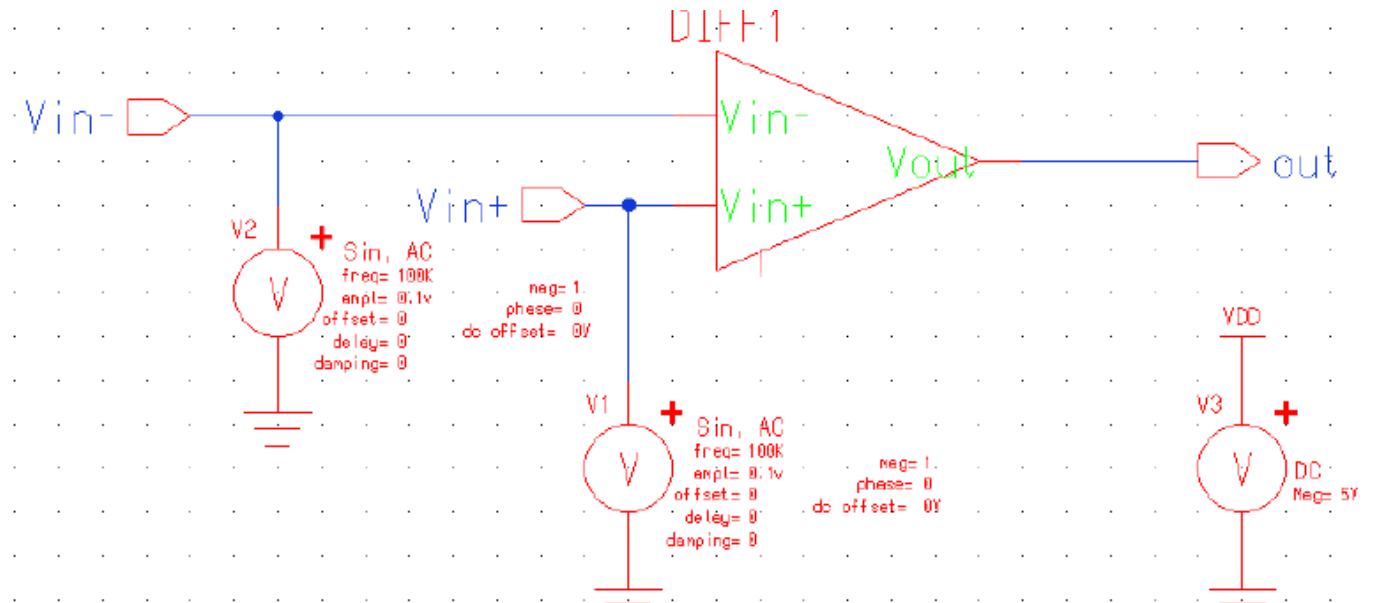Simulation Circuit:**PROCEDURE:**

1. Connect the Circuit as shown in the circuit diagram using Pyxis schematic.
2. Create a simulation schematic for simulation.
3. Add necessary nets in outputs to view waveforms.
4. Run the Simulation and observe results in EZwave.
5. Draw the Layout for the circuit using Pyxis Layout.
7. Run the physical verification (DRC, LVS, PEX) using Calibre tool .
8. Run the post layout simulation by adding the .dspf file generated in PEX.
9. Observe the post layout results.

 RESULTS:**AC Analysis result:**

Transient Analysis**Result:**