

**ANALOG CIRCUITS  
LABORATORY MANUAL  
(R22A0481)  
(II YEAR–I SEM)  
(2024-25)**



**Designed BY**

**K. VIJAYA BHARATHI  
ASSISTANT PROFESSOR**

**Department of Electronics and Communication Engineering**

**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY**

**(Autonomous Institution –UGC, Govt. of India)  
Recognized under 2(f) and 12 (B) of UGC Act 1956**

**Affiliated to JNTUH, Hyderabad, Approved by AICTE - Accredited by NBA & NAAC – ‘A’ Grade -  
ISO 9001:2015 Certified) Maisammaguda, Dhulapally (Post Via. Kompally), Secunderabad–  
500100, Telangana, India**





## DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING VISION

**To evolve into a center of excellence in Engineering Technology through creative and innovative practices in teaching-learning, promoting academic achievement & research excellence to produce internationally accepted competitive and world class professionals.**

## MISSION

**To provide high quality academic programmes, training activities, research facilities and opportunities supported by continuous industry institute interaction aimed at employability, entrepreneurship, leadership and research aptitude among students.**

## QUALITY POLICY

### PROGRAMME EDUCATIONAL OBJECTIVES

- ❖ **Impart up-to-date knowledge to the students in Electronics & Communication area to make them quality engineers.**
- ❖ **Make the students experience the applications on quality equipment and tools.**
- ❖ **Provide systems, resources and training opportunities to achieve continuous improvement.**
- ❖ **Maintain global standards in education, training and services.**

**PEO1: PROFESSIONALISM & CITIZENSHIP**

To create and sustain a community of learning in which students acquire knowledge and learn to apply it professionally with due consideration for ethical, ecological and economic issues.

**PEO2: TECHNICAL ACCOMPLISHMENTS**

To provide knowledge based services to satisfy the needs of society and the industry by providing hands on experience in various technologies in core field.

**PEO3: INVENTION, INNOVATION AND CREATIVITY**

To make the students to design, experiment, analyze, interpret in the core field with the help of other multi disciplinary concepts wherever applicable.

**PEO4: PROFESSIONAL DEVELOPMENT**

To educate the students to disseminate research findings with good soft skills and become a successful entrepreneur.

**PEO5: HUMAN RESOURCE DEVELOPMENT**

To graduate the students in building national capabilities in technology, education and research.

**PROGRAM OUTCOMES (POs)****Engineering Graduates should possess the following**

1. **Engineering knowledge:** Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
2. **Problem analysis:** Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
3. **Design / development of solutions:** Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
4. **Conduct investigations of complex problems:** Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
5. **Modern tool usage:** Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.
6. **The engineer and society:** Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
7. **Environment and sustainability:** Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
8. **Ethics:** Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
9. **Individual and team work:** Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.
10. **Communication:** Communicate effectively on complex engineering activities with the

engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.

11. **Project management and finance:** Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multi-disciplinary environments.

**CODE OF CONDUCT FOR THE LABORATORIES**


1. All students must observe the Dress Code while in the laboratory.
2. Sandals or open-toed shoes are NOT allowed.
3. Foods, drinks and smoking are NOT allowed.
4. All bags must be left at the indicated place.
5. The lab timetable must be strictly followed.
6. Be punctual for your laboratory session.
7. Program must be executed within the given time.
8. Noise must be kept to a minimum.
9. Workspace must be kept clean and tidy at all time.
10. Handle the systems and interfacing kits with care.
11. All students are liable for any damage to the accessories due to their own negligence.
12. All interfacing kits connecting cables must be RETURNED if you taken from the lab supervisor.
13. Students are strictly PROHIBITED from taking out any items from the laboratory.
14. Students are NOT allowed to work alone in the laboratory without the Lab Supervisor
15. USB Ports have been disabled if you want to use USB drive consult lab supervisor.
16. Report immediately to the Lab Supervisor if any malfunction of the accessories, is there.

**Before leaving the lab**

1. Place the chairs properly.
2. Turn off the system properly
3. Turn off the monitor.
4. Please check the laboratory notice board regularly for updates.



# CERTIFICATE

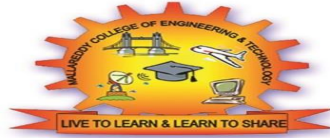

**MALLA REDDY COLLEGE OF ENGINEERING AND TECHNOLOGY**  
(Autonomous Institution – UGC, Govt. of India)  
(Affiliated to JNTUH, Hyderabad, Approved by AICTE- Accredited by NBA & NAAC ‘A’  
Grade –  
ISO 9001:2015 Certified)

## Certificate

*Department of **Electronics and Communication Engineering** certified that in the  
bonafide Record of the work done by Mr./Miss \_\_\_\_\_  
Reg.No \_\_\_\_\_ of B.Tech **ECE** \_\_\_\_\_ year \_\_\_\_\_ semester  
for the Academic year 20\_\_\_\_ to 20\_\_\_\_ in \_\_\_\_\_ Laboratory.*

*Date:*

*Staff In charge*

*HOD*

*Internal Examiner*

*External Examiner*



**(R22A0481) ANALOG CIRCUITS LAB****COURSE OBJECTIVES:**

- 1) To design Multistage, Power amplifiers and multivibrators according to given specifications.
- 2) To analyze various amplifiers such as Common Emitter, Common Source, Cascade and Cascode amplifiers.
- 3) To build circuit construction skills using circuit simulation software tool.
- 4) To simulate different amplifier circuits.
- 5) To design Feedback amplifiers

**LIST OF EXPERIMENTS**

1. INPUT & OUTPUT CHARACTERISTICS OF TRANSISTOR CB CONFIGURATION
2. INPUT & OUTPUT CHARACTERISTICS OF TRANSISTOR CE CONFIGURATION
3. CALCULATION OF  $h$ -PARAMETERS of CC CONFIGURATION FROM INPUT & OUTPUT CHARACTERISTICS
4. CALCULATION OF  $h$ -PARAMETERS of CB CONFIGURATION FROM INPUT & OUTPUT CHARACTERISTICS
5. CALCULATION OF  $h$ -PARAMETERS of CE CONFIGURATION FROM INPUT & OUTPUT CHARACTERISTICS
6. FREQUENCY RESPONSE OF CE AMPLIFIER
7. FREQUENCY RESPONSE OF CS AMPLIFIER
8. FREQUENCY RESPONSE OF TWO STAGE RC COUPLED AMPLIFIER
9. VOLTAGE SERIES FEEDBACK AMPLIFIERS
10. CURRENT SHUNT FEEDBACK AMPLIFIERS
11. COLPITTS OSCILLATOR
12. HARTLEY OSCILLATOR

**COURSE OUTCOMES :**

- 1) Design Multistage, Power amplifiers and multivibrators according to given specifications.
- 2) Analyze various amplifiers such as Common Emitter, Common Source, Cascade and Cascode amplifiers.
- 3) Build circuit construction skills using circuit simulation software tool.
- 4) Simulate different amplifier circuits.
- 5) Design Feedback amplifiers

**LIST OF EXPERIMENTS**

1. **INPUT & OUTPUT CHARACTERISTICS OF TRANSISTOR CB CONFIGURATION**
2. **INPUT & OUTPUT CHARACTERISTICS OF TRANSISTOR CE CONFIGURATION**
3. **CALCULATION OF  $h$ -PARAMETERS of CC CONFIGURATION FROM INPUT & OUTPUT CHARACTERISTICS**
4. **CALCULATION OF  $h$ -PARAMETERS of CB CONFIGURATION FROM INPUT & OUTPUT CHARACTERISTICS**
5. **CALCULATION OF  $h$ -PARAMETERS of CE CONFIGURATION FROM INPUT & OUTPUT CHARACTERISTICS**
6. **FREQUENCY RESPONSE OF CE AMPLIFIER**
7. **FREQUENCY RESPONSE OF CS AMPLIFIER**
8. **FREQUENCY RESPONSE OF TWO STAGE RC COUPLED AMPLIFIER**
9. **VOLTAGE SERIES FEEDBACK AMPLIFIERS**
10. **CURRENT SHUNT FEEDBACK AMPLIFIERS**
11. **COLPITTS OSCILLATOR**
12. **HARTLEY OSCILLATOR**



## EXPERIMENT 1

### 1. COMMON BASE INPUT & OUTPUT CHARACTERISTICS

**AIM:** 1. To observe and draw the input and output characteristics of a transistor connected in Common Base configuration.

2. To find  $\alpha$  of the given transistor and also its input and output Resistances.

#### APPARATUS:

Transistor, BC107	-1No.
Regulated power supply (0-30V)	-1No.
Voltmeter (0-20V)	- 2No.
Ammeters (0-10mA)	- 2No.
Resistor, 1K $\Omega$	- 2No
Bread board	
Connecting wires	

#### THEORY:

A transistor is a three terminal active device. The terminals are emitter, base, collector. In CB configuration, the base is common to both input (emitter) and output (collector). For normal operation, the E-B junction is forward biased and C-B junction is reverse biased. In CB configuration,  $I_E$  is +ve,  $I_C$  is -ve and  $I_B$  is -ve.

$$V_{EB} = F_1 (V_{CB}, I_E) \text{ and}$$

$$I_C = F_2 (V_{EB}, I_B)$$

With an increasing the reverse collector voltage, the space-charge width at the output junction increases and the effective base width 'W' decreases. This phenomenon is known as "Early effect". Then, there will be less chance for recombination within the base region. With increase of charge gradient within the base region, the current of minority carriers injected across the emitter junction increases.


The current amplification factor of CB configuration is given by,

$$\alpha = \Delta I_C / \Delta I_E$$

Input Resistance,  $r_i = \Delta V_{BE} / \Delta I_E$  at Constant  $V_{CB}$

Output Resistance,  $r_o = \Delta V_{CB} / \Delta I_C$  at Constant  $I_E$


### CIRCUIT DIAGRAM:

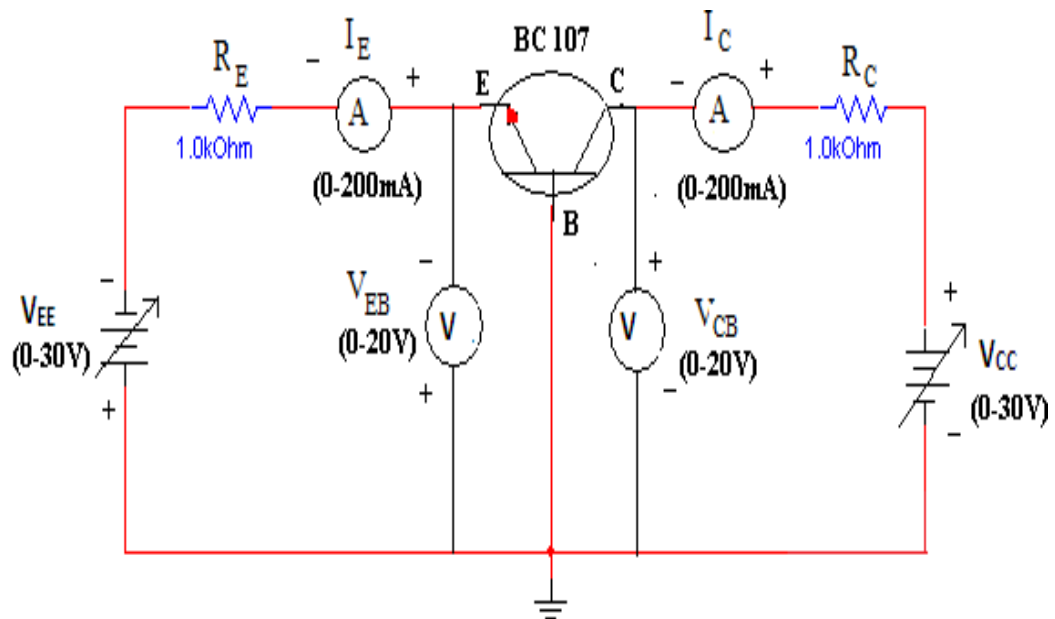


### MODEL GRAPHS:

#### A) INPUT CHARACTERISTICS

Input Characteristics

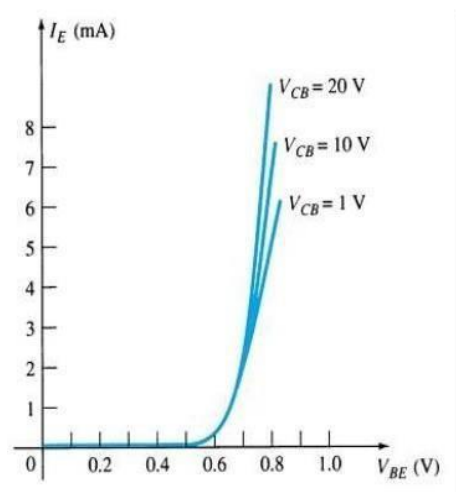

## B) OUTPUT CHARACTERISTICS

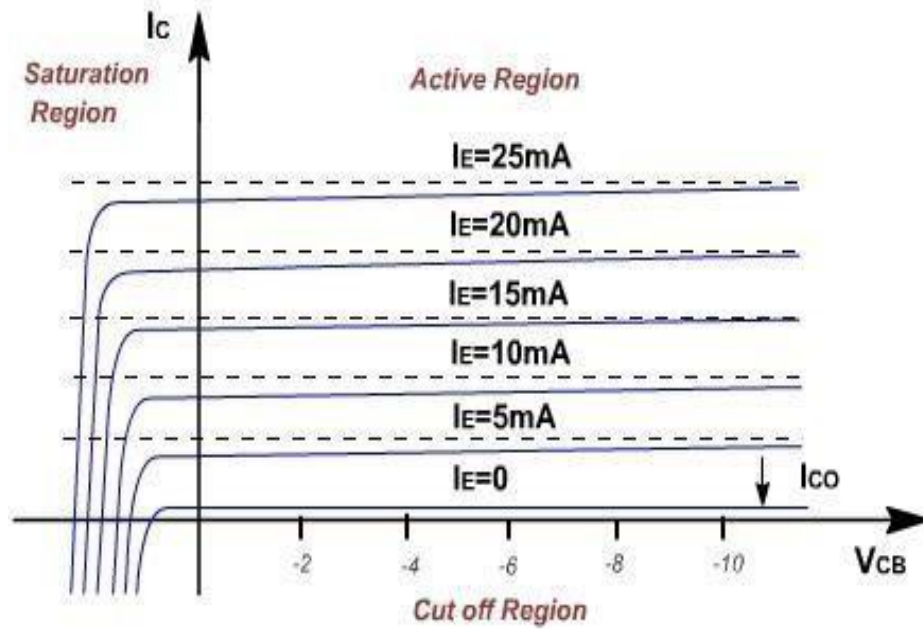

### OBSERVATIONS:

#### A) INPUT CHARACTERISTICS:

$V_{EE}(V)$	$V_{CB}=1V$		$V_{CB}= 2V$		$V_{CB}= 4V$	
	$V_{EB}(V)$	$I_E(mA)$	$V_{EB}(V)$	$I_E(mA)$	$V_{EB}(V)$	$I_E(mA)$





**B) OUTPUT CHARACTERISTICS:**


1. Connections are made as per the circuit diagram.
2. For plotting the output characteristics, the input  $I_E$  is kept constant at 0.5mA and for different values of  $V_{CC}$ , note down the values of  $I_C$  and  $V_{CB}$ .
3. Repeat the above step for the values of  $I_E$  at 1mA, 5mA and all the readings are tabulated.
4. A graph is drawn between  $V_{CB}$  and  $I_C$  for constant  $I_E$


**PRECAUTIONS:**


1. The supply voltages should not exceed the rating of the transistor.
2. Meters should be connected properly according to their polarities.
3. While performing the experiment do not exceed the ratings of the transistor. This may lead to damage the transistor.
4. Connect voltmeter and ammeter in correct polarities as shown in the circuit diagram.
5. Do not switch ON the power supply unless you have checked the circuit connections as per the circuit diagram.
6. Make sure while selecting the emitter, base and collector terminals of the transistor.


**RESULT:****VIVA QUESTIONS:**

 1. What is the range of  $\alpha$  for the transistor?
2. Draw the input and output characteristics of the transistor in CB configuration?
3. Identify various regions in output characteristics?
4. What is the relation between  $\alpha$  and  $\beta$ ?
5. What are the applications of CB configuration?
6. What are the input and output impedances of CB configuration?
7. Define  $\alpha$  (alpha)?
8. What is early effect?
9. Draw Circuit diagram of CB configuration for PNP transistor?



 

 

 



## EXPERIMENT 1

### 1. INPUT & OUTPUT CHARACTERISTICS OF TRANSISTOR CE CONFIGURATION

#### AIM:

1. To draw the input and output characteristics of transistor connected in CE configuration
2. To find  $\beta$  of the given transistor and also its input and output Resistances

#### APPARATUS:

- |                                   |        |
|-----------------------------------|--------|
| 1. Transistor, BC107              | -1No.  |
| 2. Regulated power supply (0-30V) | -1No.  |
| 3. Voltmeter (0-20V)              | - 2No. |
| 4. Ammeters (0-20mA)              | -1No.  |
| 5. Ammeters (0-200 $\mu$ A)       | -1No.  |
| 6. Resistor, 100 $\Omega$         | -1No   |
| 7. Resistor, 1K $\Omega$          | -1No.  |
| 8. Bread board                    |        |
| 9. Connecting wires               |        |

#### THEORY:

In common emitter configuration, input voltage is applied between base and emitter terminals and output is taken across the collector and emitter terminals. Therefore the emitter terminal is common to both input and output. The input characteristics resemble that of a forward biased diode curve. This is expected since the Base-Emitter junction of the transistor is forward biased. As compared to CB arrangement  $I_B$  increases less rapidly with  $V_{BE}$ . Therefore input resistance of CE circuit is higher than that of CB circuit. The output characteristics are drawn between  $I_C$  and  $V_{CE}$  at constant  $I_B$  the collector current varies with  $V_{CE}$  up to few volts only. After this the collector current becomes almost constant, and independent of  $V_{CE}$ . The value of  $V_{CE}$  up to which the collector current changes with  $V_{CE}$  is known as Knee voltage. The transistor always operated in the region above Knee voltage,  $I_C$  is always constant and is




approximately equal to  $I_B$ . The current amplification factor of CE configuration is given by

$$\beta = \Delta I_C / \Delta I_B$$

$$\text{Input Resistance, } r_i = \Delta V_{BE} / \Delta I_B (\mu A) \text{ at Constant } V_{CE}$$


$$\text{Output Resistance, } r_o = \Delta V_{CE} / \Delta I_C \text{ at Constant } I_B (\mu A)$$

**CIRCUIT DIAGRAM:**

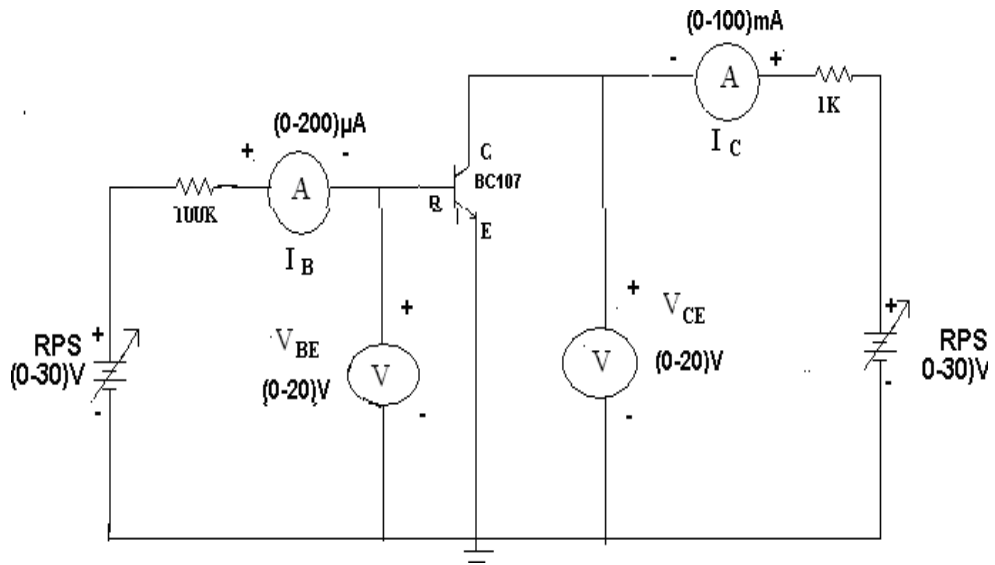


**MODEL GRAPHS:**

**A) INPUT CHARACTERISTICS:**

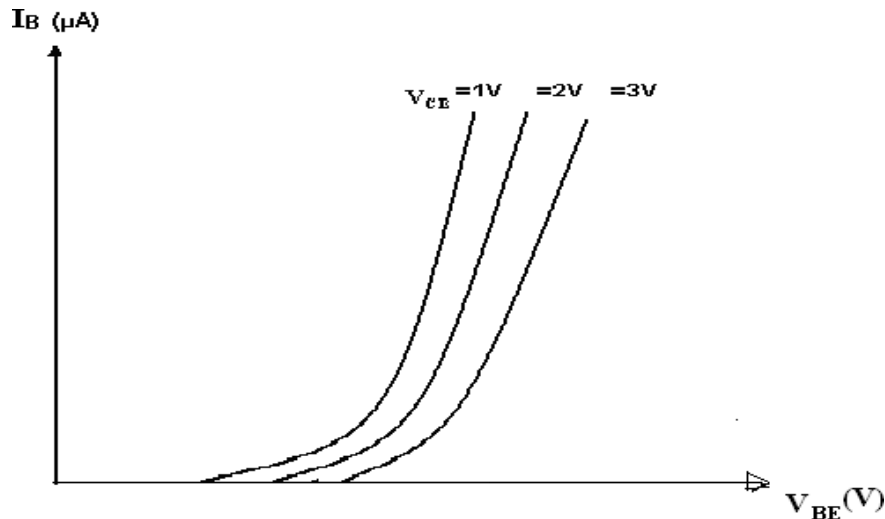

**A) OUTPUT CHARACTERISTICS:**

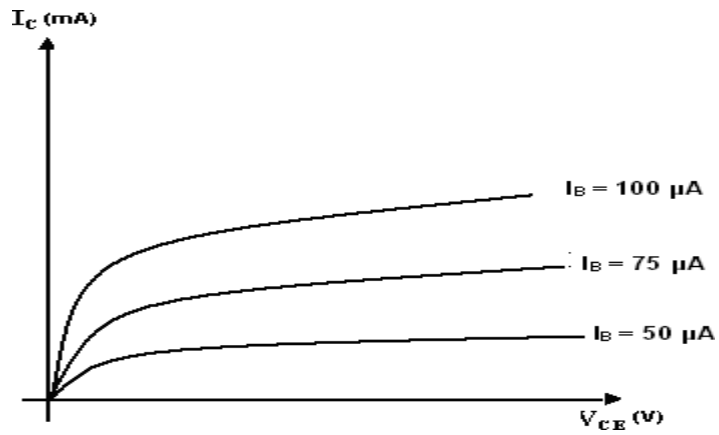

**OBSERVATIONS:**

**A) INPUT CHARACTERISTICS:**

$V_{BB}$	$V_{CE} = 1V$		$V_{CE} = 2V$		$V_{CE} = 4V$	
	$V_{BE}(V)$	$I_B(\mu A)$	$V_{BE}(V)$	$I_B(\mu A)$	$V_{BE}(V)$	$I_B(\mu A)$

**B) OUTPUT CHARACTERISTICS:**

S.NO	$I_B = 50 \mu A$		$I_B = 75 \mu A$		$I_B = 100 \mu A$	
	$V_{CE}(V)$	$I_C(mA)$	$V_{CE}(V)$	$I_C(mA)$	$V_{CE}(V)$	$I_C(mA)$

**PROCEDURE:****A) INPUT CHARACTERISTICS:**

1. Connect the circuit as per the circuit diagram.
2. For plotting the input characteristics the output voltage  $V_{CE}$  is kept constant at 1V and for different values of  $V_{BB}$ , note down the values of  $I_B$  and  $V_{BE}$
3. Repeat the above step by keeping  $V_{CE}$  at 2V and 4V and tabulate all the readings.
4. plot the graph between  $V_{BE}$  and  $I_B$  for constant  $V_{CE}$

**B) OUTPUT CHARACTERISTICS:**


1. Connect the circuit as per the circuit diagram
2. for plotting the output characteristics the input current  $I_B$  is kept constant at  $50\mu A$  and for different values of  $V_{CC}$  note down the values of  $I_C$  and  $V_{CE}$
3. Repeat the above step by keeping  $I_B$  at  $75 \mu A$  and  $100 \mu A$  and tabulate the all the readings
4. plot the graph between  $V_{CE}$  and  $I_C$  for constant  $I_B$


**PRECAUTIONS:**


1. The supply voltage should not exceed the rating of the transistor
2. Meters should be connected properly according to their polarities
3. While performing the experiment do not exceed the ratings of the transistor. This may lead to damage the transistor.
4. Connect voltmeter and ammeter in correct polarities as shown in the circuit diagram.
5. Do not switch ON the power supply unless you have checked the circuit connections as per the circuit diagram.
6. Make sure while selecting the emitter, base and collector terminals of the transistor.


**RESULT:****VIVA QUESTIONS:**

 1. What is the range of  $\beta$  for the transistor?
2. What are the input and output impedances of CE configuration?
3. Identify various regions in the output characteristics?
4. What is the relation between  $\alpha$  and  $\beta$ ?
5. Define current gain in CE configuration?
6. Why CE configuration is preferred for amplification?
7. What is the phase relation between input and output?
8. Draw diagram of CE configuration for PNP transistor?
9. What is the power gain of CE configuration?
10. What are the applications of CE configuration?



 

 

 





## EXPERIMENT 3

### **h-PARAMETERS OF CC CONFIGURATION**

**AIM:** To draw the input and output characteristics of transistor connected in CC (Common Collector) or Emitter follower configuration.


**APPARATUS:**

1. Transistor (SL100 or BC107)
2. R.P.S (0-30V) 2Nos
3. Voltmeters (0-20V) 2Nos
4. Ammeters (0-200 $\mu$ A),(0-200mA)
5. Resistors 100Kohm
6. Bread board and connecting wires
- 7.

**THEORY:**

A transistor is a three terminal device. Bipolar Junction Transistor (BJT) is a three terminal (emitter, base, collector) semiconductor device. There are two types of BJTs, namely NPN and PNP. It consists of two PN junctions, namely emitter junction and collector junction. The terminals are emitter, base, collector. In emitter follower configuration, input voltage is applied between base and ground terminals and output is taken across the emitter and collector terminals. The input characteristics resemble that of a forward biased diode curve. This is expected since the Base-Emitter junction of the transistor is forward biased. The output characteristics are drawn between  $I_E$  and  $V_{CE}$  at constant  $I_B$ . The emitter current varies with  $V_{CE}$  upto few volts only. After this the emitter current becomes almost constant, and independent of  $V_{CE}$ . The value of  $V_{CE}$  up to which the collector current changes with  $V_{CE}$  is known as Knee voltage. The transistor always operated in the region above Knee voltage,  $I_E$  is always constant and is approximately equal to  $I_B$ .

### Circuit Diagram:

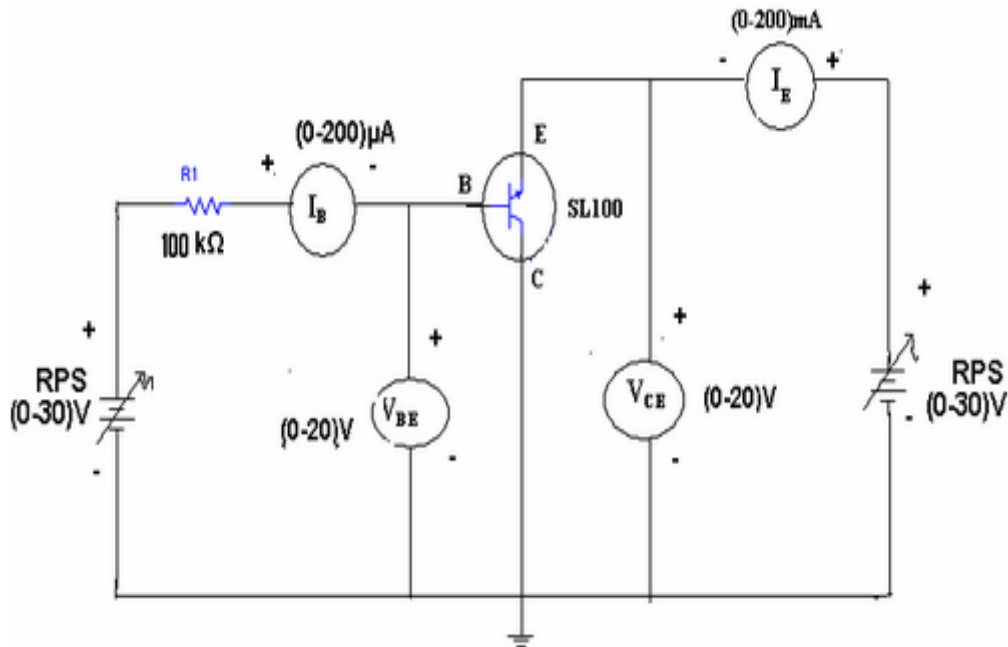

### **Procedure:**

#### **Input Characteristics:**

1. Connect the circuit as per the circuit diagram.
2. For plotting the input characteristics the output voltage  $V_{CE}$  is kept constant at 2V and note down values of  $V_{CB}$  for each value of  $I_B$
3. Change  $V_{CE}$  to 10 V and repeat the above step.
4. Disconnect the voltmeter from input circuit.
5. Plot the graph between  $V_{CB}$  and  $I_B$  for constant  $V_{CE}$


#### **Output Characteristics:**

1. Connect the circuit as per the circuit diagram
2. With  $I_B$  set at  $0\mu A$ , vary  $V_{CE}$  and note down the corresponding  $I_E$  value
3. Set  $I_B$  at  $40\mu A$ ,  $80\mu A$  and repeat the above step.
4. Plot the output characteristics between  $V_{CE}$  and  $I_E$  for constant  $I_B$ .




**Model Graphs:**

**Input Characteristics:**

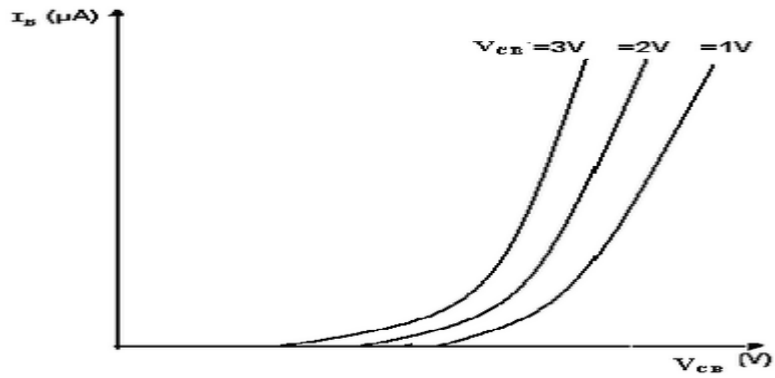

**Output Characteristics:**

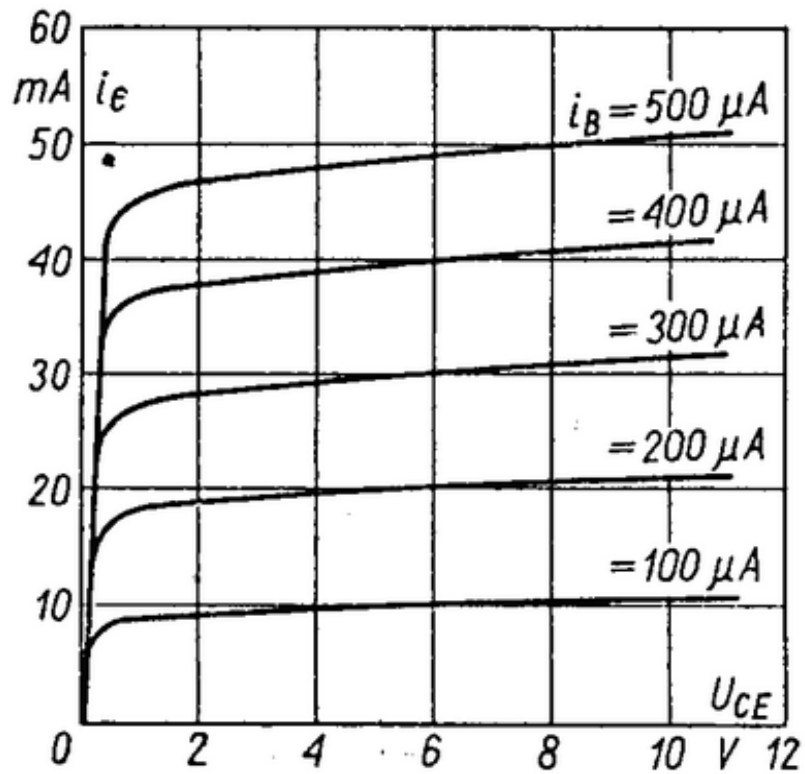

### Calculations from Graph:

The h-parameters are to be calculated from the following formulae:

1. **Input Characteristics:** To obtain input resistance, find  $\Delta V_{CB}$  and  $\Delta I_B$  for a constant  $V_{CB}$  on one of the input characteristics.

$$\text{Input impedance} = h_{ic} = R_i = \Delta V_{CB} / \Delta I_B \quad (V_{CE} = \text{constant})$$

$$\text{Reverse voltage gain} = h_{rc} = \Delta V_{CB} / \Delta V_{CE} \quad (I_B = \text{constant})$$

2. **Output Characteristics:** To obtain output resistance, find  $\Delta I_E$  and  $\Delta V_{CE}$  at a constant  $I_E$ .

$$\text{Output admittance} = h_{oc} = 1/R_o = \Delta I_E / \Delta V_{CE} \quad (I_B = \text{constant})$$

$$\text{Forward current gain} = h_{fc} = \Delta I_E / \Delta I_B \quad (V_{CE} = \text{constant})$$

### PRECAUTIONS:

1. The supply voltage should not exceed the rating of the transistor
2. Meters should be connected properly according to their polarities


### The h-parameters for a transistor in CC configuration are:


- a. The Input resistance ( $h_{ic}$ ) \_\_\_\_\_ MOhms.
- b. The Reverse Voltage Transfer Ratio ( $h_{rc}$ ) \_\_\_\_\_.
- c. The Output Admittance ( $h_{oc}$ ) \_\_\_\_\_ Ohms.
- d. The Forward Current gain ( $h_{fc}$ ) \_\_\_\_\_.
- e.

### RESULT:


### Viva Questions:

 1. What are the input and output impedances of CC configuration?
2. Identify various regions in the output characteristics?
3. Why CC configuration is preferred for buffering?
4. What is the phase relation between input and output?
5. Draw diagram of CC configuration for PNP transistor?
6. What are the applications of CC configuration?



 



 



## EXPERIMENT 4

### h- PARAMETERS CALCULATION OF CB CONFIGURATION

**AIM:** To calculate the h-parameters of transistor in CB configuration.

**APPARATUS:**

S.No.	Name	Quantity
1	Transistor BC 107	1(One) No.
2	Resistors (1K $\Omega$ )	2(Two) No.
3	Bread board	1(One) No.

**Equipment:**

S.No.	Name	Quantity
1	Dual DC Regulated Power supply (0 – 30 V)	1(One) No.
2	Digital Ammeters ( 0 – 200 mA)	2(Two) No.
3	Digital Voltmeter (0-20V)	2(Two) No.
4	Connecting wires (Single Strand)	2


**THEORY**

The basic circuit diagram for studying input characteristics is shown in the circuit diagram. The input is applied between emitter and base, the output is taken between collector and base. Here base of the transistor is common to both input and output and hence the name is Common Base Configuration.


Input characteristics are obtained between the input current and input voltage at constant output voltage. It is plotted between  $V_{EE}$  and  $I_E$  at constant  $V_{CB}$  in CB configuration.

Output characteristics are obtained between the output voltage and output current at constant input current. It is plotted between  $V_{CB}$  and  $I_C$  at constant  $I_E$  in CB configuration.

### Circuit Diagram

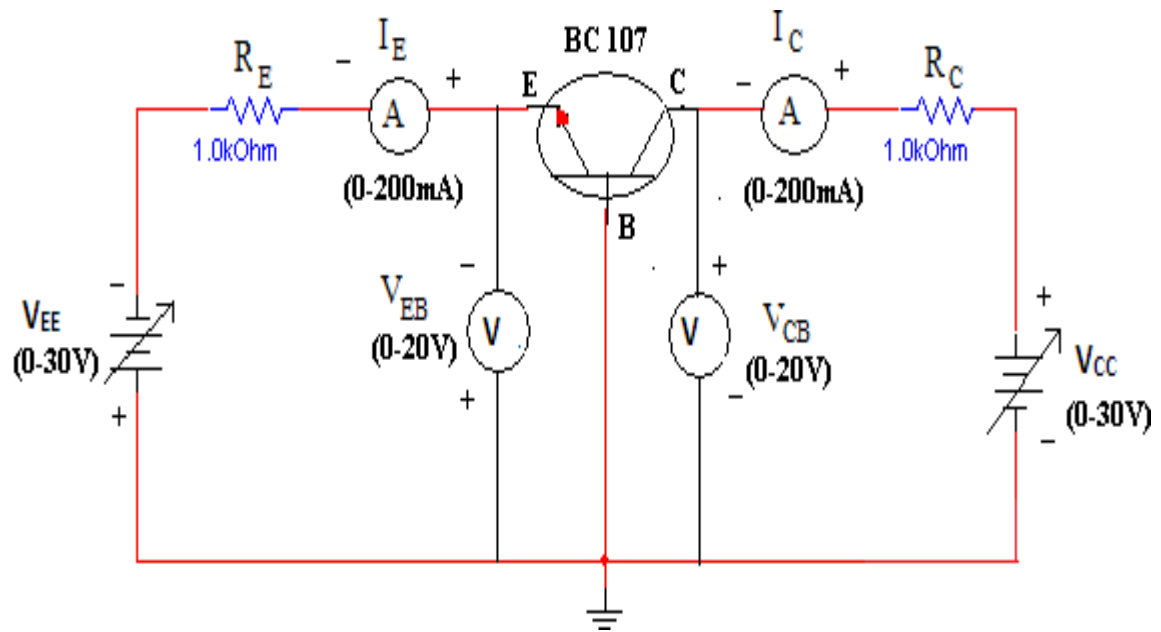

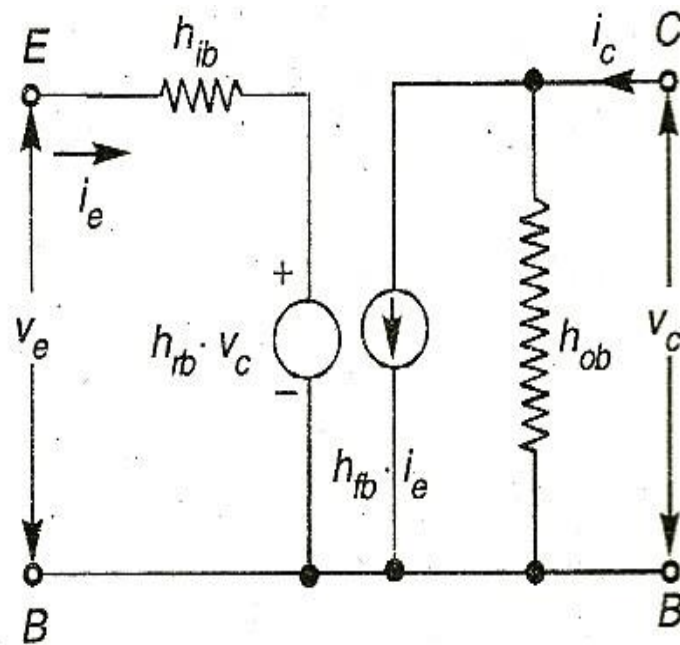**h – Parameter model of CB transistor:**



## **Procedure:**

### **Input Characteristics:**

1. Connect the circuit as shown in the circuit diagram.
2. Keep output voltage  $V_{CB} = 0V$  by varying  $V_{CC}$ .
3. Varying  $V_{EE}$  gradually, note down emitter current  $I_E$  and emitter-base voltage ( $V_{EE}$ ).
4. Step size is not fixed because of nonlinear curve. Initially vary  $V_{EE}$  in steps of 0.1 V. Once the current starts increasing vary  $V_{EE}$  in steps of 1V up to 12V.
5. Repeat above procedure (step 3) for  $V_{CB} = 4V$ .

### **Output Characteristics:**

1. Connect the circuit as shown in the circuit diagram.
2. Keep emitter current  $I_E = 5mA$  by varying  $V_{EE}$ .
3. Varying  $V_{CC}$  gradually in steps of 1V up to 12V and note down collector current  $I_C$  and collector-base voltage ( $V_{CB}$ ).
4. Repeat above procedure (step 3) for  $I_E = 10mA$ .


Repeat above procedure (step 3) for  $I_E = 10mA$ .

## **PRECAUTIONS:**

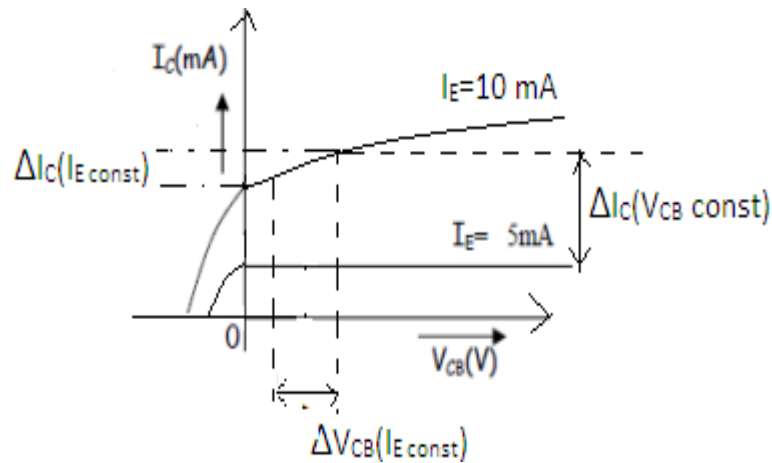1. While performing the experiment do not exceed the ratings of the transistor. This may lead to damage the transistor
2. .Connect voltmeter and ammeter in correct polarities as shown in the circuit diagram
3. The supply voltage should not exceed the rating of transistor
4. .Do not switch ON the power supply unless you have checked the circuit connections as per the circuit diagram.
5. Make sure while selecting the emitter, base and collector terminals of the transistor.
6. Take readings without any parallax error







1. Plot the input characteristics for different values of  $V_{CB}$  by taking  $V_{EE}$  on X-axis and  $I_E$  on Y-axis taking  $V_{CB}$  as constant parameter.
2. Plot the output characteristics by taking  $V_{CB}$  on X-axis and taking  $I_C$  on Y-axis taking  $I_E$  as a constant parameter.

### Calculations from Graph:

The h-parameters are to be calculated from the following formulae:

1. **Input Characteristics:** To obtain input resistance, find  $\Delta V_{EE}$  and  $\Delta I_E$  for a constant  $V_{CB}$  on one of the input characteristics.

$$\text{Input impedance} = h_{ib} = R_i = \Delta V_{EE} / \Delta I_E \quad (V_{CB} = \text{constant})$$

$$\text{Reverse voltage gain} = h_{rb} = \Delta V_{EB} / \Delta V_{CB} \quad (I_E = \text{constant})$$

2. **Output Characteristics:** To obtain output resistance, find  $\Delta I_C$  and  $\Delta V_{CB}$  at a constant  $I_E$ .

$$\text{Output admittance} = h_{ob} = 1/R_o = \Delta I_C / \Delta V_{CB} \quad (I_E = \text{constant})$$

$$\text{Forward current gain} = h_{fb} = \Delta I_C / \Delta I_E \quad (V_{CB} = \text{constant})$$

**The h-parameters for a transistor in CB configuration are:**

- a. The Input resistance ( $h_{ib}$ ) \_\_\_\_\_ Ohms.
- b. The Reverse Voltage Transfer Ratio ( $h_{rb}$ ) \_\_\_\_\_.
- c. The Output Admittance ( $h_{ob}$ ) \_\_\_\_\_ Mhos.
- d. The Forward Current gain ( $h_{fb}$ ) \_\_\_\_\_



**Result:**

**Discussion/Viva Questions:**

1. What is transistor?
2. Write the relation between  $\alpha$  and  $\beta$ ?
3. Define  $\alpha$  (alpha)? What is the range of  $\alpha$ ?
4. Why  $\alpha$  is less than unity?
5. Input and output impedance equations for CB configuration?
6. What is carrier lifetime?
7. What is the importance of Fermi level?
8. Can the junction less transistors be realized?
9. What is the doping level of E, B and C layers
- 10 List the various current components in BJT.
11. Can transistor be replaced by two back to back connected diodes?
12. To operate a transistor as amplifier, emitter junction is forward biased and collector junction is reverse biased. Why?
13. Which transistor configuration provides a phase reversal between the input and output signals?











## EXPERIMENT 5

### h-PARAMETERS OF CE CONFIGURATION

**1.AIM:** To calculate the h-parameters of transistor in CE configuration.

**2.APPRATUS:**

- |  |            |
|--|------------|
| 1. Transistor BC107                      | - 1No.     |
| 2. Resistors 100 K $\Omega$ 100 $\Omega$ | - 1No.Each |
| 3. Ammeter (0-200 $\mu$ A)               | - 1No.     |
| 4. Ammeter(0-200mA)                      | -1No.      |
| 5. Voltmeter (0-20V)                     | - 2Nos     |
| 6. Regulated Power Supply (0-30V)        | - 2Nos     |
| 7. Breadboard                            |            |

**3.THEORY:**

The basic circuit diagram for studying input characteristics is shown in the circuit diagram. The input is applied between base and emitter, the output is taken between collector and emitter. Here emitter of the transistor is common to both input and output and hence the name Common Emitter Configuration.

Input characteristics are obtained between the input current and input voltage at constant output voltage. It is plotted between  $V_{BE}$  and  $I_B$  at constant  $V_{CE}$  in CE configuration.

Output characteristics are obtained between the output voltage and output current at constant input current. It is plotted between  $V_{CE}$  and  $I_C$  at constant  $I_B$  in CE configuration.

**A) INPUT CHARACTERISTICS:**

The two sets of characteristics are necessary to describe the behaviour of the CE configuration, in which one for input or base emitter circuit and other for the output or collector emitter circuit. In input characteristics the emitter base junction forward biased by a very small voltage  $V_{BB}$  where as collector base junction reverse biased by a very large voltage  $V_{CC}$ . The input characteristics are a plot of input current  $I_B$  Versus, the input voltage  $V_{BE}$  for a range of values of output voltage  $V_{CE}$  . The following important points can be observed from these characteristics curves.

1. Input resistance is high as  $I_B$  increases less rapidly with  $V_B$
2. The input resistance of the transistor is the ratio of change in base emitter voltage  $\Delta V_{BE}$  to change in base current  $\Delta I_B$  at constant collector emitter

voltage ( $V_{CE}$ ) i.e... Input resistance or input impedance  $h_{ie} = \Delta V_{BE} / \Delta I_B$  at  $V_{CE}$  constant.

## B) OUTPUT CHARACTERISTICS:

A set of output characteristics or collector characteristics are a plot of output current  $I_C$  vs output voltage  $V_{CE}$  for a range of values of input current  $I_B$ . The following important points can be observed from these characteristics curves.

1. The transistor always operates in the active region. i.e. the collector current  $I_C$  increases with  $V_{CE}$  very slowly. For low values of the  $V_{CE}$  the  $I_C$  increases rapidly with a small increase in  $V_{CE}$ . The transistor is said to be working in saturation region.
2. Output resistance is the ratio of change of collector emitter voltage  $\Delta V_{CE}$ , to change in collector current  $\Delta I_C$  with constant  $I_B$ . Output resistance or Output impedance  $h_{oe} = \Delta V_{CE} / \Delta I_C$  at  $I_B$  constant.


Input Impedance  $h_{ie} = \Delta V_{BE} / \Delta I_B$  at  $V_{CE}$  constant

Output impedance  $h_{oe} = \Delta V_{CE} / \Delta I_C$  at  $I_B$  constant

Reverse Transfer Voltage Gain  $h_{re} = \Delta V_{BE} / \Delta V_{CE}$  at  $I_B$  constant


Forward Transfer Current Gain  $h_{fe} = \Delta I_C / \Delta I_B$  at constant  $V_{CE}$

## CIRCUIT DIAGRAM:

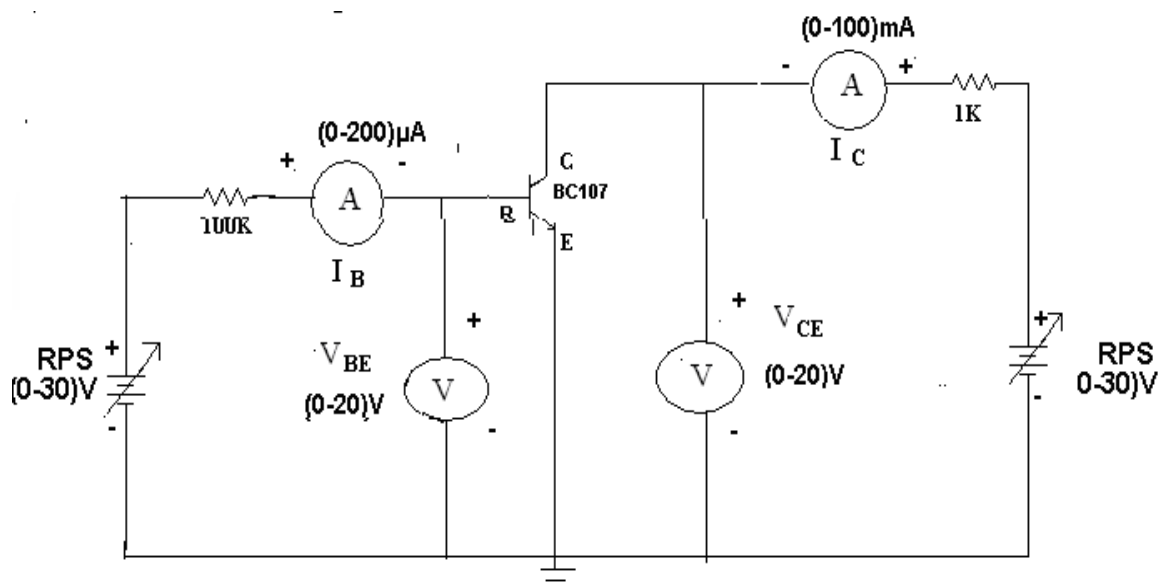



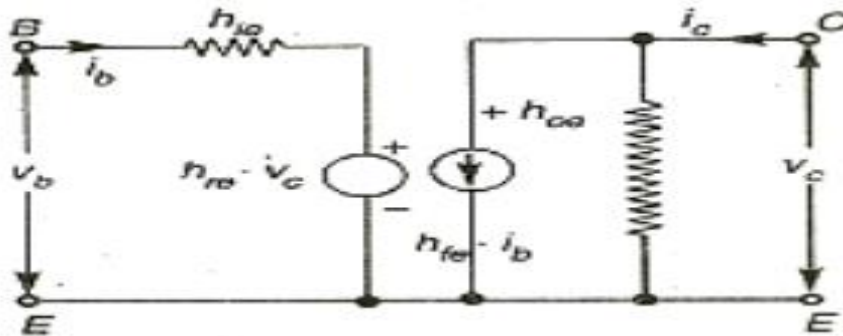
**h – Parameter model of CE transistor:**



**MODEL GRAPH:**


**A) INPUT CHARACTERISTICS:**

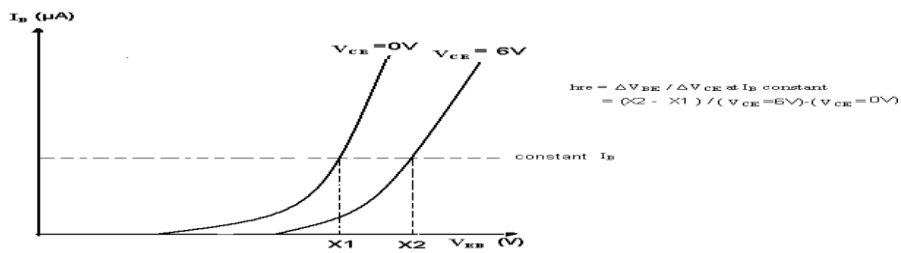- i) calculation of  $h_{ie}$
- ii) calculation of  $h_{re}$



**OUTPUT CHARACTERISTICS:**

- i) calculation of  $h_{fe}$

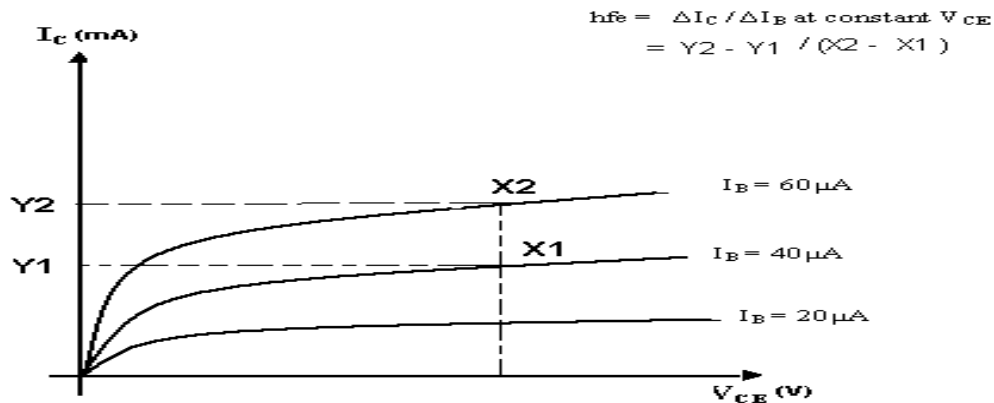





### **Output Characteristics:**

1. Connect the circuit as shown in the circuit diagram.
  2. Keep emitter current  $I_B = 20\mu\text{A}$  by varying  $V_{BB}$ .
  3. Varying  $V_{CC}$  gradually in steps of 1V up to 12V and note down collector current  $I_C$  and Collector-Emitter Voltage( $V_{CE}$ ).
  4. Repeat above procedure (step 3) for  $I_B = 60\mu\text{A}, 0\mu\text{A}$ .
- 
1. Plot the input characteristics by taking  $V_{BE}$  on X-axis and  $I_B$  on Y-axis at a constant  $V_{CE}$  as a constant parameter
  2. Plot the output characteristics by taking  $V_{CE}$  on X-axis and taking  $I_C$  on Y-axis taking  $I_B$  as a constant parameter

### **Calculations from Graph:**

1. **Input Characteristics:** To obtain input resistance find  $\Delta V_{BE}$  and  $\Delta I_B$  for a constant  $V_{CE}$  on one of the input characteristics.  
Input impedance =  $h_{ie} = R_i = \Delta V_{BE} / \Delta I_B$  ( $V_{CE}$  is constant)  
Reverse voltage gain =  $h_{re} = \Delta V_{EB} / \Delta V_{CE}$  ( $I_B = \text{constant}$ )
2. **Output Characteristics:** To obtain output resistance find  $\Delta I_C$  and  $\Delta V_{CB}$  at a constant  $I_B$ .  
Output admittance  $1/h_{oe} = R_o = \Delta I_C / \Delta V_{CE}$  ( $I_B$  is constant)  
Forward current gain =  $h_{fe} = \Delta I_C / \Delta I_B$  ( $V_{CE} = \text{constant}$ )

### **PRECAUTIONS:**

1. While performing the experiment do not exceed the ratings of the transistor. This may lead to damage the transistor.
2. Connect voltmeter and ammeter in correct polarities as shown in the circuit diagram.
3. Do not switch ON the power supply unless you have checked the circuit connections as per the circuit diagram.
4. Make sure while selecting the emitter, base and collector terminals of the transistor.


**The h-parameters for a transistor in CE configuration are:**


- a. The Input Resistance ( $h_{ie}$ ) \_\_\_\_\_ Ohms.
- b. The Reverse Voltage Gain ( $h_{re}$ ) \_\_\_\_\_.
- c. The Output Conductance ( $h_{oe}$ ) \_\_\_\_\_ Mhos.
- d. The Forward Current Gain ( $h_{fe}$ ) \_\_\_\_\_.


**RESULT:**

**VIVA QUESTIONS:**

 
1. What are the h-parameters?
2. What are the limitations of h-parameters?
3. What are its applications?
4. Draw the Equivalent circuit diagram of H parameters?
5. Define H parameter?
6. What are tabular forms of H parameters monoculture of a transistor?
7. What is the general formula for input impedance?
8. What is the general formula for Current Gain?
9. What is the general formula for Voltage gain?



 

 



 



## EXPERIMENT 6

### FREQUENCY RESPONSE OF CE AMPLIFIER

**AIM:** - 1. To Design Transistor CE amplifier and find its voltage gain.  
2. To draw the frequency response curve of CE amplifier

#### COMPONENTS & EQUIPMENTS REQUIRED: -

S.No	Devices / Components	Range/Rating	Quantity
1.	(a) DC supply voltage	12V	1
	(b) BJT	BC107	1
	(c) Capacitors	10 $\mu$ F, 100 $\mu$ F	Each 2
	(d) Resistors	2.2K, 10k, 1K	Each 2
2.	Signal generator	10Hz-1MHz	1
3.	CRO	0Hz-30MHz	1
4.	Connecting wires & CRO Probes		4


#### THEORY:

The single stage common emitter amplifier circuit shown above uses what is commonly called "Voltage Divider Biasing" or "self biasing". This type of biasing arrangement uses two resistors as a potential divider network and is commonly used in the design of bipolar transistor amplifier circuits. This type of biasing arrangement greatly reduces the effects of varying Beta, ( $\beta$ ) by holding the Base bias at a constant steady voltage. This type of biasing produces the greatest stability.

The Common Emitter Amplifier circuit has a resistor in its Collector circuit. The current flowing through this resistor produces the voltage output of the amplifier. The value of this resistor is chosen so that at the amplifiers quiescent operating point, Q-point this output voltage lies half way along the transistors load line. In Common Emitter Amplifier circuits, capacitors C1 and C2 are used as Coupling Capacitors to separate the AC signals from the DC biasing voltage. This ensures that the bias condition set up for the circuit to operate correctly is not affected by any additional amplifier stages, as the capacitors will only pass AC signals and block any DC component. The output AC signal is then superimposed on the biasing of the following stages. Also a bypass capacitor, CE is included in the Emitter leg circuit. This capacitor is an open circuit component for DC bias meaning that the biasing currents and voltages are not affected by the addition of the capacitor maintaining a good Q-point stability.


However, this bypass capacitor short circuits the Emitter resistor at high frequency signals and only  $R_L$  plus a very small internal resistance acts as the transistors load increasing the voltage gain to its maximum. Generally, the value of the bypass capacitor,  $C_E$  is chosen to provide a reactance of at most,  $1/10$ th the value of  $R_E$  at the lowest operating signal frequency. A single stage Common Emitter Amplifier is also an "Inverting Amplifier" as an increase in Base voltage causes a decrease in  $V_{out}$  and a decrease in Base voltage produces an increase in  $V_{out}$ . The output signal is  $180^\circ$  out of phase with the input signal

**CIRCUIT DIAGRAM:**

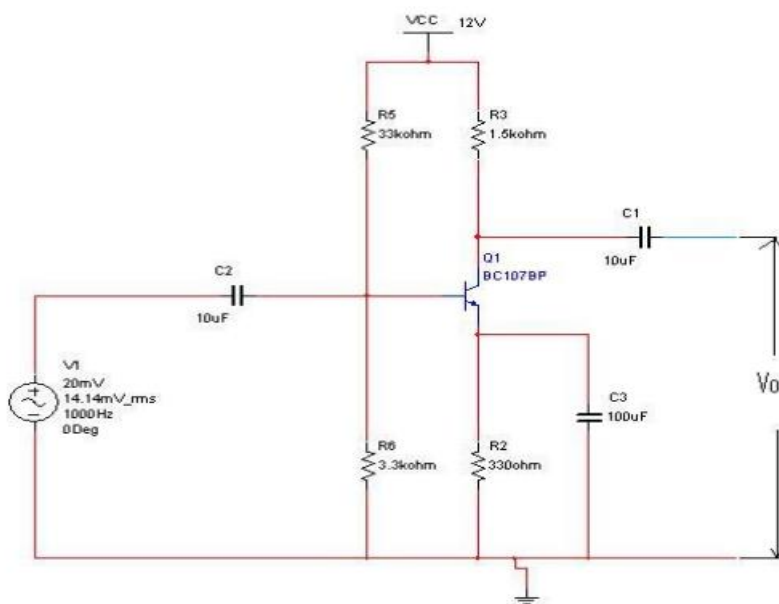


**MODELWAVE FORMS:**


**A) INPUT WAVE FORM:**

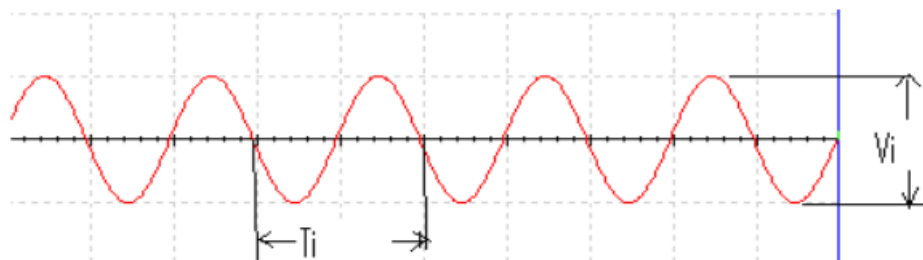

**B) OUTPUT WAVE FORM:**

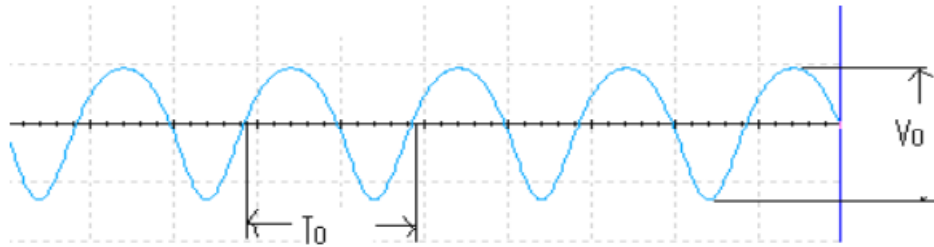

**FREQUENCY RESPONSE:**

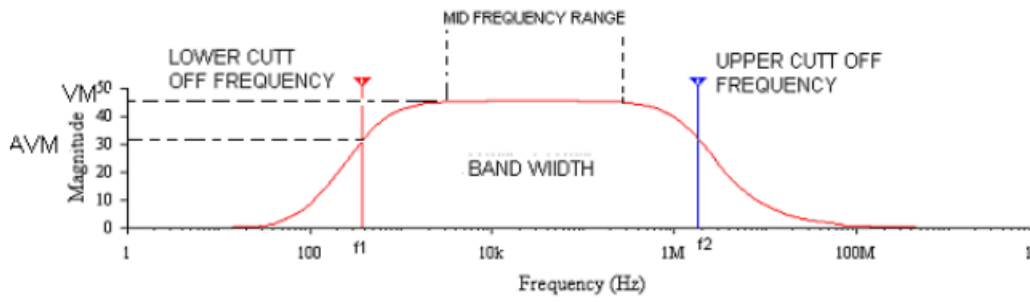

**OBSERVATIONS**

**INPUT VOLTAGE =20 MILLI VOLTS**

Frequency (in Hz)	Output Voltage (V <sub>o</sub> )	Gain $A_v = V_o/V_i$	Gain(in dB) $= 20\log_{10}(V_o/V_i)$
20			
50			
100			
1k			
10k			
100k			
200,500K			
1M			

**PROCEDURE: -**

1. Connect the circuit as shown in circuit diagram
2. Apply the input of 20mV peak-to-peak and 1 KHz frequency using Function Generator
3. Measure the Output Voltage  $V_o$  (p-p) for various load resistors
4. Tabulate the readings in the tabular form.
5. The voltage gain can be calculated by using the expression  $A_v = (V_o/V_i)$
6. For plotting the frequency response the input voltage is kept Constant at 20mV peak-to-peak and the frequency is varied from 100Hz to 1MHz Using function generator
7. Note down the value of output voltage for each frequency.
8. All the readings are tabulated and voltage gain in dB is calculated by Using The expression  $A_v = 20 \log_{10} (V_o/V_i)$
9. A graph is drawn by taking frequency on x-axis and gain in dB on y-axis On Semi-log graph.
10. The band width of the amplifier is calculated from the graph Using the expression, Bandwidth,  $BW = f_2 - f_1$   
Where  $f_1$  lower cut-off frequency of CE amplifier, and  
Where  $f_2$  upper cut-off frequency of CE amplifier
11. The bandwidth product of the amplifier is calculated using the Expression  
Gain Bandwidth product = 3-dB midband gain X Bandwidth

**PRECAUTIONS:**

1. Connections should be made carefully and avoid loose connections.
2. Check connections before switching ON power supply.
3. Don't apply over voltage
4. When you are not using the equipment switch them Off.
5. While performing the experiment do not exceed the ratings of the transistor. This may lead to damage the transistor.
6. Connect voltmeter and ammeter in correct polarities as shown in the circuit diagram.
7. Do not switch ON the power supply unless you have checked the circuit connections as per the circuit diagram.
8. Make sure while selecting the emitter, base and collector terminals of the transistor.

**APPLICATIONS:**


1. Common-emitter amplifiers are also used in radio frequency transceiver circuits.
2. Common emitter configuration commonly used in low-noise amplifiers.

**RESULT:**


1. Frequency response of BJT amplifier is plotted.
2. Gain = \_\_\_\_\_dB (maximum).
3. Bandwidth=  $f_H - f_L =$  \_\_\_\_\_Hz


**VIVA QUESTIONS:**

 1. What is the phase difference between input and output waveforms of CE amplifier?
2. What type of biasing is used in the given circuit?
3. If the given transistor is replaced by P-N-P, can we get the output or not?
4. What is the effect of emitter bypass capacitor on frequency response?
5. What is the effect of coupling capacitor?
6. What is the region of transistor so that it operates as an amplifier?
7. Draw the h-parameter model of CE amplifier.
8. How does transistor acts as an amplifier.
9. Mention the characteristics of CE amplifier





 

 



## EXPERIMENT 7

# FREQUENCY RESPONSE OF CC AMPLIFIER

### AIM:

1. To measure the voltage gain of a CC amplifier
2. To draw the frequency response of the CC amplifier


### APPARATUS:

1. Transistor BC 107 -1No.
2. Regulated Power Supply (0-30V) -1No.
3. Function Generator -1No.
4. CRO-1No.
5. Resistors
6.  $33\text{K}\Omega$ ,  $3.3\text{K}\Omega$ ,  $330\Omega$ , -1No.Each
7.  $1.5\text{K}\Omega$ ,  $1\text{K}\Omega$ ,  $2.2\text{K}\Omega$  &  $4.7\text{K}\Omega$
8. Capacitors  $10\mu\text{F}$  -2Nos  $100\mu\text{F}$  -1No
9. . Breadboard
10. Connecting wires

 
### THEORY:

In common-collector amplifier the input is given at the base and ground terminals and the output is taken across the emitter and collector terminals. In this amplifier, there is no phase inversion between input and output. The input impedance of the CC amplifier is very high and output impedance is low. The voltage gain is less than unity. Here the collector is at ac ground and the capacitors used must have a negligible reactance at the frequency of operation. This amplifier is used for impedance matching and as a buffer amplifier. This circuit is also known as emitter follower. The most common use of the emitter follower is as a circuit, which performs the function of impedance transformation over a wide range of frequencies.

The input characteristics resemble that of a forward biased diode curve. This is expected since the Base-Emitter junction of the transistor is forward biased. The output characteristics are drawn between  $I_E$  and  $V_{CE}$  at constant  $I_B$ . The emitter current varies with  $V_{CE}$  upto few volts only. After this the emitter current becomes almost constant, and independent of  $V_{CE}$ . The value of  $V_{CE}$  up to which the collector current changes with  $V_{CE}$  is known as Knee voltage. The transistor always operated in the region above Knee voltage,  $I_E$  is always constant and is approximately equal to  $I_B$ .




**CIRCUIT DIAGRAM:**

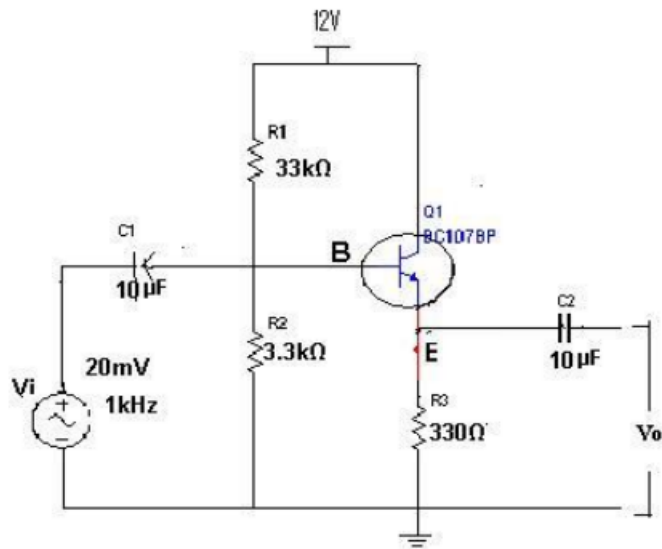


**MODEL WAVEFORM:**


**A) INPUT WAVEFORM:**

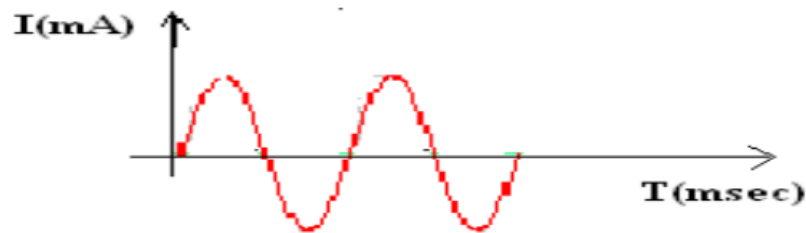

**B) OUTPUT WAVEFORM:**

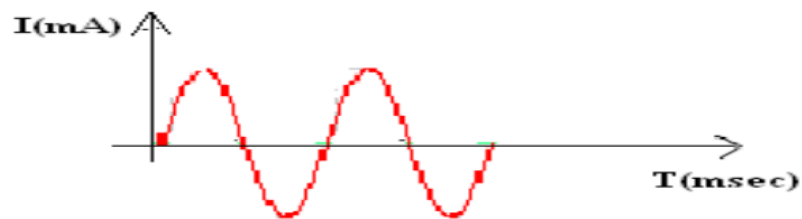

**FREQUENCY RESPONSE PLOT:**

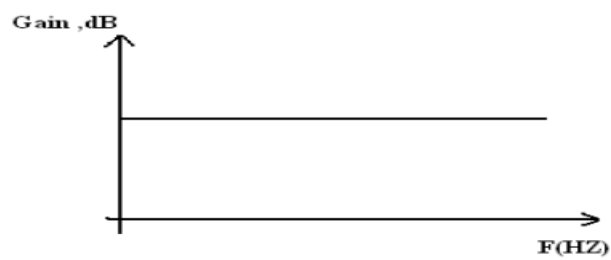

**OBSERVATIONS:**

**A) FREQUENCY RESPONSE,  $V_i = 20\text{mV}$**

Frequency(HZ)	Output Voltage( $V_o$ )	Gain in dB $A_v=20\log_{10}(V_o/V_i)$

**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. The voltage gain calculated by using the expression  $A_v=V_o/V_i$
3. For plotting the frequency response the input voltage is kept constant a 20mV peak-to- peak and the frequency is varied from 100Hz to 1MHz.
4. Note down the values of output voltage for each frequency.
5. The voltage gain in dB is calculated by using the expression,  $A_v=20\log_{10}(V_o/V_i)$
6. A graph is drawn by taking frequency on X-axis and gain in dB on y-axis on semi-log graph sheet.
7. The Bandwidth of the amplifier is calculated from the graph using the Expression,  
Bandwidth  $BW=f_2-f_1$   
Where  $f_1$  is lower cut-off frequency of CE amplifier  
 $f_2$  is upper cut-off frequency of CE amplifier
8. The gain Bandwidth product of the amplifier is calculated using the Expression,  
Gain -Bandwidth product=3-dB midband gain X Bandwidth

**PRECAUTIONS:**

1. The input voltage must be kept constant while taking frequency response.
2. Proper biasing voltages should be applied.
3. The supply voltages should not exceed the rating of the transistor.
4. Meters should be connected properly according to their polarities.
5. While performing the experiment do not exceed the ratings of the transistor.  
This may lead to damage the transistor.


6. Connect voltmeter and ammeter in correct polarities as shown in the circuit diagram.
7. Do not switch ON the power supply unless you have checked the circuit connections as per the circuit diagram.
8. Make sure while selecting the emitter, base and collector terminals of the transistor.


**RESULT:**


**VIVA QUESTIONS:**

 1. What are the applications of CC amplifier?
2. What is the voltage gain of CC amplifier?
3. What are the values of input and output impedances of the CC amplifier?
4. To which ground the collector terminal is connected in the circuit?
5. Identify the type of biasing used in the circuit?
6. Give the relation between  $\alpha$ ,  $\beta$  and  $\gamma$ .
7. Write the other name of CC amplifier?
8. What are the differences between CE, CB and CC?
9. When compared to CE, CC is not used for amplification. Justify your answer
10. What is the phase relationship between input and output in CC?





 

 



## EXPERIMENT 8

### 8.TWO STAGE RCCOUPLED AMPLIFIER

**AIM:** To obtain the frequency response of a two stage RC coupled amplifier.  
Calculate gain. & Calculate bandwidth.

#### **Apparatus:**

1. Transistors BC 107
2. Resistors
3. Capacitors
4. Signal Generators
5. CRO
6. Breadboard
7. Connecting wires

#### **THEORY:**


The output from a single stage amplifier is usually insufficient to drive an o/p device. To achieve more gain, the o/p of one stage is given as the input to the other stage which forms multistage amplifier. If the two stages are coupled by R and C, then the amplifier is called RC coupled amplifier. The performance of an amplifier can be determined from the following terms.

**Gain:-** The gain is defined as ratio of output to input. The gain of multistage amplifier is equal to the product of gains of individual stages i.e  $G=G_1.G_2.G_3$ .

#### **Frequency Response:**

At low frequencies (<50HZ) the reactance of coupling capacitor  $C_c$  is high and hence very small part of signal will pass from one stage to next stage. This increases the loading effect of next stage and reduces the voltage gain. At high frequencies, capacitance reduces. Due to this base emitter junction is low which increases the base current. This reduces the amplification factor. At mid frequencies, the voltage gain of the amplifier is Constant. In this range, as frequency increases, reactance of  $CC$  reduces which tends to increase the gain. At the same time, lower reactance means higher reactance of first stage and hence lowers gain; these two factors cancel each other resulting in a uniform gain at mid frequency


## CIRCUIT DIAGRAM:

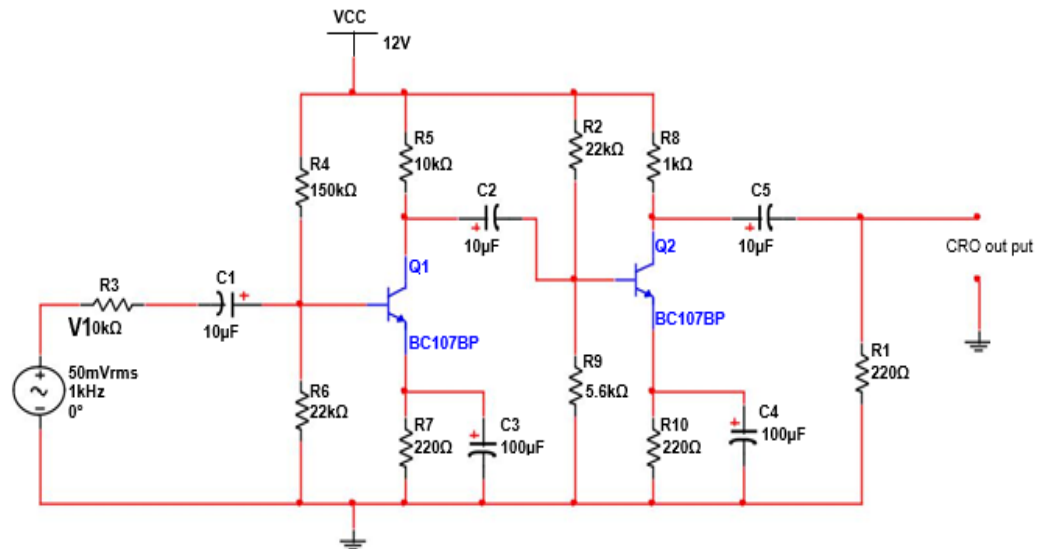

## PROCEDURE

1. Connect the circuit as per the circuit diagram
2. Give 1 KHz signal, 25 mV (p-p) as  $V_s$  from signal generator
3. Observe the output on CRO for proper working of the amplifier
4. After ensuring the amplifier function, vary signal frequency from 50 Hz to 600 Hz in proper steps for 15 to 20 readings.
5. Keeping  $V_s = 25$  mV (p-p) at every frequency,
6. note down the resetting output voltage and tabulate in a table.
7. Calculate gain db
8. plot on semi log graph paper for frequency VS gain db.

### Expected waveforms:

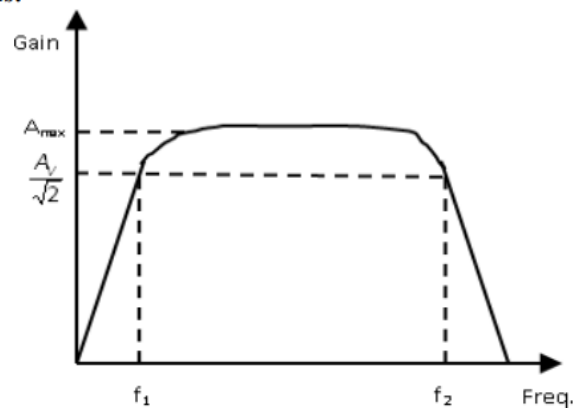

**TABULAR FORM:**

Input voltage = 50mv

TABULAR COLUMN:

Input = 50mV

Frequency (in Hz)	Output Voltage ( $V_o$ )		Gain $A_v = V_o/V_i$		Gain (in dB) = $20\log_{10}(V_o/V_i)$	
	With feedback	Without feedback	With feedback	Without feedback	With feedback	Without feedback
20						
40						
80						
100						
1K						
10k						
50k, 100K						
1M						

**PRECAUTIONS:**

1. Wires should be checked for good continuity
2. Transistor terminals must be identified and connected carefully
3. Avoid loose connections and give proper input Voltage


**RESULT:**


1. Frequency response of BJT in Two Stage RC Coupled Amplifier is plotted.
2. Gain = \_\_\_\_\_ dB (maximum).
  1. Bandwidth=  $f_H$ -- $f_L$  = \_\_\_\_\_ Hz. At stage I
  2. Bandwidth=  $f_H$ -- $f_L$  = \_\_\_\_\_ Hz. At stage 2


### **VIVA QUESTIONS:**

 1. Why do you need more than one stage of amplifiers in practical circuits?
2. What is the effect of cascading on gain and bandwidth?
3. What happens to the 3dB frequencies if the number of stages of amplifiers increases?
4. Why we use a logarithmic scale to denote voltage or power gains, instead of using the simpler linear scale?
5. What is loading effect in multistage amplifiers?





 

 



## EXPERIMENT 9

### VOLTAGE SERIES FEEDBACK AMPLIFIER

**AIM:** To study the voltage gain, frequency response, and Bandwidth of a Voltage Series feed-back amplifier with and without feedback.

#### Apparatus Required:

S.No	Device	Range/Rating	Qty
1	(a) DC supply voltage (b) BJT (c) Capacitors (d) Resistors	12V BC107BP 10 $\mu$ F,47 $\mu$ F , 10k $\Omega$ ,47 k $\Omega$ ,100k $\Omega$ 5 k $\Omega$ ,4.7k $\Omega$ ,1k $\Omega$ ,470 $\Omega$	1  1,2 2,1 From each one
2	Signal generator	0.1Hz-1MHz	1
3	CRO	0Hz-20MHz	1
4	Connecting wires		Required


#### THEORY:

Feedback plays a very important role in electronic circuits and the basic parameters, such as input impedance, output impedance, current and voltage gain and bandwidth, may be altered considerably by the use of feedback for a given amplifier. A portion of the output signal is taken from the output of the amplifier and is combined with the normal input signal and thereby the feedback is accomplished. There are two types of feedback. They are i) Positive feedback and ii) Negative feedback. Negative feedback helps to increase the bandwidth, decrease gain, distortion, and noise, modify input and output resistances as desired.


Here the amplifier and feedback network are connected in series-parallel. A fraction of the output voltage is applied in series opposition to the input voltage through feedback network Thus feedback voltage is given as As seen, the input impedance of the amplifier and output impedance of the feedback network appear in series to the input and therefore input impedance to the

amplifier is increased by factor  $(1 + \beta A)$ . Similarly input to the feedback network and output of the amplifier appear in parallel to the amplifier output.

**CIRCUIT DIAGRAM:  
WITHOUT FEEDBACK**

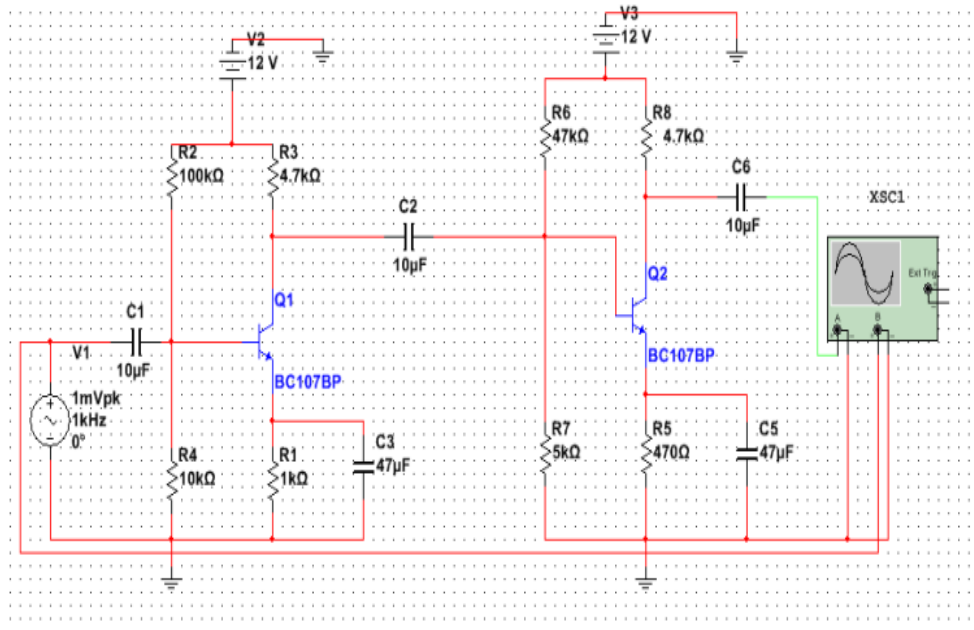

**WITH FEEDBACK:**

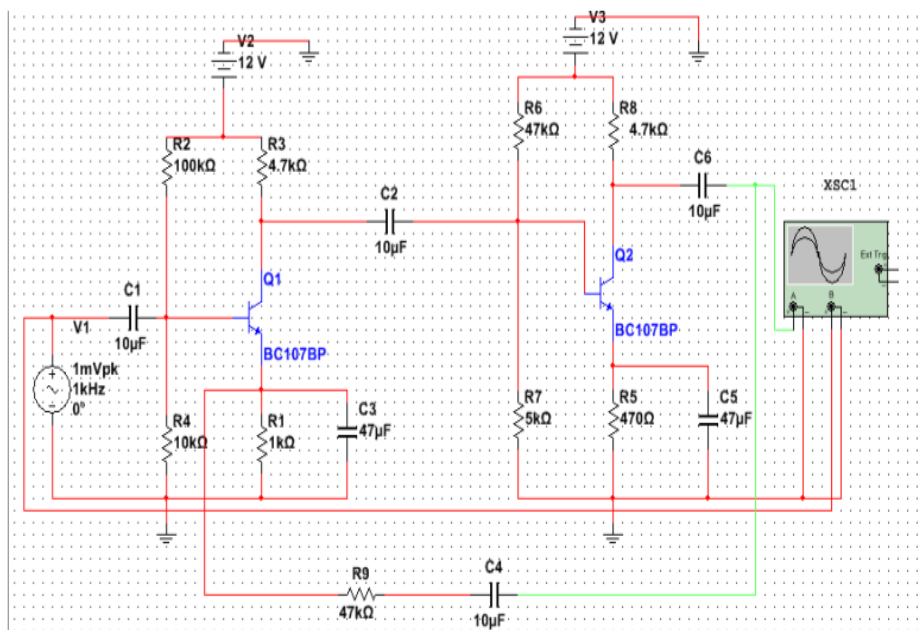

**PROCEDURE:**

1. Connections are made as per circuit diagram.
2. Keep the input voltage constant at 20mV peak-peak and 1kHz frequency.
3. For different values of load resistance, note down the output voltage and calculate the gain by using the expression  $A_v = 20\log(V_0 / V_i)$  db
4. Remove the emitter bypass capacitor and repeat STEP 2. And observe the effect of feedback on the gain of the amplifier.
5. For plotting the frequency the input voltage is kept constant at 20mV peak-peak and the frequency is varied from 100Hz to 1MHz.
6. Note down the value of output voltage for each frequency.
7. All the readings are tabulated and the voltage gain in dB is calculated by using expression 8.  $A_v = 20\log(V_0 / V_i)$  dB
8. A graph is drawn by taking frequency on X-axis and gain on Y-axis on semi log graph
9. The Bandwidth of the amplifier is calculated from the graph using the expression

$$\text{Bandwidth B.W} = f_2 - f_1.$$

Where  $f_1$  is lower cutt off frequency of CE amplifier

$f_2$  is upper cutt off frequency of CE amplifier

13. The gain-bandwidth product of the amplifier is calculated by using the expression

$$\text{Gain-Bandwidth Product} = 3\text{-dB mid band gain} \times \text{Bandwidth}$$

**APPLICATIONS:**



1. They are used in almost all electronic amplifiers.
2. They are used in regulated power supplies.
3. In amplifiers having large bandwidth.

**TABULAR COLOUMN:**


$V_{in}=20\text{mv}$

Frequency (in Hz)	Output voltage without feedback	Output voltage with feedback	Gain without feedback $(\frac{V_0}{V_{in}})$	Gain with feedback $(\frac{V_0}{V_{in}})$	Gain in dB without feedback $20 \log(\frac{V_0}{V_{in}})$	Gain in dB with feedback $20 \log(\frac{V_0}{V_{in}})$
20						
50						
100						
1K						
10K						
100K						
200K,500K						
1M						

**Model Graph:**

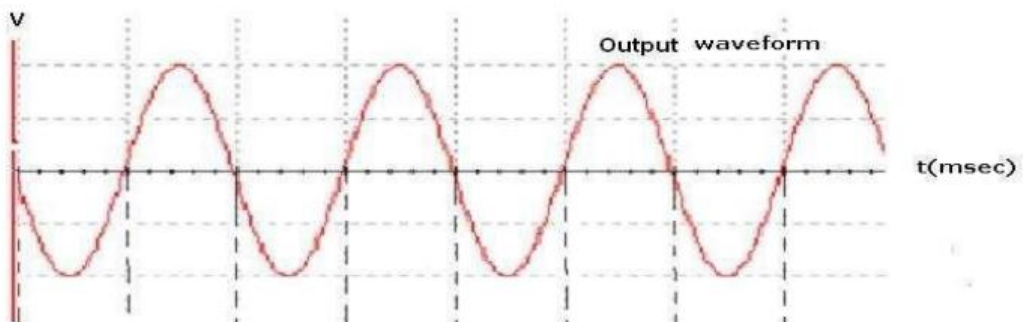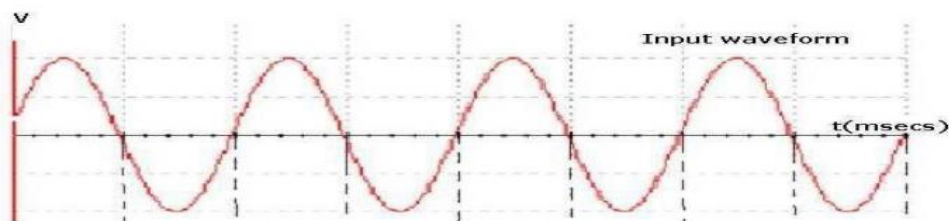



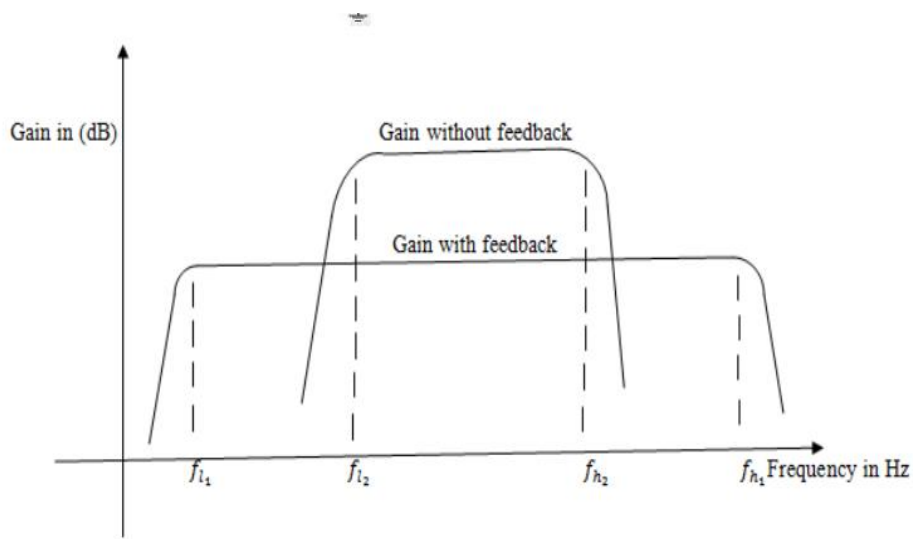



**RESULT:** - With feed-back, gain decreases and band width increases


1. Frequency response of Voltage-Series Feedback amplifier is plotted.
2. Gain = \_\_\_\_\_ dB (maximum).without Feed-back.
- 3 Gain = \_\_\_\_\_ dB (maximum).with Feed-back.
4. Bandwidth=  $f_H - f_L$  = \_\_\_\_\_ Hz. without Feed-back.
5. Bandwidth=  $f_H - f_L$  = \_\_\_\_\_ Hz. with Feed-back.

### VIVA QUESTIONS:

 - 1.What is feedback?
2. What are the characteristics of feedback?
3. What is meant by sampling and mixing?
4. What are the configurations of feedback amplifiers?
5. What is the effect of feedback on an amplifier?
6. What is the effect of feedback on input and output resistances?



 

 



## EXPERIMENT-10

### CURRENT SHUNT FEEDBACK AMPLIFIER

#### AIM:

To determine the effect of feedback on the frequency response of a current shunt feedback amplifier.

1. To calculate gain without feedback.
2. To calculate gain with feedback.

#### COMPONENTS AND EQUIPMENTS REQUIRED:


S.No	Devices / Components	Range/ Rating	Quantity(in No.s)
1.	a) DC Supply voltage.	12 V	1
2.	b) NPN Transistor.	BC 107	2
3.	c) Resistors.	47k $\Omega$	2
		2.2K $\Omega$	2
		10k $\Omega$	1
		1k	2
4.	d) Capacitor.	0.1 $\mu$ F.	1
		22 $\mu$ F.	3
5.	Function Generator.	0.1 Hz-10 MHz	1
6.	CRO	0-20MHZ	1
7.	Connecting wires and Probes		4

#### THEORY:

Feedback plays a very important role in electronic circuits and the basic parameters, such as input impedance, output impedance, current and voltage gain and bandwidth, may be altered considerably by the use of feedback for a given amplifier. A portion of the output signal is taken from the output of the amplifier and is combined with the normal input signal and thereby the feedback is accomplished. There are two types of feedback. They are i) Positive

feedback and ii) Negative feedback. Negative feedback helps to increase the bandwidth, decrease gain, distortion, and noise, modify input and output resistances as desired. A current shunt feedback amplifier circuit is illustrated in the figure. It is called a series-derived, shunt-fed feedback. The shunt connection at the input reduces the input resistance and the series connection at the output increases the output resistance. This is a true current amplifier.

**CIRCUIT DIAGRAM:**

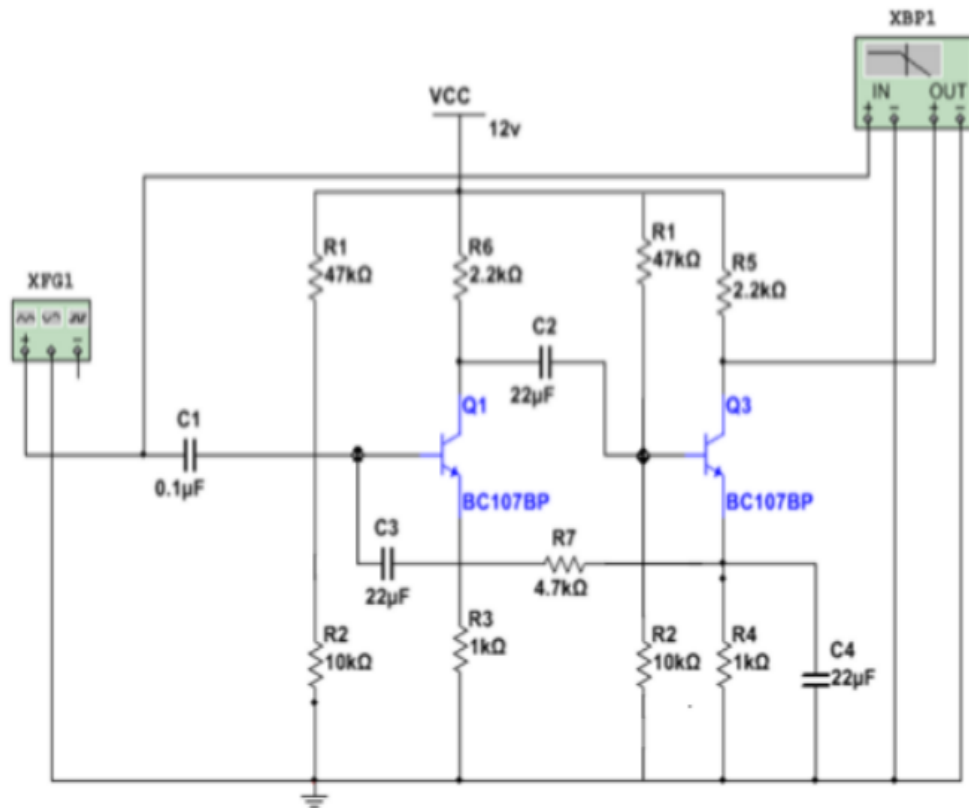


**PROCEDURE:**

1. Connect the circuit as shown in figure
2. Adjust input signal amplitude in the function generator and observe an amplified voltage at the output without distortion
3. By keeping input signal voltage, say at 50 mV, vary the input signal frequency from 10HZ to 1 MHz as shown in tabular column and note the corresponding output voltage.
4. Calculate the voltage gain in dB using the formula  $A_v = 20 \log(V_o/V_i)$ .
5. Plot AV VS frequency on the Semi-log Sheet.

6. For current shunt feedback amplifier with feedback connect the output of the feedback amplifier to the other channel of the CRO and Repeat the above procedure.

**EXPECTED GRAPH:**

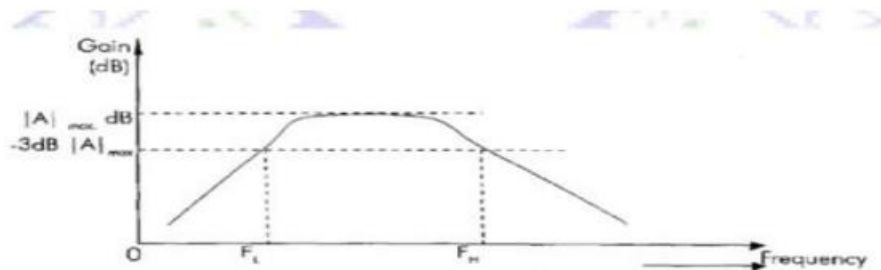

**OBSERVATIONS**

Input = 50mV

Frequency (in Hz)	Output Voltage (Vo)		Gain $A_v = V_o/V_i$		Gain (in dB) $= 20 \log_{10}(V_o/V_i)$	
	With feedback	Without feedback	With Feedback	Without Feedback	With feedback	Without feedback
10 HZ						
20 HZ						
40 HZ						
80 HZ						
100 HZ						
1K						
10 K						
20 K						
40 K						
50 K						

**PRECAUTIONS:**

1. All the connections are to be connected properly.
2. Check the connections before giving the power supply
3. Observations should be taken carefully.



**APPLICATIONS:**


1. They are used in almost all electronic amplifiers.
2. They are used in regulated power supplies.
3. In amplifiers having large bandwidth.


**RESULT:**


The  $A_v$  of the current shunt feedback amplifier is \_\_\_\_\_ and the bandwidth is \_\_\_\_\_ without feedback and The  $A_v$  of the current shunt feedback amplifier is \_\_\_\_\_ and the bandwidth is \_\_\_\_\_ with feedback


**. VIVA QUESTIONS:**

 1. What is feedback?
2. What are the characteristics of feedback?
3. What is meant by sampling and mixing?
4. What are the configurations of feedback amplifiers?
5. What is the effect of feedback on an amplifier?
6. What is the effect of feedback on input and output resistances



 

 

 



## EXPERIMENT 11 COLPITTS OSCILLATOR

### AIM:

Find practical frequency of Colpitt's oscillator and to compare it with theoretical Frequency for 1.  $L= 20\text{mH}$  and  $C= 0.001\mu\text{F}$ , 2.  $L= 20\text{mH}$  and  $0.1\mu\text{F}$

### COMPONENTS :


S.No	Devices / Components	Range/Rating	Quantity
1	a) DC supply voltage	12V	1
	b) Inductors	20Mh	1
	c) Capacitor	0.01 $\mu\text{F}$ ,0.1 $\mu\text{F}$ ,100nf	1
	d) Resistor	10K $\Omega$ ,100K $\Omega$ ,2.5K $\Omega$ ,5K $\Omega$ ,1K $\Omega$	1
	e) NPN Transistor	BC 107	1
2	Cathode Ray Oscilloscope	(0-20) MHz	1
3	Connecting wires& CRO Probes		4

### THEORY:

The Colpitts circuit, like other LC oscillators, consists of a gain device with its output connected to its input in a feedback loop containing a parallel LC circuit (tuned circuit) which functions as a bandpass filter to set the frequency of oscillation. Colpitts oscillator is the electrical dual of a Hartley oscillator, where the feedback signal is taken from an "inductive" voltage divider consisting of two coils in series (or a tapped coil).  $L$  and the series combination of  $C_1$  and  $C_2$  form the parallel resonant tank circuit which determines the frequency of the oscillator. The voltage across  $C_2$  is applied to the base-emitter junction of the transistor, as feedback to create oscillations. Here the voltage across  $C_1$  provides feedback. The frequency of oscillation is approximately the resonant frequency of the LC circuit, which is the series combination of the two capacitors in parallel with the inductor. The actual frequency of oscillation will be slightly lower due to junction capacitances and resistive loading of the transistor. As with any oscillator, the amplification of the active component should be marginally larger than the attenuation of the capacitive voltage divider, to obtain stable operation. Thus, a Colpitts oscillator used as a variable frequency oscillator (VFO) performs best when a variable inductance is used for tuning, as

opposed to tuning one of the two capacitors. If tuning by variable capacitor is needed, it should be done via a third capacitor connected in parallel to the inductor (or in series as in the Clapp oscillator).


### CIRCUIT DIAGRAM:

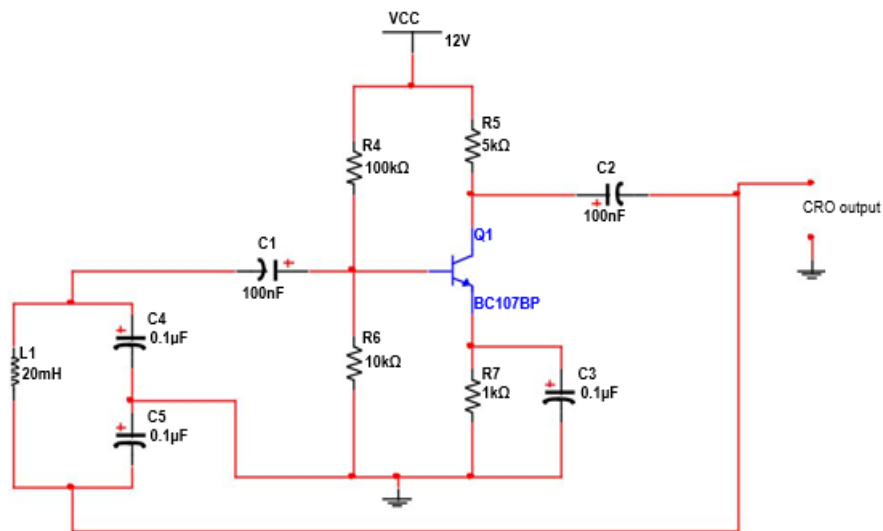

### PROCEDURE:-

1. Connect the circuit as shown in the figure
2. Connect the output of the Colpitts Oscillator kit to the CRO.
3. Observe the sinusoidal signal as an output and note down the time period of the oscillation
4. Compare the practical frequency with the theoretical frequency

### EXPECTED GRAPH:

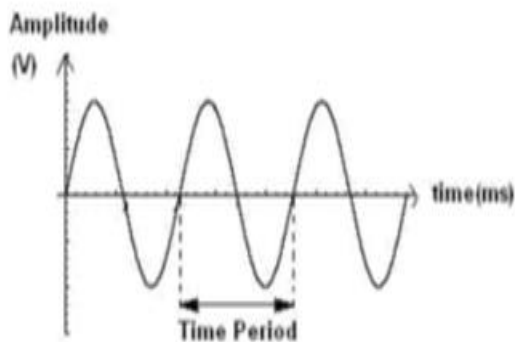



**OBSERVATION TABLE:**

S.No	L (mH)	C1( $\mu$ F)	C2( $\mu$ F)	Theoretical frequency(KHz)	Practical frequency(KHz)
1	20	0.01	0.01		
2	20	0.1	0.1		

**PRECAUTIONS:-**

- 1.No loose connections at the junctions & Check the continuity of the connecting terminals before going to connect the circuit.
2. Identify the emitter, base and collector of the transistor properly before connecting it in the circuit.
3. The horizontal length between two successive peaks should accurately be measure

**APPLICATIONS**

1. Colpitts oscillators are used for high frequency range and high frequency stability
2. It is used for generation of sinusoidal output signals with very high frequencies.
3. A surface acoustical wave (SAW) resonator
4. It is used for the development of mobile and radio communications.
5. Used for applications in which undamped and continuous oscillations are desired for functioning.

**RESULT:**

1. For C=0.01 $\mu$ F, 0.1uf & L= 20mH  
Theoretical frequency = \_\_\_\_\_  
Practical frequency = \_\_\_\_\_
2. For C=0.1 $\mu$ F, 0.1uf & L= 20mH  
Theoretical frequency = \_\_\_\_\_  
Practical frequency = \_\_\_\_\_

**VIVA-QUESTIONS:**

1. What is an Oscillator?
2. What is the main difference between an amplifier and an oscillator?
3. State Barkhausen criterion for oscillation.
4. State the factors on which oscillators can be classified.
5. What are the factors which contribute to change in frequency in oscillators
6. State the applications of Colpitt's oscillator?



## EXPERIMENT 12

### HARTLEY OSCILLATOR

**AIM:**

Find practical frequency of a Hartley oscillator and to compare it with theoretical frequency for  $L = 10\text{mH}$  and  $C = 20\text{nF}$ .

**APPARATUS REQUIRED:**


S.No	Device	Range/Rating	Quantity
1	a) DC supply voltage	12V	1
	b) Inductors	10mH	2
	c) Capacitor	20nF, 10uF, 47uF	1,2,1
	d) Resistor	1K $\Omega$ , 10K $\Omega$ , 4.7K $\Omega$ , 100K $\Omega$	Each 1
	e) NPN Transistor	BC 107	1
2	Cathode Ray Oscilloscope	(0-20) MHz	1
3	BNC Connector		1
4	Connecting wires		Required

**THEORY:**

In a Hartley oscillator the oscillation frequency is determined by a tank circuit comprising of two inductors and one capacitor. The inductors are connected in series and the capacitor is connected across them in parallel. Hartley oscillators are commonly used in radio frequency (RF) oscillator applications and the recommended frequency range is from 20KHz to 30MHz. Hartley oscillators can be operated at frequencies lower than 20KHz, but for lower frequencies the inductor value need to be high and it has a practical limit.

The circuit diagram of a typical Hartley oscillator is shown in the figure .


## CIRCUIT DIAGRAM:

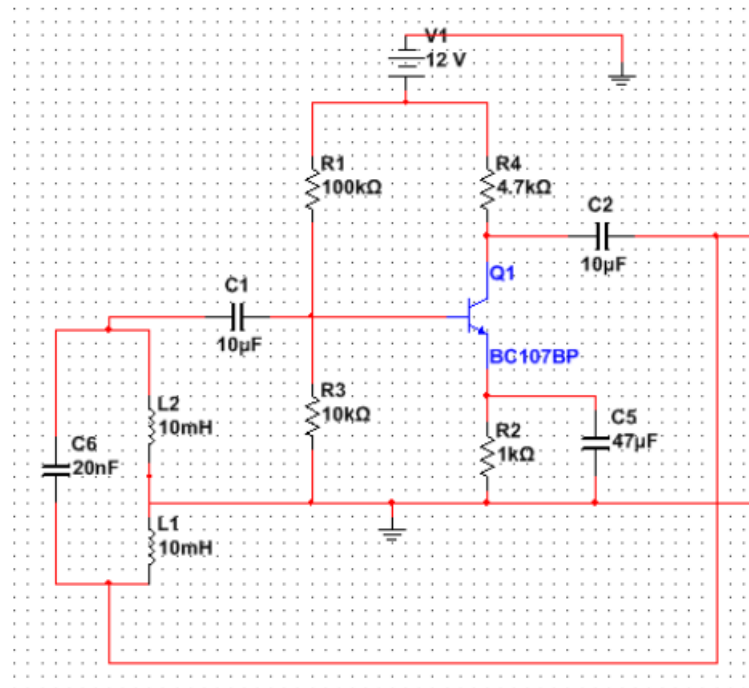

## PROCEDURE:

1. Connect the circuit as shown in figure.
2. With  $C6=20\text{nF}$  capacitor and  $L1=L2=10\text{mH}$  in the circuit and observe the waveform.
3. Time period of the waveform is to be noted and frequency is to be calculated by the formula  $f = 1/T$ .
4. Find the theoretical frequency from the formula  
$$f = \frac{1}{2\pi\sqrt{L_T C}}$$
Where  $L_T = L1 + L2 = 10\text{mH} + 10\text{mH} = 20\text{mH}$
5. compare theoretical and practical values

## EXPECTED GRAPH:

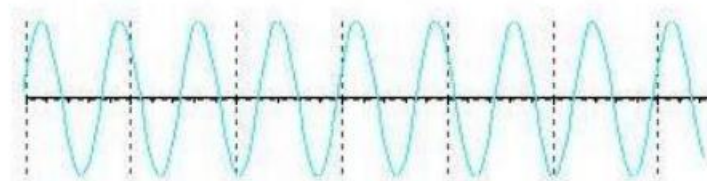

## OBSERVATIONS:

I. Theoretical frequency of oscillation:  $L_1=L_2=$  \_\_\_\_\_ AND  $C=$  \_\_\_\_\_

$$L = L_1 + L_2$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

II. Practical frequency of oscillation:  $T=$  \_\_\_\_\_

$$f_0 = 1/T = \text{ Hz } \underline{\hspace{2cm}}$$

## OBSERVATION TABLE:

S.No	L1 mH	L2 mH	C( $\mu$ F)	Theoretical frequency(KHz)	Practical frequency(KHz)
1					
2					
3					

## PRECAUTIONS:

1. Observations should be taken carefully
2. Identify the emitter, base and collector of the transistor properly before connecting it in the circuit.
3. The horizontal length between two successive peaks should accurately be measured.

## APPLICATIONS

1. The Hartley oscillator is to produce a sine wave with the desired frequency
2. Hartley oscillators are mainly used as radio receivers
3. The Hartley oscillator is Suitable for oscillations in RF (Radio-Frequency) range, up to 30MHZ

**RESULT:**

1. For  $C = 20\text{nF}$ , &  $L = 20\text{ mH}$ ;  
Theoretical frequency =  
Practical frequency =

**VIVA QUESTIONS:**

1. Classification of oscillators.
2. Give the applications of oscillator
3. Give an example for LC oscillator.
4. Which phenomenon is employed for crystal oscillator.
5. What is the main difference between an amplifier and an oscillator?
6. State Barkhausen criterion for oscillation.
7. State the factors on which oscillators can be classified.
8. What are the factors which contribute to change in frequency in oscillators?

