

Code No: R15A0401**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****II B.Tech I Semester Supplementary Examinations, April 2023****Electronic Devices and Circuits****(ECE & CSE)**

Roll No										
----------------	--	--	--	--	--	--	--	--	--	--

Time: 3 hours**Max. Marks: 75****Note:** This question paper contains two parts A and B

Part A is compulsory which carries 25 marks and Answer all questions.

Part B Consists of 5 SECTIONS (One SECTION for each UNIT). Answer FIVE Questions, Choosing ONE Question from each SECTION and each Question carries 10 marks.

PART-A (25 Marks)

- 1). a Draw the ideal diode model for forward and reverse bias. [2M]
- b Compare the V-I Characteristics of Ideal diode and non-ideal diode. [3M]
- c Draw the circuit diagram of half wave rectifier. [2M]
- d Draw the block diagram of the regulated power supply. Name the function of each block. [3M]
- e Enumerate the operating regions of a transistor. In which regions it operates like a switch. [2M]
- f The operating point of a Class B amplifier is located at which portion in the load line. What is its maximum efficiency? [3M]
- g What do you mean by Thermal runaway? [2M]
- h List out the advantages of self-biasing circuit? [3M]
- i Draw the drain characteristics of JFET [2M]
- j Mention three different regions of operation of MOSFET. In which region MOSFET acts as resistor? [3M]

PART-B (50 MARKS)**SECTION-I**


- 2 Construct a PN-junction diode and illustrate the formation of the depletion region in a p-n junction. How does the width of this region change when the junction is: (i) Forward biased (ii) Reverse biased. At the temperature of 27°C, calculate the thermal voltage. [10M]

OR

- 3 Define static and dynamic resistance of a junction diode. Derive an expression for dynamic resistance. [10M]

SECTION-II

- 4 [10M]

 Consider the diode circuit shown in Fig. Sketch V_o if $V_i = 40 \sin \omega t$.

Indicate all voltage levels. Assume that all diodes are ideal.

OR

- 5 Explain the working principle and operation of centre tapped transformer based full wave rectifier. [10M]

SECTION-III

- 6 Draw and explain input and output characteristics of an NPN transistor in CE configuration. Suppose the base current is $100\mu\text{A}$ and I_{CO} is 0.5mA . Calculate the collector and emitter currents for CE configuration. Assume $\alpha=0.9$. [10M]

OR


- 7 Develop hybrid model for transistor in CE configuration. [10M]

SECTION-IV

- 8 Derive the expressions for operating point and stability factor of voltage divider bias method. [10M]

OR

 - 9 For the amplifier shown in the Figure below, assume $h_{ie} = 1\text{K}\Omega$ and $h_{fe} = 100$. Also $h_{oe} = h_{re} = 0$. Find A_v , A_{vS} , R_i and R_o . Assume all capacitors to be short circuit. [10M]



to be short circuit.

SECTION-V

- 10 Explain the operation of N-channel enhancement MOSFET and draw its I_D - V_{DS} characteristics. [10M]

OR

- 11 Explain the transfer and drain characteristics of Junction Field Effect Transistor. [10M]
