

Code No: R18A0271

**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY**

(Autonomous Institution – UGC, Govt. of India)

**II B.Tech I Semester Supplementary Examinations, April 2023****Network Analysis & Transmission Lines****(ECE)**

<b>Roll No</b>									
----------------	--	--	--	--	--	--	--	--	--

**Time: 3 hours****Max. Marks: 70**

**Note:** This question paper Consists of 5 Sections. Answer **FIVE** Questions, Choosing ONE Question from each SECTION and each Question carries 14 marks

\*\*\*

**SECTION-I**

- 1 Determine the steady state current for RC series network when connected to voltage source  $V_m \sin \omega t$ . [14M]

OR

- 2 Define the terms natural response and time constant? Derive the step response of a series RLC circuit? [14M]

**SECTION-II**

- 3 Explain 'Z' and 'Y' parameters and also derive the relation between them. [14M]

OR

- 4 Define ABCD parameters for typical four terminal networks. Derive the relationship between ABCD parameters and Y parameters of a two port network [14M]

**SECTION-III**

- 5 Draw the locus diagrams for RL, RC series circuit by varying 'R' [14M]

OR

- 6 A Series RLC circuit has  $R=3\Omega$ ,  $L=3\text{mH}$  and  $C=15\ \mu\text{F}$ . Calculate the Resonant Frequency, Bandwidth, Quality factor and Half power frequencies. [14M]

**SECTION-IV**

- 7 A transmission line operating at 500 MHz has  $Z_0=80\Omega$ ,  $\alpha=0.04\text{ Np/m}$ ,  $\beta=1.5\text{ rad/m}$ . Find the line parameters R, L, G and C? [14M]

OR

- 8 Explain the distortion in a transmission line in detail and also derive the conditions that characterize a distortion less transmission line. [14M]

**SECTION-V**

- 9 Define and discuss input impedance of a loss less transmission line. [14M]

OR

- 10 A loss less line of  $300\Omega$  impedance is terminated to load impedance of  $100+j650\Omega$ . The frequency of operation is 60MHz. Find the length and location of a single stub matching needed for impedance match [14M]

\*\*\*