

Code No: R18A0404**MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****II B.Tech I Semester Supplementary Examinations, April 2023****Switching Theory & Logic Design****(ECE)**

Roll No									
----------------	--	--	--	--	--	--	--	--	--

Time: 3 hours**Max. Marks: 70**

Note: This question paper Consists of 5 Sections. Answer **FIVE** Questions, Choosing ONE Question from each SECTION and each Question carries 14 marks.

SECTION-I

- 1 **A** Perform the following addition using 2's complement of 386+756 [4M]
 B Given the 8bit data word 01010011, generate the 12 bit composite word for the hamming code that corrects and detects single errors [10M]

OR

- 2 **A** Convert the given expression in standard SOP form $f(A,B,C)=AC+BA+BC$ [7M]
 B What is the difference between canonical form and standard form? Explain [7M]

SECTION-II

- 3 **A** Simplify the following Boolean expressions using K-map and implement it by using NAND gates. [7M]
 $F(A,B,C,D)=AB'C' + AC+A'CD'$
 B Simplify the following Boolean expressions using K-map and implement it by using NAND gates. [7M]
 $F(W,X,Y,Z)=w' x'y'z' + wxy'z' + w'x'yz + wxyz$

OR

- 4 **A** Design BCD to gray code converter and realize using logic gates. [7M]
 B Design and implement a two bit comparator using logic gates. [7M]

SECTION-III

- 5 **A** Draw the logic diagram of a JK flip-flop and using excitation table explain its operation [7M]
 B Convert D flip-flop into JK flip-flops. [7M]

OR

- 6 **A** Draw the logic diagram of a SR latch using NOR gates. Explain its Operation using excitation table. [7M]
 B Explain the working of JK Flipflop. What is race around condition? How is it overcome? [7M]

SECTION-IV

- 7 **A** What is a Universal shift register and explain the operation with neat sketch. [7M]
 B Explain how a shift register is used as a converter from i) serial to parallel data and ii) parallel to serial data [7M]

OR

- 8 **A** How does ripple counter differ from synchronous counter? [7M]
 B Design Mod-10 Asynchronous counter. [7M]

SECTION-V

- 9 A** Convert the following Mealy machine into equivalent Moore machine. Draw the state transition diagrams for both. **[8M]**

P.S	N.S			
	A		B	
	state	o/p	state	o/p
Q1	Q1	1	Q2	0
Q2	Q4	1	Q4	1
Q3	Q2	1	Q3	1
Q4	Q3	0	Q1	1

- B** Compare Mealy and Moore Machines **[6M]**

OR

- 10 A** Explain about state diagrams & state tables **[7M]**
B With the help of State table and State diagram explain the operation of Sequence generator. **[7M]**
