

**Code No: R15A0408****MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY****(Autonomous Institution – UGC, Govt. of India)****III B.Tech I Semester Supplementary Examinations, April 2023****IC Applications****(ECE)**

<b>Roll No</b>									
----------------	--	--	--	--	--	--	--	--	--

**Time: 3 hours****Max. Marks: 75****Note:** This question paper contains two parts A and B

Part A is compulsory which carries 25 marks and Answer all questions.

Part B Consists of 5 SECTIONS (One SECTION for each UNIT). Answer FIVE Questions, Choosing ONE Question from each SECTION and each Question carries 10 marks.

\*\*\*

**PART-A (25 Marks)**

- 1). a What is CMRR? [2M]
- b Write the DC characteristics of Op-Amp [3M]
- c What are the advantages of Active filter over passive filters? [2M]
- d Find the frequency response of first order low-pass Butterworth filter? [3M]
- e Define resolution of a converter [2M]
- f Define Stability of a converter [3M]
- g Write the specifications of combinational logic ICs [2M]
- h What is the importance of selection lines in multiplexer? [3M]
- i What is meant by dynamic RAM? [2M]
- j What are the applications of flash ROM? [3M]

**PART-B (50 MARKS)****SECTION-I**

- 2 How an Op-Amp is used as Inverting and Non-inverting amplifier? [10M]  
Explain

OR

- 3 Derive the output response of instrumentation amplifier using 1&2 Op-amp [10M]

**SECTION-II**

- 4 Determine the output frequency response of narrow band pass filter? [10M]

OR

- 5 Draw and explain the block diagram of Phase Locked Loop. [10M]

**SECTION-III**

- 6 Illustrate the operation of binary weighted DAC with suitable diagrams. [10M]

OR

- 7 Explain the operation of dual slope ADC with suitable diagrams. [10M]

**SECTION-IV**

- 8 Demonstrate the operation of encoder with the help of ICs. [10M]

OR

- 9 Explain the operation of TTL and Write the applications of TTL. [10M]

**SECTION-V**

- 10 Describe the operation of ring counter and explain the operation in detail. [10M]

OR

- 11 Give the architectural details of RAM and explain. [10M]

\*\*\*\*\*

