

Code No: **R18A0409****MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY**

(Autonomous Institution – UGC, Govt. of India)

III B.Tech I Semester Supplementary Examinations, April 2023**Linear & Digital IC****(EEE & ECE)**

Roll No									
----------------	--	--	--	--	--	--	--	--	--

Time: 3 hours**Max. Marks: 70**

Note: This question paper Consists of 5 Sections. Answer **FIVE** Questions, Choosing ONE Question from each SECTION and each Question carries 14 marks.

SECTION-I

1 **A** What are characteristics of ideal Op-Amp? Draw the equivalent circuit of ideal Op-amp. **[7M]**

B Explain the DC characteristics of Op-Amp. **[7M]**

OR

2 **A** Draw the inverting amplifier and find its gain. Design an amplifier with gain of -10 and input resistance of 20K Ω . **[7M]**

B Derive the output voltage of a Differential amplifier. **[7M]**

SECTION-II

3 **A** What are the characteristics of bandpass and band reject filters? **[7M]**

B Draw the first order Butterworth LPF and find its Transfer function. **[7M]**

OR

4 **A** Draw the block schematic of PLL and describe each block in detail. **[9M]**

B List the applications of PLL. **[5M]**

SECTION-III

5 **A** Explain the basic DAC technique. Calculate the values of the LSB, MSB and full scale output of an 8 bit DAC for the 0 to 10V range. **[7M]**

B Illustrate the functioning of Weighted resistor DAC. **[7M]**

OR

6 **A** What are the specifications of ADC's? Explain any two. **[6M]**

B Describe the working principle of successive approximation type ADC with an example. **[8M]**

SECTION-IV

7 **A** Explain about the classification of Integrated circuits. **[7M]**

B Make differences between two major logic families CMOS and TTL. **[7M]**

OR

8 **A** Design 4 bit Binary to Grey code converter **[7M]**

B Draw and explain 3 to 8 line decoder **[7M]**

SECTION-V

9 **A** Draw the JK flip-flop and explain its operation with truth table. **[7M]**

B What is the shift register? What are the different kinds of shift Register? List the applications. **[7M]**

OR

10 **A** Design a 3 bit Synchronous counter and explain its operation. **[7M]**

B Describe the RAM Architecture and its functioning. **[7M]**
