

MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY
(Autonomous Institution – UGC, Govt. of India)

UG Model question paper-I
ELECTRICAL CIRCUIT ANALYSIS
EEEII YEARI SEMESER

Time: 3 hours


Max Marks: 70

Note: This question paper contains of 5 sections. Answer five questions, choosing onequestion from each section and each question carries 14 marks.

5*14=70M

SECTION-I

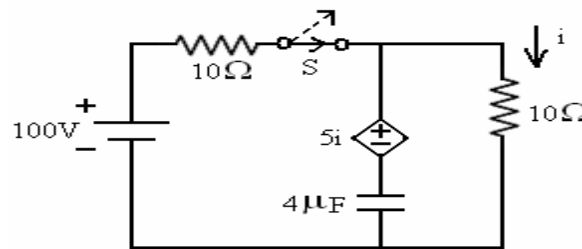1. a) For the circuit shown below Figure, find the current equation when switch S is opened at $t = 0$. [7M]




b) Explain the DC response of series R-C circuit with neat waveforms. [7M]


(OR)

2. a) In the given circuit the switch is opened at $t=0$. Find [7M]

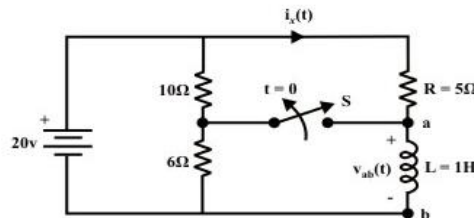- (i) $V_{ab}(0^-)$
- (ii) $i_x(0^-)$
- (iii) $i_x(0^+)$
- (iv) $V_{ab}(0^+)$
- (v) $i_x(t=\infty)$
- (vi) $i_x(t)$ for $t > 0$.



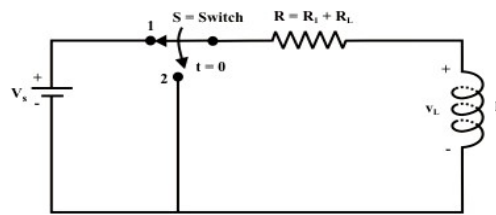b) In the given circuit the switch is shifted from position 1 to 2 at $t=0$. Determine $i(t)$ for $t > 0$. [7M]



SECTION-II

3. Explain the transient response in time domain with sinusoidal excitation as input for a RC circuit. Draw the voltage waveform across R and C. [14M]

(OR)

4. Explain the transient response in time domain with sinusoidal excitation as input for a RL circuit. Draw the voltage waveform across R and L. [14M]

SECTION-III


5. a) A balanced delta-connected load has a phase current $I_{AC} = 10 \angle -30^\circ$ A. [7M]

i) Determine the three line currents assuming that the circuit operates in the positive phase sequence.

ii) Calculate the load impedance if the line voltage is $V_{AB} = 110 \angle 0^\circ$ V.

b) A balanced star-connected load absorbs a total power of 5 KW at a leading power factor of 0.6 when connected to a line voltage of 240 V. Find the impedance of each phase and total complex power of load. [7M]

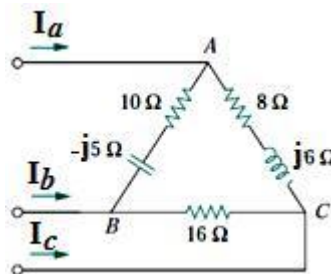6.a) The unbalanced load as shown in Figure 4 below is supplied by balanced voltages of 200V in the positive sequence. Find the line currents. Take V_{ab} as reference. [7M]



b) Prove that two watt-meters are sufficient to measure power in three phase system. [7M]

SECTION-IV


7. Explain about Series Resonance in detail along with quality factor and band width. [14M]

(OR)

8. Draw the locus diagram of series R-L circuit and R-C circuit when R is variable.[14M]

SECTION-V

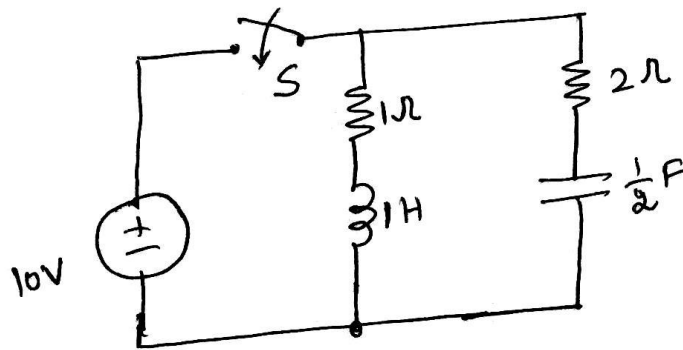9. For the network shown below figure, 'S' is switched on at $t=0$. Find the driving point impedance and source current in s-domain.[14M]



(OR)

10. a) List the necessary conditions for transfer functions.[7M]

b) Find the pole zero locations of the current transfer ratio I_2 / I_1 in s- domain for circuit [7M]

MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY

(Autonomous Institution – UGC, Govt. of India)

UG Model question paper-II

ELECTRICAL CIRCUIT ANALYSIS

EEE II YEAR I SEMESER

Time: 3 hours


Max Marks: 70

Note: This question paper contains of 5 sections. Answer five questions, choosing one question from each section and each question carries 14 marks.

5*14=70M

SECTION-I

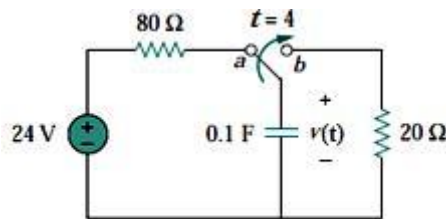
1. a) The switch in the figure has been in position *a* for a long time, At $t = 4$ s the switch is moved to position *b* and left there. Determine $v(t)$ at $t = 10$ s. [7M]



- b) The switch in Figure was open for a long time but closed at $t = 0$. Determine:


- (i) $i(0+)$, $v(0+)$,
 (ii) $i(\infty)$, $v(\infty)$.

[7M]

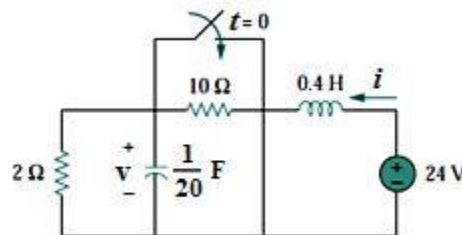


(OR)

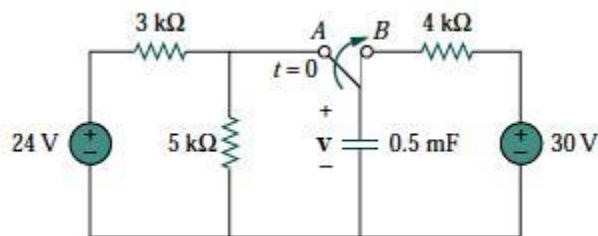- 2.a) The switch in figure has been in position A for a long time. At $t = 0$, the switch moves to B. Determine $V(t)$ for $t > 0$ and calculate its value at $t = 1$ s and 4 s. [7M]



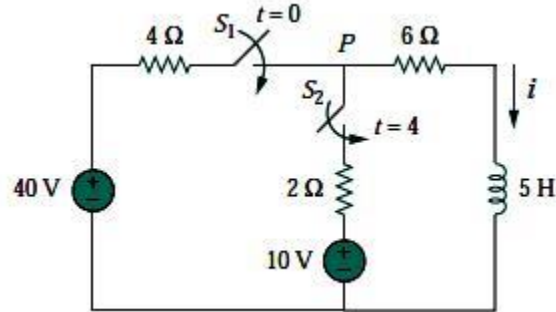- b) At $t = 0$, switch 1 in Figure 8 is closed, and switch 2 is closed 4 s later. Find $i(t)$ for $t > 0$. Calculate i for $t = 2$ s and $t = 5$ s. [7M]



SECTION-II

3. Derive the expression for the current in a series RL circuit ($R = 10\Omega$, $L = 10$ mH) excited by a sinusoidal voltage of 100V, 50 Hz if the supply is connected at $t = 0$. Assume zero initial conditions. [14M]

(OR)

4. Derive the expression for the voltage across the capacitor in a series RLC circuit ($R = 5\Omega$, $L = 5$ mH, $C = 5\mu\text{F}$) excited by a sinusoidal voltage of 100V, 50 Hz if the supply is connected at $t = 0$. Assume zero initial conditions. [14M]

SECTION-III

- 5.a) Three impedances each of $(10+j3)$ ohms are connected in star to a 220 V, 3-phase, 50 Hz supply. Calculate the line currents and power delivered to the load. [7M]

- b) Derive the relation between phase and line values of a 3-phase balanced delta connected system. [7M]

(OR)

- 6.a) Explain the measurement of power in a balanced 3-phase system using a single watt meter. [7M]

- b) Three coils each having a resistance of 50Ω and an inductive reactance of 45Ω are connected in star and fed by a 3-phase, 400 V, 50 Hz system. Find

- i) Line current
- ii) Power
- iii) Power factor

[7M]

SECTION-IV

7. Explain about Parallel Resonance in detail along with quality factor and band width. [14M]


(OR)

8. Draw and explain about the locus diagram of parallel R-C circuit and R-L circuit when R is variable. [14M]

SECTION-V


9. a) Explain the concept of Complex Frequency.[7M]

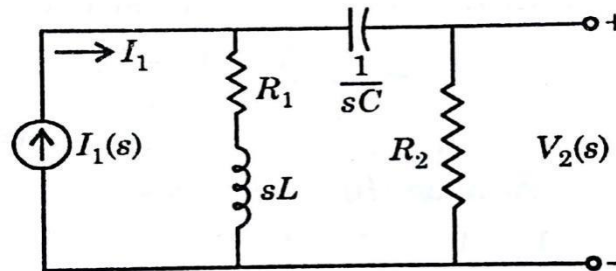b) Find the Transfer Impedance function for the network given below.[7M]



(OR)

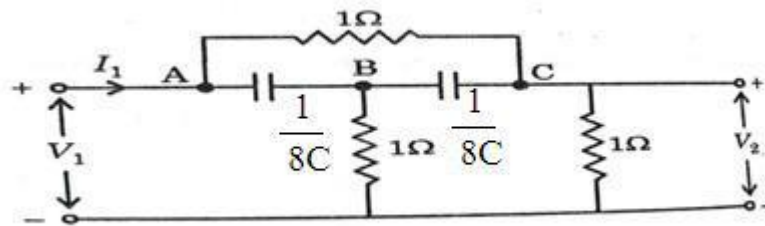10) Find the Driving Point Impedance, Transfer Impedance and Voltage Transfer Function for the circuit given below. [14M]



MALLA REDDY COLLEGE OF ENGINEERING & TECHNOLOGY
 (Autonomous Institution – UGC, Govt. of India)

UG Model question paper-III
ELECTRICAL CIRCUIT ANALYSIS
EEE II YEAR I SEMESER

Time: 3 hours

Max Marks: 70


Note: This question paper contains of 5 sections. Answer five questions, choosing one question from each section and each question carries 14 marks.

5*14=70M


SECTION-I

1 a) In the circuit shown figure, the capacitor voltage just before $t = 0$ is

[7M]

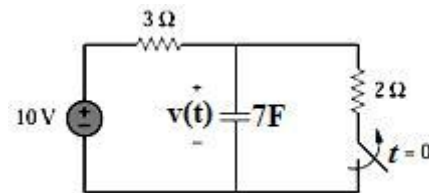

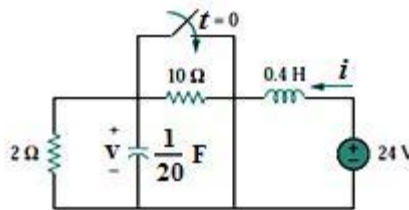
b) The switch in the figure 3 has been open for a long time. It is open at $t = 0$, the value of $v(\infty)$.



(OR)

2. a) Deduce the transient response of RL series circuit excited by DC source. [7M]

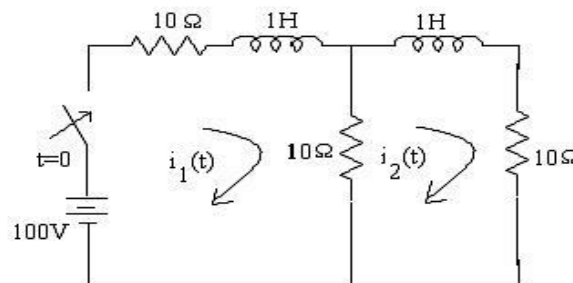b) In the network shown in the figure below, the switch is closed at $t = 0$. Find the values of $i_1(t)$ and $i_2(t)$ assuming zero initial currents through inductors. [7M]



SECTION-II

3. What is damping ratio? Derive the time constant for a parallel RC circuit excited by AC supply. [14M]


(OR)

4. What is the condition for the response of a series RLC circuit excited by DC supply to have critically damped response? [14M]

SECTION-III

5. a) Two watt meters connected to a 3-phase motor indicate the total power input to be 12 kW. The power factor is 0.6. Determine the readings of each wattmeter. [7M]

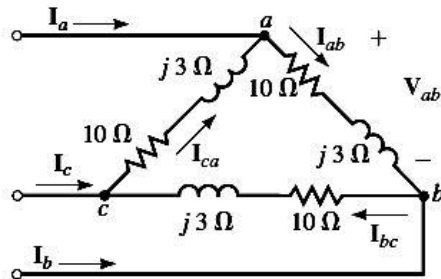b) If $V_{ab} = 240 \text{ V} \angle 15^\circ$ for the circuit shown figure 1 below, what is the value of I_{ab} . [7M]



(OR)

6. a) Explain about three phase system? List out the merits of three phase system. [7M]

b) Three coils, each having resistance of 25Ω and inductive reactance of 10Ω are connected in Star to a 400V, 3-phase, 50Hz AC supply. Calculate the power supplied. [7M]

SECTION-IV


7. Explain about Series and Parallel Resonance in detail along with quality factor and bandwidth. [14M]

(OR)

8. Draw and explain about the locus diagram of Series R-C circuit and R-L circuit when X_L is variable. [14M]

SECTION-V

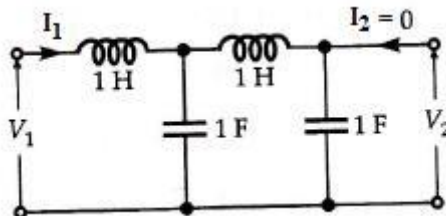9. What is the driving point and transfer impedance of the network shown figure below? [14M]



(OR)

10. Find the expression for voltage transformation ratio for the network shown in figure [14M]

