

ELECTRICAL AND ELECTRONICS ENGINEERING

LABORATORY MANUAL

(FOR MECH& ANE)



DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

MALLA REDDY COLLEGE OF ENGINEERING AND TECHNOLOGY

(Sponsored by CMR Educational Society)

(Affiliated to JNTU, Hyderabad)

Secunderabad-14.

ELECTRONICS & COMMUNICATION ENGINEERING**VISION**

To evolve into a center of excellence in Engineering Technology through creative and innovative practices in teaching-learning, promoting academic achievement & research excellence to produce internationally accepted competitive and world class professionals.

MISSION

To provide high quality academic programmes, training activities, research facilities and opportunities supported by continuous industry institute interaction aimed at employability, entrepreneurship, leadership and research aptitude among students.

QUALITY POLICY

- ❖ Impart up-to-date knowledge to the students in Electronics & Communication area to make them quality engineers.
- ❖ Make the students experience the applications on quality equipment and tools.
- ❖ Provide systems, resources and training opportunities to achieve continuous improvement.
- ❖ Maintain global standards in education, training and services.

PROGRAMME EDUCATIONAL OBJECTIVES (PEOs)

PEO1: PROFESSIONALISM & CITIZENSHIP

To create and sustain a community of learning in which students acquire knowledge and learn to apply it professionally with due consideration for ethical, ecological and economic issues.

PEO2: TECHNICAL ACCOMPLISHMENTS

To provide knowledge based services to satisfy the needs of society and the industry by providing hands on experience in various technologies in core field.

PEO3: INVENTION, INNOVATION AND CREATIVITY

To make the students to design, experiment, analyze, interpret in the core field with the help of other multi disciplinary concepts wherever applicable.

PEO4: PROFESSIONAL DEVELOPMENT

To educate the students to disseminate research findings with good soft skills and become a successful entrepreneur.

PEO5: HUMAN RESOURCE DEVELOPMENT

To graduate the students in building national capabilities in technology, education and research.

PROGRAMME SPECIFIC OBJECTIVES (PSOs)

PSO1

To develop a student community who acquire knowledge by ethical learning and fulfill the societal and industry needs in various technologies of core field.

PSO2

To nurture the students in designing, analyzing and interpreting required in research and development with exposure in multi disciplinary technologies in order to mould them as successful industry ready engineers/entrepreneurs

PSO3

To empower students with all round capabilities who will be useful in making nation strong in technology, education and research domains.

PROGRAM OUTCOMES (POs)

Engineering Graduates will be able to:

1. **Engineering knowledge:** Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
2. **Problem analysis:** Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
3. **Design / development of solutions:** Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
4. **Conduct investigations of complex problems:** Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
5. **Modern tool usage:** Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.
6. **The engineer and society:** Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
7. **Environment and sustainability:** Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
8. **Ethics:** Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
9. **Individual and team work:** Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.
10. **Communication:** Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
11. **Project management and finance:** Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multi disciplinary environments.
12. **Life- long learning:** Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

Laboratory Rules

General Rules of Conduct in Laboratories:

1. You are expected to arrive on time and not depart before the end of a laboratory.
2. You must not enter a lab unless you have permission from a technician or lecturer.
3. You are expected to comply with instructions, written or oral, that the laboratory Instructor gives you during the laboratory session.
4. You should behave in an orderly fashion always in the lab.
5. You must not stand on the stools or benches in the laboratory.
6. Keep the workbench tidy and do not place coats and bags on the benches.
7. You must ensure that at the end of the laboratory session all equipment used is stored away where you found it.
8. You must put all rubbish such as paper outside in the corridor bins. Broken components should be returned to the lab technician for safe disposal.
9. You must not remove test equipment, test leads or power cables from any lab without permission.
10. Eating, smoking and drinking in the laboratories are forbidden.
11. The use of mobile phones during laboratory sessions is forbidden.
12. The use of email or messaging software for personal communications during laboratory sessions is forbidden.
13. Playing computer games in laboratories is forbidden.

Specific Safety Rules for Laboratories:

1. You must not damage or tamper with the equipment or leads.
2. You should inspect laboratory equipment for visible damage before using it. If there is a problem with a piece of equipment, report it to the technician or lecturer. DO NOT return equipment to a storage area
3. You should not work on circuits where the supply voltage exceeds 40 volts without very specific approval from your lab supervisor. If you need to work on such circuits, you should contact your supervisor for approval and instruction on how to do this safely before commencing the work.
4. Always use an appropriate stand for holding your soldering iron.
5. Turn off your soldering iron if it is unlikely to be used for more than 10 minutes.
6. Never leave a hot soldering iron unattended.
7. Never touch a soldering iron element or bit unless the iron has been disconnected from the mains and has had adequate time to cool down.
8. Never strip insulation from a wire with your teeth or a knife, always use an appropriate wire stripping tool.
9. Shield wire with your hands when cutting it with a pliers to prevent bits of wire flying about the bench.

LIST OF EXPERIMENTS**SECTION-A: ELECTRICAL ENGINEERING**

S.NO	EXPERIMENT NAME	PAGE NO
1.	MAGNETISATION CHARACTERISTICS OF D.C SHUNT GENERATOR	8-11
2.	SPEED CONTROL OF D.C SHUNT MOTOR	12-15
3.	SWINBURNE'S TEST ON D.C SHUNT MACHINE	16-20
4.	BRAKE TEST ON D.C SHUNT MOTOR	21-24
5.	OC & SC TEST ON 1-PHASE TRANSFORMER	25-31
6.	BRAKE TEST ON 3-PHASE INDUCTION MOTOR	32-35
7.	REGULATION OF ALTERNATOR BY SYNCHRONOUS IMPEDANCE METHOD	36-39

INTRODUCTION TO ELECTRONIC DEVICES

S.NO	DEVICE NAME	PAGE NO
1.	BASIC ELECTRONIC COMPONENTS	41-45
2.	CIRCUIT SYMBOLS	46-53
3.	STUDY OF CRO	54-57
4.	STUDY OF FUNCTION GENERATOR	58-60
5.	STUDY OF REGULATED POWER SUPPLY	61-61
6.	TYPES OF CIRCUIT BOARD	62-63

SECTION-B: ELECTRONICS ENGINEERING

S.NO	EXPERIMENT NAME	PAGE NO
1.	PN JUNCTION DIODE CHARACTERISTICS	65-68
2.	ZENER DIODE CHARACTERISTICS	69-73
3.	HALF WAVE RECTIFIER WITH AND WITHOUT FILTER	74-78
4.	FULL WAVE RECTIFIER WITH AND WITHOUT FILTER	79-83
5.	TRANSISTOR CB CHARACTERISTICS (INPUT AND OUTPUT)	84-87
6.	TRANSISTOR CE CHARACTERISTICS (INPUT AND OUTPUT)	88-91

SECTION-A

1. MAGNETIZATION or OPEN CIRCUIT CHARACTERISTICS OF D.C SHUNT GENERATOR

AIM:

To obtain the no load characteristics of a DC shunt generator and to determine the critical field resistance.


NAME PLATE DETAILS:

S.NO	Characteristics	D.C Motor	D.C Generator
1	Voltage	220V	220V
2	Current	13.6A	20A
3	Speed	1500rpm	1500rpm
4	Power	5HP	3KW

APPARATUS:

S.NO	Name Of The Equipment	Type	Range	Quantity
1	Voltmeters	MC	0-300V	2NO
2	Ammeters	MC	0-2A	1NO
3	Rheostats	WW	370 Ω /2A	2NO
4	Tachometers	Digital	0-10000rpm	1NO

CIRCUIT DIAGRAM:

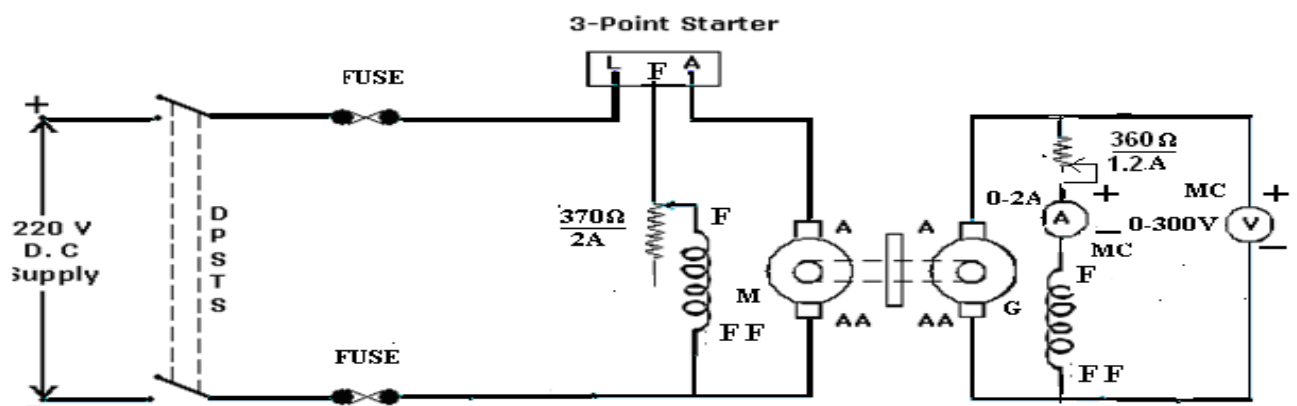

THEORY:

Magnetization curve is relation between the magnetizing forces and the flux density B . this is also expressed as a relation between the field current and the induced e.m.f, in a D.C machine. Varying the field current and noting corresponding values of induced e.m.f can determine this.

For a self-excited machine the theoretical shape of the magnetization Curve is as shown in the figure. The induced e.m.f corresponding to residual magnetism exists when the field current is zero. Hence the curve starts, a little above the origin on y-axis. The field resistance line R_{sh} is a straight-line passing through the origin.

If field resistance is increased so much that the resistance line does not cut the OCC at all then obviously the machine will fail to excite. If the resistance line just lies along the slope, then machine will just excite. The value of the resistance represented by the tangent to the curve is known as critical field resistance R_c for a given speed.

CRITICAL FIELD RESISTANCE: it is the resistance of the field winding of the generator below which generator fail to build up the voltage.

First OCC is plotted from the the readings then tangent is drawn to its initial position. The slope of this curve gives the critical field resistance.

From the graph the critical field resistance $R_c = AB/BC$.

PROCEDURE:


1. Connect the circuit as per the circuit diagram shown in fig.
2. Keep the motor field rheostat R_{sh} at minimum position and generator field rheostat at maximum position.
3. Check that the belt on the pulley is free so that there is no load on the pulley.
4. Switch on the DPST switch. Start the motor slowly by using starter.
5. Adjust the current so that the motor runs at its rated speed.
6. Now vary the generator field rheostat to increase the field current and take the no load voltage and field current readings.
7. Take the no load voltage values until field gets saturated.
8. Finally set the field rheostats to initial positions then switch off the supply.
9. Draw the graph between generated voltage and field current. Find the critical field resistance from the tangent line.

TABULAR COLUMN:

Residual Voltage =		Speed=
SNO	$I_f(A)$	$E_g(V)$

MODEL GRAPH:

Draw the graph between generated voltage at no load and field current. By taking Generated voltage E_g in volts on Y axis and field current I_f in amps on X-axis.

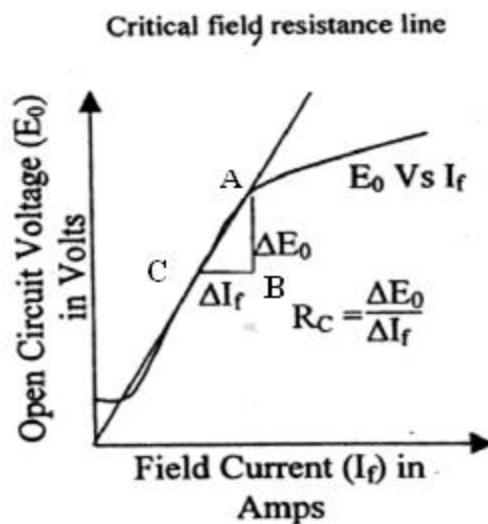**PRECAUTIONS:**

- 1) The rheostat is connected such that minimum resistance is included in field circuit of motor.
- 2) The rheostat is connected such that maximum resistance is included in field circuit of generator.
- 3) Starter handle is moved slowly.

RESULT:

EXERCISE QUESTIONS:

1. The **magnetization** curve of a d.c. shunt generator running at 1000 r.p.m. is as follows :

Field Amperes : (A)	0.25	0.5	1.0	1.5	2.0	2.5	3.0
E.M.F. Volts : (V)	36.0	72.0	138.0	188.0	225.0	250.0	270.0

Find (i) the value of field resistance to give 240 V on no load (ii) The speed at which the generator just fails to build up.

VIVA QUESTIONS:

1. What is meant by critical field resistance?
2. Residual magnetism is necessary for self excited generators or not.
3. Why this test is conducted at constant speed?

5. SPEED CONTROL OF DC SHUNT MOTOR

AIM:

To control the speed of a DC shunt motor using the following methods

- i). field flux control
- ii). Armature voltage control


NAME PLATE DETAILS:

CHARECTERISTIC	RATING
Voltage	220V
Speed	1500rpm
current	1.2A

APPARATUS:

S.No	NAME OF THE EQUIPMENT	Type	Range	Qty
1	DC shunt motor	DC	220V	1
2	Rheostat	Wire wound	370Ω/2.5A	2
3	Ammeter	MC	(0-2)A	1
4	Voltmeter	MC	(0-220)V	1
5	Tachometer	Digital	(0-30000)rpm	1

CIRCUIT DIAGRAM:

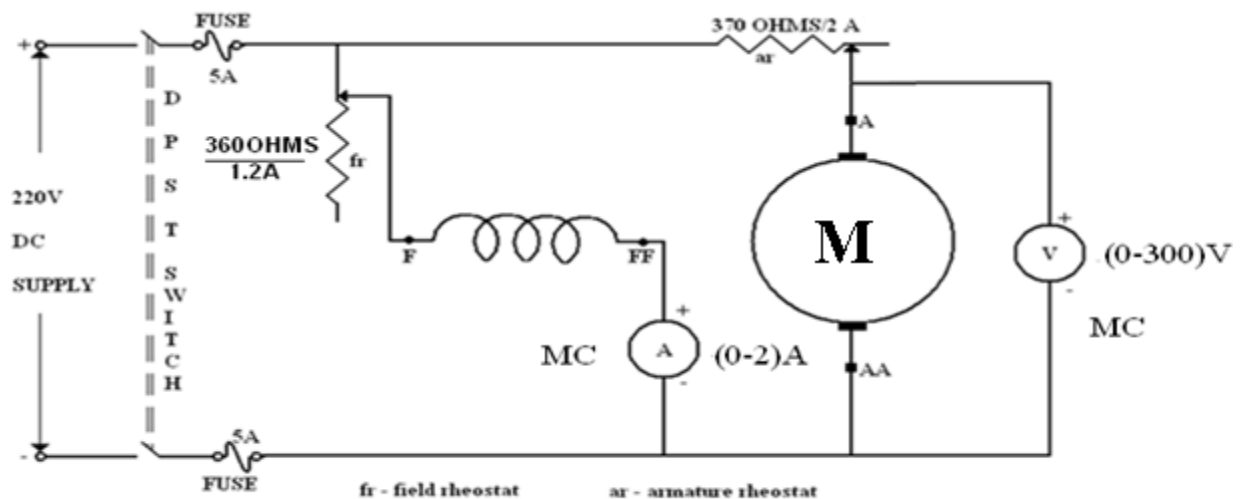

THEORY:

The term speed control means intentional speed variation, carried out manually or automatically. DC motors are most suitable for wide range speed control and are therefore indispensable for many adjustable speed drives. The speed of a motor is given by

$$\omega_m = (V_t - I_a R_a) / K_a \phi$$

Where K_a – armature constant = $PZ/2\pi A$

And ϕ is the flux per pole.

Hence it follows that, for a DC motor, there are basically three methods of speed control and these are:

1. Variation of resistance in armature circuit
2. Variation of the field flux
3. Variation of armature terminal voltage.

Variation of the field flux:

This method of speed control, also called as flux weakening method or field current control method gives speeds above the base speed only. Base speed is nothing but the rated speed of the machine. This is one of the simplest and economical methods and is, therefore extensively used in modern electric drives. Under steady state running conditions, if the field circuit resistance is increased, the field current and hence the field flux are reduced. Since the rotor speed cannot change suddenly due to inertia, a decrease in field current causes a reduction of counter emf. As a result of it, more current flows through armature. The percentage increase in armature current is much more than the percentage decrease in the field current. In view of this, the electromagnetic torque is increased and this being more than the load torque, the motor gets accelerated. The disadvantages of this method are:

- a. The armature may get over heated at higher speeds, because the increased armature current results in more ohmic losses whereas cooling by ventilation does not improve proportionally.
- b. If the field flux is weakened considerably, the speed becomes very high and due to these changes; the motor operation may become unstable.

Variation of armature terminal voltage:

If the voltage applied to the armature changes the speed changes directly with it. Using this method, speeds below rated speeds are attained.

PROCEDURE:

1. Make the connections as per the circuit diagram.
2. Keep the field rheostat in minimum position and armature in maximum position and close the DPST switch.
3. Bring the motor to rated speed using field rheostat.
4. At this point take a note of the voltmeter and tachometer readings.


5. Now start varying the armature rheostat in steps and for each step note down the voltmeter and tachometer readings. Take 10 to 15 such readings and bring back the armature rheostat to initial position.
6. Bring back the field rheostat to initial position. Using the armature rheostat set the motor at rated speed.
7. Vary the field rheostat in steps and for each step note down the ammeter and tachometer readings. Take 10 to 15 such readings.
8. Set both the rheostats to their initial positions and open the DPST switch.


TABULAR COLUMN:**Armature voltage control:**

S.No	Va(Armature Voltage(volts))	N(Speed(rpm))

Field Flux Control:

S.No	If(Field current(amperes))	N (Speed(rpm))

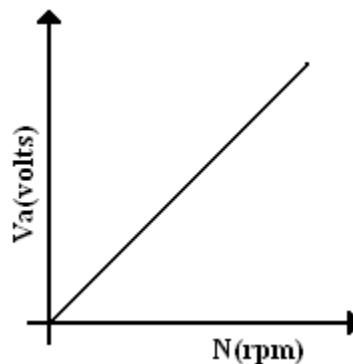MODEL GRAPHS:**Armature Voltage Control:**

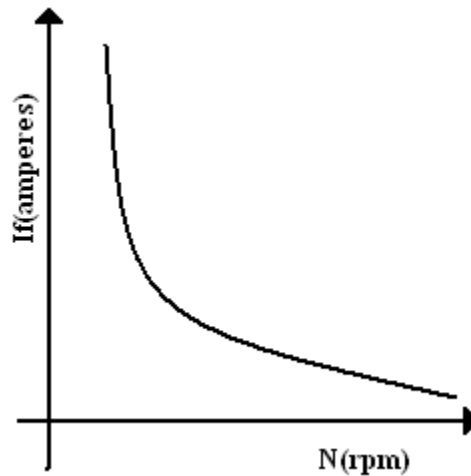Field Flux Control:**PRECAUTIONS:**

1. We should start the motor under no load
2. Take the reading without parallax error.
3. The connections must be tight.

RESULT:**EXERCISE QUESTIONS:**

1. A 500 V shunt motor runs at its normal speed of 250 r.p.m. when the armature current is 200 A. The resistance of armature is 0.12 ohm. Calculate the speed when a resistance is inserted in the field reducing the shunt field to 80% of normal value and the armature current is 100 ampere

VIVA QUESTIONS:

1. What are the three methods of speed control?
2. What is the main purpose of speed control?
3. Why is three point starters not used in this circuit?
4. What is the method opted to get speeds above rated speed?
5. How is flux per pole related to the speed of the machine?

3. SWINBURNE'S TEST ON D.C SHUNT MACHINE

AIM: To perform Swinburne's test on the given D.C machine and predetermine the efficiency at any desired load both as motor and as generator.


NAME PLATE DETAILS:


S.NO	Characteristic	D.C Motor
1	Voltage	220V
2	Current	20A
3	Speed	1500rpm
4	Power	5HP

APPARATUS REQUIRED:

S.NO	Name Of The Equipment	Type	Range	Quantity
1	Ammeter	MC	0-2A,0-1A,0-10A	3NO
2	Voltmeter	MC	0-30V,0-300V	2NO
3	Rheostat	WW	370 Ω /2A	1NO
4	Tachometer	Digital	1000rpm	1NO

CIRCUIT DIAGRAM:

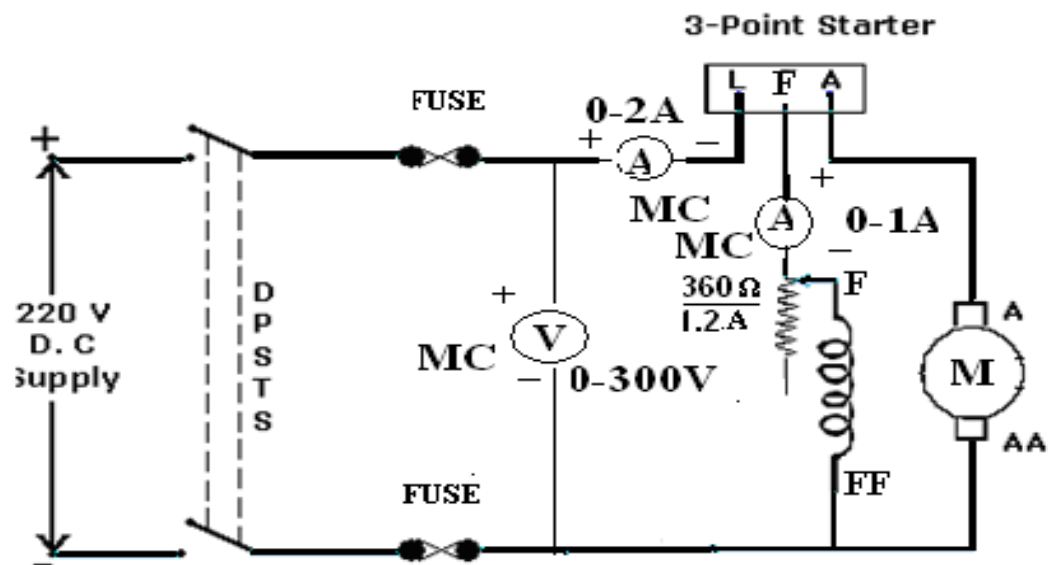

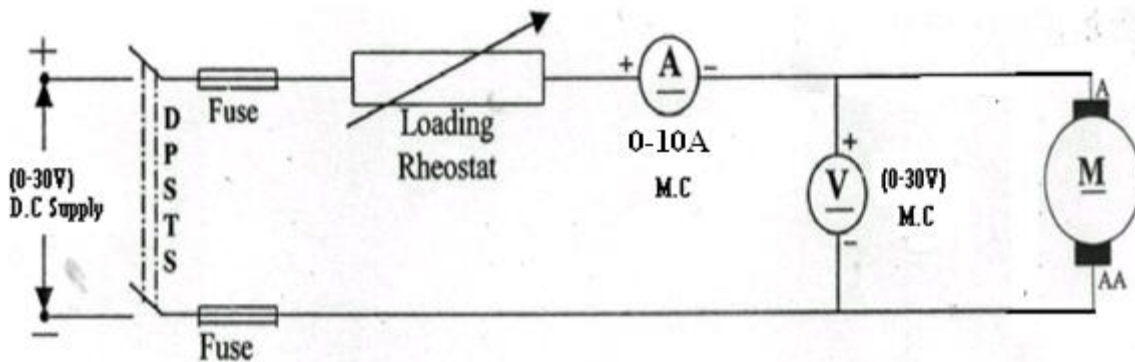CIRCUIT DIAGRAM TO FIND ARMATURE RESISTANCE:**THEORY:**

This test is to find out the efficiency of the machine. It is a simple indirect method in which losses are determined separately and from their knowledge, efficiency at any desired load can be predetermined. The only test needed is no-load test. This test cannot be performed on DC series motor. The machine is run as a no load shunt motor at rated speed and with a rated terminal voltage. However, this test is applicable to those machines in which flux is practically constant.

The constant losses in a dc shunt machine = W_c = stray losses (magnetic & mechanical losses) + shunt field copper losses.

$$\begin{aligned} W_c &= \text{No load input} - \text{No load armature copper losses} \\ &= V I_{L0} - I_{a0}^2 R_a \text{ where } R_a \text{ is the armature resistance} \\ \text{And } I_{a0} &= I_L - I_{sh} \end{aligned}$$

PROCEDURE:

- 1) Make all the connections as per the circuit diagram.
- 2) Keep the field rheostat in **minimum** resistance position.
- 3) Excite the motor with **220V, DC** supply by closing the **DPST** switch and start the Motor by moving the handle of 3-point starter from **OFF** to **ON** position.
- 4) By adjusting the rheostat in motor field bring the speed of the motor to its rated value. Note down the readings of Ammeter and Voltmeter at no load condition.
- 5) The necessary calculations to find efficiency of machine as motor & generator at any given value of armature current is done.

TO FIND ARMATURE RESISTANCE (R_a):

- 1) Connect the circuit per the circuit diagram
- 2) Keep the rheostat in maximum position.
- 3) Now excite the motor terminals by 30V supply by closing DPST switch.
- 4) Note down the readings of Ammeter and voltmeter.

MODEL CALCULATIONS:-**For motor:**

$$I_L = I_a + I_f$$

$$\text{No load losses} = W_o = VI_o - I_{ao}^2 R_a$$

$$\text{Input} = VI$$

$$\text{Cu losses} = I_a^2 R_a$$

$$\text{Total losses} = \text{No load losses} + \text{cu losses}$$

$$\text{Output} = \text{Input} - \text{Total losses}$$

$$\% \text{Efficiency } (\eta) = (\text{Output} / \text{Input}) * 100$$

For generator:

$$I_a = I_L + I_f$$

$$\text{No load losses} = W_o = V I_o - I_{ao}^2 R_a$$

$$\text{Output} = VI$$

$$\text{Cu losses} = I_a^2 R_a$$

$$\text{Total losses} = \text{No load losses} + \text{cu losses}$$

$$\text{Input} = \text{Output} + \text{Total losses}$$

$$\% \text{Efficiency } (\eta) = (\text{Output} / \text{Input}) * 100$$

TABULAR COLOUMN:

S.NO	Voltmeter reading V in Volts	Ammeter Reading I in Amps	Ammeter reading I_{sh} in Amps	Speed in RPM

ARMATURE RESISTANCE (Ra):


S.No	Voltage	Current

CALCULATION TABLE:**As a Motor:**

S.NO	I_L (A)	$I_a = (I_L - I_{sh})$ in A	$W = I_a^2 R_a$ in watts	Total losses	%Efficiency

As a Generator:

S.NO	I_L (A)	$I_a = (I_L + I_{sh})$ in A	$W = I_a^2 R_a$ in watts	Total losses	%Efficiency

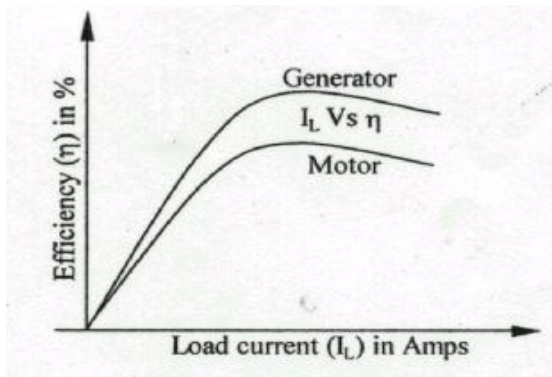MODEL GRAPH:**PRECAUTIONS:**

1. We should start the motor under no load
2. Take the reading without parallax error.
3. The connections must be tight.

RESULT:

EXERCISE QUESTIONS:

1. A 220v dc shunt motor at no load takes a current of 2.5A. The resistances of armature and shunt field are $0.8\ \Omega$ and 200Ω respectively. Estimate the efficiency of the motor when the input current is 20A. State precisely assumptions made

VIVA QUESTIONS:

1. Why the magnetic losses calculated by this method are less than the actual value?
2. Is it applied to D.C series machines?
3. Comment on the efficiency determined by this method.

4. BRAKE TEST ON D.C SHUNT MOTOR

AIM:

To conduct the brake test on a D.C shunt motor and to draw its performance curves.


NAME PLATE DETAILS:

S.NO	Characteristic	D.C Motor
1	Voltage	220V
2	Current	20A
3	Speed	1500rpm
4	Power	5HP

APPARATUS REQUIRED:

S.NO	Description	Type	Range	Quantity
1	Ammeter	MC	0-20A	1NO
2	Voltmeter	MC	0-300V	1NO
3	Rheostat	WW	370 Ω /2A	1NO
4	Tachometer	Digital	0-10000rpm	1NO

CIRCUIT DIAGRAM:

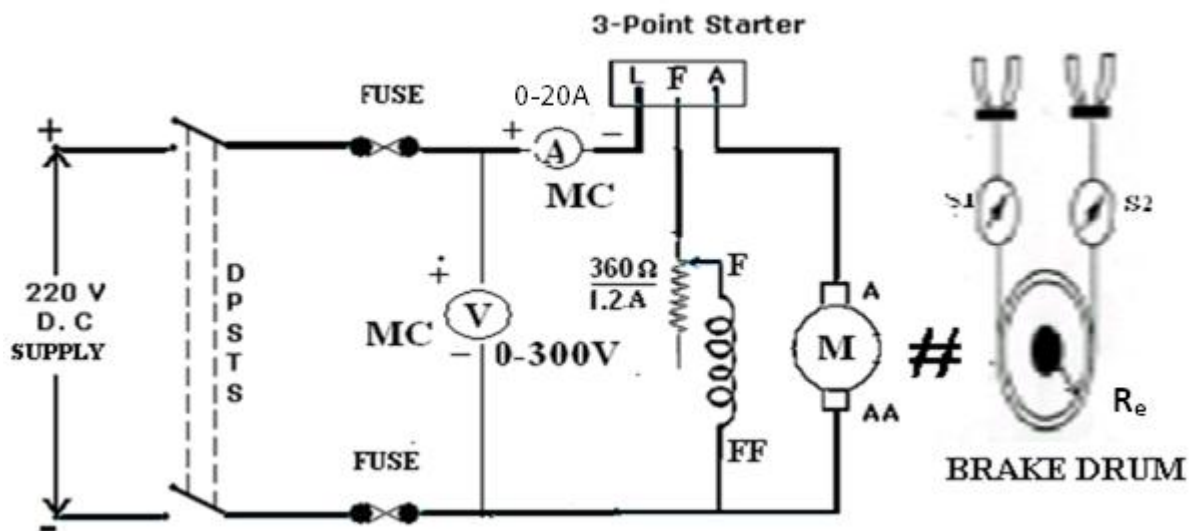

THEORY:

This test is direct test to find the efficiency of the DC shunt motor. In this test the motor directly loaded by connecting brakes which are with pulley and motor is subjected to rated load and entire power is wasted. belt around the water cooled pulley has its ends attached to spring balances S1 and S2. The belt tightening hand wheels h1 and h2 help in adjusting the load on the pulley so that the load on the motor can be varied.

Output power of the motor = $(S1-S2)*Re*9.81*w$ (watts)

S1, S2 = weights on the pulley.

Re= Effective radius of the pulley.

w= motor speed in rad/sec.

If V is the terminal voltage IL is the line current

Power in put = $V*I_L$ watts.

Efficiency ($\% \eta$) = $(w(S1-S2)*Re*9.81/V*I_L)*100$

PROCEDURE:

1. All the connections are as per the circuit diagram.
2. **220V**, DC supply is given to the motor by closing **DPST** switch.
3. Move the 3-point starter handle from '**OFF**' to '**ON**' position slowly and motor starts running.
4. Vary the field rheostat until the motor reaches its rated Speed and take voltmeter and ammeter readings.
5. Apply the load by break drum pulley and for each applications of load the Corresponding Voltmeter (V), Ammeter (I), spring forces S1 & S2 and Speed (N) Readings are noted.
6. Calculate output & efficiency for each reading.
7. Note down all the readings in the tabular form carefully.
8. Remove the load slowly and keep the rheostat as starting position and switch '**OFF**' the supply by using **DPST** switch.

TABULAR COLUMN:


S. NO	Voltage (V)	Current (A)	Input = VI watts	Forces in KG S ₁ S ₂		Net force F = S ₁ ~S ₂ in kg	Torque(T) = F*Re*9.81 (N-M)	Speed in RPM (N)	O/p= 2πNT/60 (Watts)	%Efficiency η=output/input
1										
2										
3										
4										
5										
6										
7										

GRAPH:

The graph is drawn between

- a) Output in Watts Vs Speed(N) in RPM
- b) Output in Watts Vs Torque (T) in N-m
- c) Output in Watts Vs Current (I) in A
- d) Output in Watts Vs Efficiency (%η)

By taking output in Watts on X axis and speed, Torque, current, Efficiency on Y- axis .

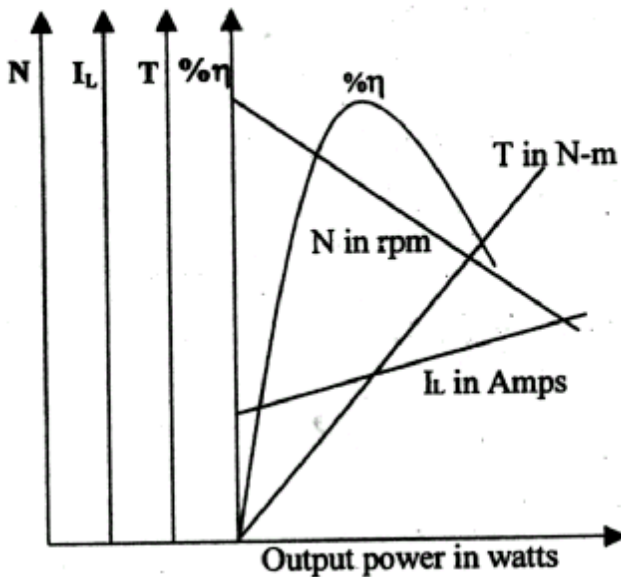Electrical characteristics:

PRECAUTIONS:

1. Initially 3-point starter should be kept at 'OFF' position and later it must be varied slowly and uniformly from 'OFF' to 'ON' position.
2. The field regulator must be kept at its minimum output position.
3. The brake drum of the motor should be filled with cold water.
4. The motor should be started without load.

RESULT:**EXERCISE QUESTIONS:**

1. In a brake test the effective load on the branch pulley was 38.1kg, the effective diameter of the pulley 63.5cm and speed 12 r.p.s. the motor took 49A at 220V. Calculate the output power and the efficiency at this load

VIVA QUESTIONS:

1. Why a 3-point starter is used for starting a D.C shunt motor?
2. If a 3-point starter is not available, how can a D.C motor be started?
3. Explain the function of overload release coil in 3-point starter

5. OC & SC TESTS ON 1 – PHASE TRANSFORMER

AIM:


To conduct Open circuit and Short circuit tests on 1-phase transformer to pre-determine the efficiency, regulation and equivalent parameters.


NAME PLATE DETAILS:

Voltage Ratio	220/110V
Full load Current	13.6A
KVA RATING	3KVA

APPARATUS:

S.NO	Description	Type	Range	Quantity
1	Ammeter	MI	0-20A 0-5A	2NO
2	Voltmeter	MI	0-150V 0-300V	2NO
3	Wattmeter	LPF UPF	2A,150V 20A,300V	2NO
4	Auto transformer	-	230/0-270V	1NO
5	Transformer	-	220V/110V	1NO

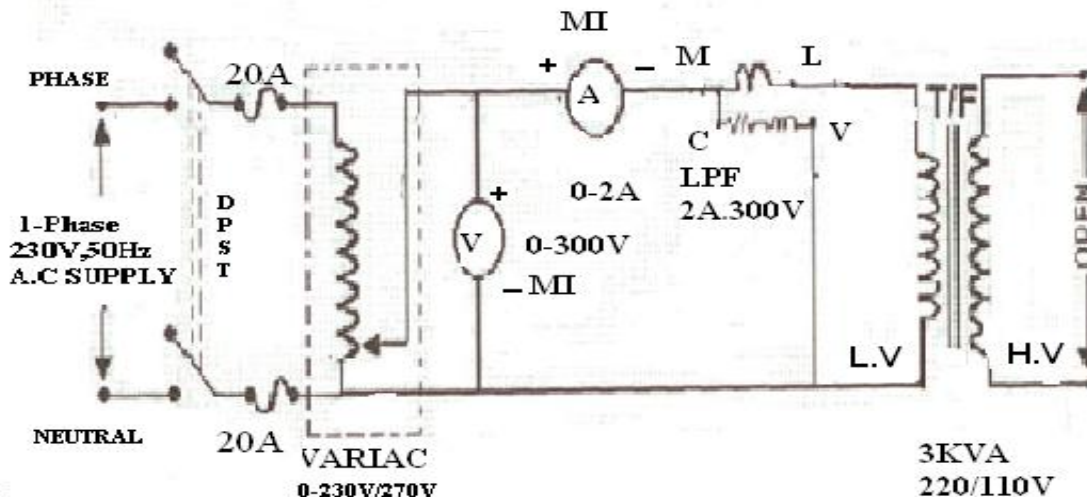CIRCUIT DIAGRAM:**OPEN CIRCUIT TEST:**

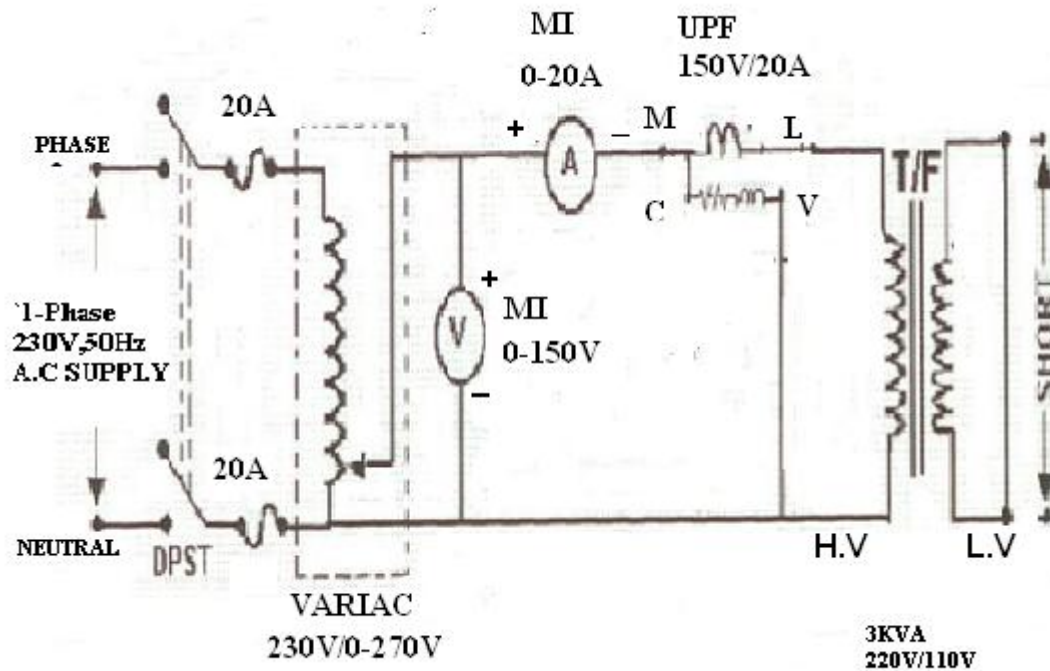SHORT CIRCUIT TEST:**THEORY:**

Transformer is a device which transforms the energy from one circuit to other circuit without change of frequency.

The performance of any transformer calculated by conducting tests .OC and SC tests are conducted on transformer to find the efficiency and regulation of the transformer at any desired power factor.

OC TEST:

The objectives of OC test are

1. To find out the constant losses or iron losses of the transformer.
2. To find out the no load equivalent parameters.

SC TEST:

The objectives of OC test are

1. To find out the variable losses or copper losses of the transformer.
2. To find out the short circuit equivalent parameters.

By calculating the losses and equivalent parameters from the above tests the efficiency and regulation can be calculated at any desired power factor.

PROCEDURE (OC TEST):

1. Connections are made as per the circuit diagram
2. Initially variac should be kept in its minimum position
3. Close the DPST switch.

4. By varying Auto transformer bring the voltage to rated voltage
5. When the voltage in the voltmeter is equal to the rated voltage of HV winding note down all the readings of the meters.
6. After taking all the readings bring the variac to its minimum position
7. Now switch off the supply by opening the DPST switch.

PROCEDURE (SC TEST):

1. Connections are made as per the circuit diagram.
2. Short the LV side and connect the meters on HV side.
3. Before taking the single phase, 230 V, 50 Hz supply the variac should be in minimum position.
4. Now close the DPST switch so that the supply is given to the transformer.
5. By varying the variac when the ammeter shows the rated current (i.e. 13.6A) then note down all the readings.
6. Bring the variac to minimum position after taking the readings and switch off the supply.

O.C TEST OBSERVATIONS:

S.NO	V_0 (VOLTS)	I_0 (AMPS)	W_0 (watts)

S.C TEST OBSERVATIONS:

S.NO	V_{sc} (VOLTS)	I_{sc} (AMPS)	W_{sc} (watts)

CALCULATIONS:**(a) Calculation of Equivalent circuit parameters:**

Let the transformer be the step down transformer.

(i) Parameters calculation from OC test

$$\cos \phi_0 = \frac{W_o}{V_o I_o} =$$

$$I_w = I_0 \cos \phi_0 =$$

$$R_\phi = \frac{V_1}{I_w} =$$

$$I_\mu = I_0 \sin \phi_0 =$$

$$X_\phi = \frac{V_1}{I_\mu} =$$

$$K = \frac{V_2}{V_1} =$$

(ii) Parameters calculation from SC test

$$R_{01} = \frac{W_{SC}}{I_{sc}^2} =$$

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} =$$

$$Z_{01} = \frac{V_{SC}}{I_{SC}} =$$

b) Calculation to find Efficiency

$$\eta = \frac{n \times KVA \times \cos \phi}{n \times KVA \times \cos \phi + n^2 \text{ Cu. Loss} + \text{constant loss}}$$

Where 'n' represents % of full load.

(C) Calculation of Regulation at full load:

$$\% \text{ Regulation} = \frac{I_1 R_{01} \cos \phi \pm I_1 X_{01} \sin \phi}{V_1} \times 100 =$$

'+' for lagging power factors



'-' for leading power factors

TABULAR COLUMN:

S.NO	% OF LOAD	EFFICIENCY
1	12.5	
2	25	
3	50	
4	75	
5	100	

TABULAR COLUMN:

LAGGING POWER FACTOR			LEADING POWER FACTOR		
SNO	PF	%REG	SNO	PF	%REG
1	0.2		1	0.2	
2	0.3		2	0.3	
3	0.4		3	0.4	
4	0.5		4	0.5	
5	0.6		5	0.6	
6	0.7		6	0.7	
7	0.8		7	0.8	
8	0.9		8	0.9	
9	UNITY		9	UNITY	

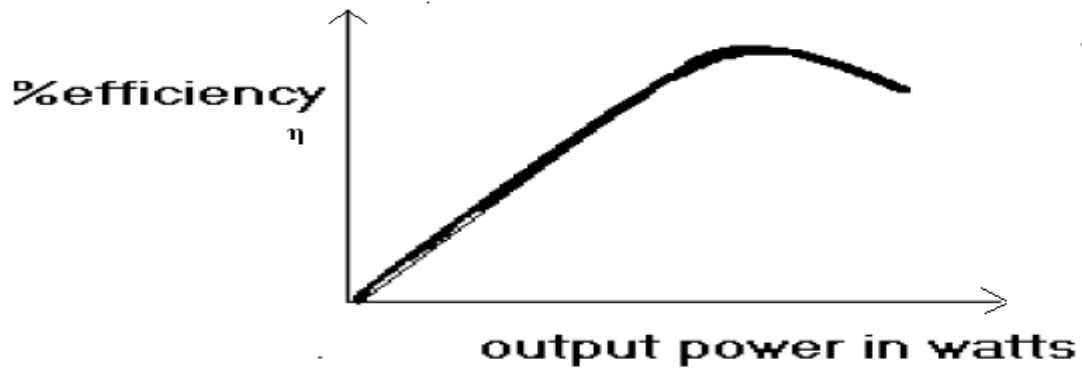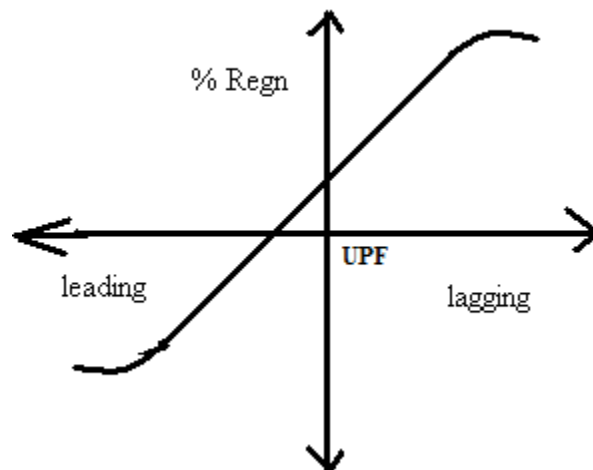MODEL GRAPHS:**1. EFFICIENCY V_s OUTPUT****2. REGULATION V_s POWER FACTOR****RESULT:****EXERCISE QUESTIONS:**

1. The readings obtained from tests on 10 KVA, 450/120V, 50Hz transformer are
O.C. Test (LV Side): 120V, 4.2A, 80W
S.C. Test (HV Side): 9.65V, 22.2A, 120W
Determine the equivalent circuit constants.

VIVQUESTIONS:

- 1) What is a transformer?
- 2) Draw the equivalent circuit of transformer?
- 3) What is the efficiency and regulation of transformer?

6. BRAKE TEST ON 3 -PHASE INDUCTION MOTOR

AIM:

To perform Brake test on 3- phase induction motor to determine performance characteristics.


NAME PLATE DETAILS:

CHARECTERISTIC	RATING
Voltage	415V
Current	7.46A
Power	5HP
Speed	1500rpm
Frequency	50Hz

APPARATUS:

S.NO	NAME OF THE EQUIPMENT	Type	Range	Quantity
1	Ammeter	MI	0-20A	1
2	Voltmeter	MI	0-150V 0-300V	2
3	Wattmeter	LPF UPF	1/2A,150V 5/10A,300V	2

CIRCUIT DIAGRAM:

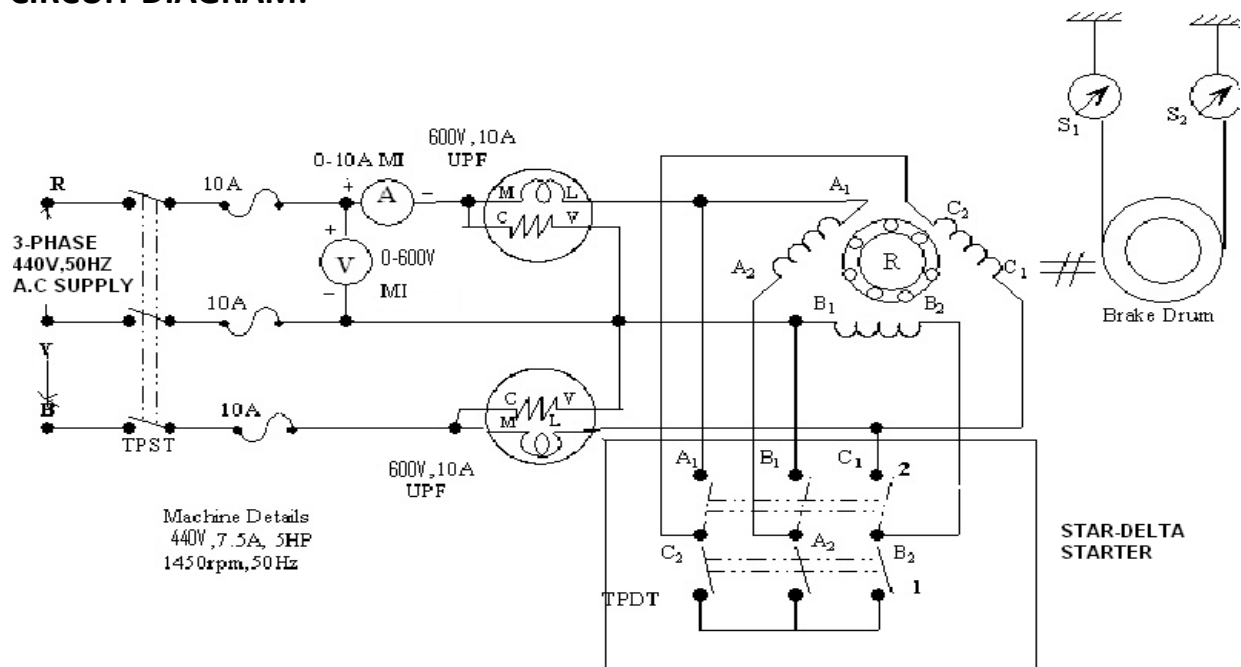

THEORY:

It is the direct method to find the efficiency of the induction motor. In this test the breaking of the rotor is done with the help of the belt which surrounds the pulley by using spring balances. When the braking power is increased by tightening the springs then the line current is increased so the

$$\text{Force on pulley (F)} = (S1-S2)*9.81 \text{ (N)}$$

$$\text{Torque (T)} = \text{Force (F)} * \text{Re. N-m}$$

$$\text{Output power of the motor} = (S1-S2)*\text{Re}*9.81*W \text{ (watts)}$$

$$W = 2\pi N/60.$$

S1, S2 = weights on the pulley.

Re= Effective radius of the pulley.

W= motor speed in rad/sec.

If V is the terminal voltage I_L is the line current and $\cos\Phi$ is the power factor.

$$\text{Power in put} = \sqrt{3}V*I_L*\cos\Phi \text{ watts.}$$

$$\text{Efficiency } (\% \eta) = (w(S1-S2)*\text{Re}*9.81/\sqrt{3}V*I_L*\cos\Phi)*100$$

$$\% \text{slip} = (N_s - N)/N_s$$

Where N_s is the synchronous speed and N is the speed of the motor.

PROCEDURE:


1. Connect the circuit as per the circuit diagram.
2. Observing precautions close the TPST switch.
3. Apply the rated voltage to the stator windings of 3 Phase induction motor with the help of starter.
4. Note down the readings of all meters on no-load.
5. Load the induction motor in steps using the brake-drum arrangement. At each step note down the readings of all meters up to full load of the motor.
6. Gradually release the load and switch OFF the supply.
7. Using thread, measure the circumference of the brake-drum when motor is at rest.


TABULAR COLUMN:

S. No.	Voltage V (volts)	Current I (Amps)	Wattmeter reading (W)		Speed N (rpm)	Spring balance reading		%Slip	Power factor	Torque N-m	Output Watts	% η
			W ₁	W ₂		S ₁ Kg	S ₂ Kg					

MODEL GRAPHS:

1. Output Vs Efficiency
2. Output Vs Torque
3. Slip Vs Torque

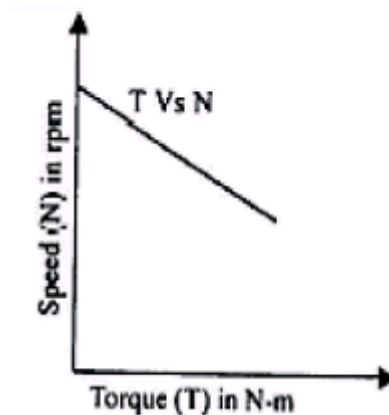Mechanical Characteristics

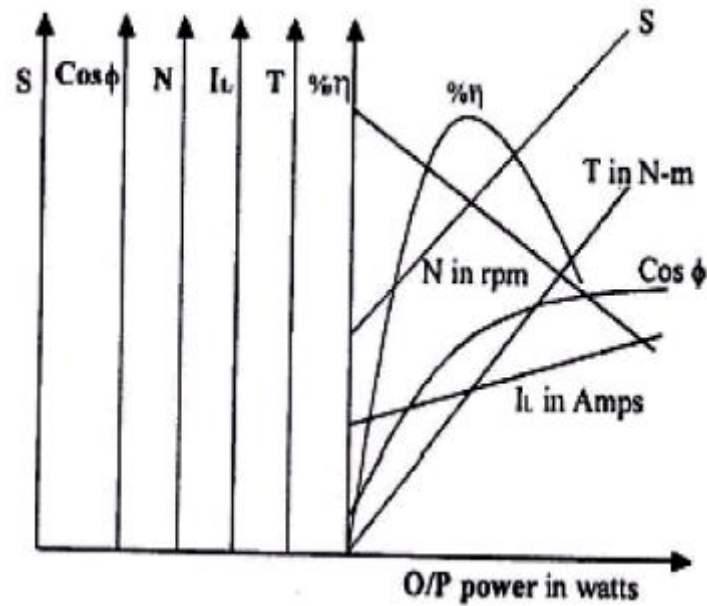Performance Characteristics**RESULT:****EXERCISE QUESTIONS:**

1. A 6 pole 3 ϕ induction motor develops 30hp including 2 hp mechanical losses at a speed of 950 r.p.m. on 550V, 50Hz Mains. The P.F. is 0.88 lagging.

Find:

- 1) Slip
- 2) Rotor Cu loss
- 3) Total input if stator losses are 2kw
- 4) η
- 5) Line current

VIVA QUESTIONS:

- 1) What is motor?
- 2) Why test is conducted on motor?
- 3) What is brake test and what is the disadvantage of brake test?

7. REGULATION OF ALTERNATOR BY SYNCHRONOUS IMPEDANCE METHOD



AIM: To predetermine the regulation of 3-phase alternator by using synchronous impedance method by conducting O.C and S.C tests.

NAME PLATE DETAILS:

CHARACTERISTIC	DC MOTOR	ALTERNATOR
Voltage	220V	415V
Current	20A	7.2A
Power	5HP	3KVA
Speed	1500rpm	1500rpm
Frequency	-	50Hz

APPARATUS REQUIRED:

S.No	NAME OF THE EQUIPMENT	RANGE	TYPE	QUANTITY
1	Voltmeter AC	0-500V	MI	1
2	Ammeter AC	0-10A	MI	1
3	Voltmeter DC	0-300V	MC	1
4	Ammeter DC	0-20A	MC	2
5	RPM Meter	---	DIGITAL	1
6	Connecting wires	---	---	Required

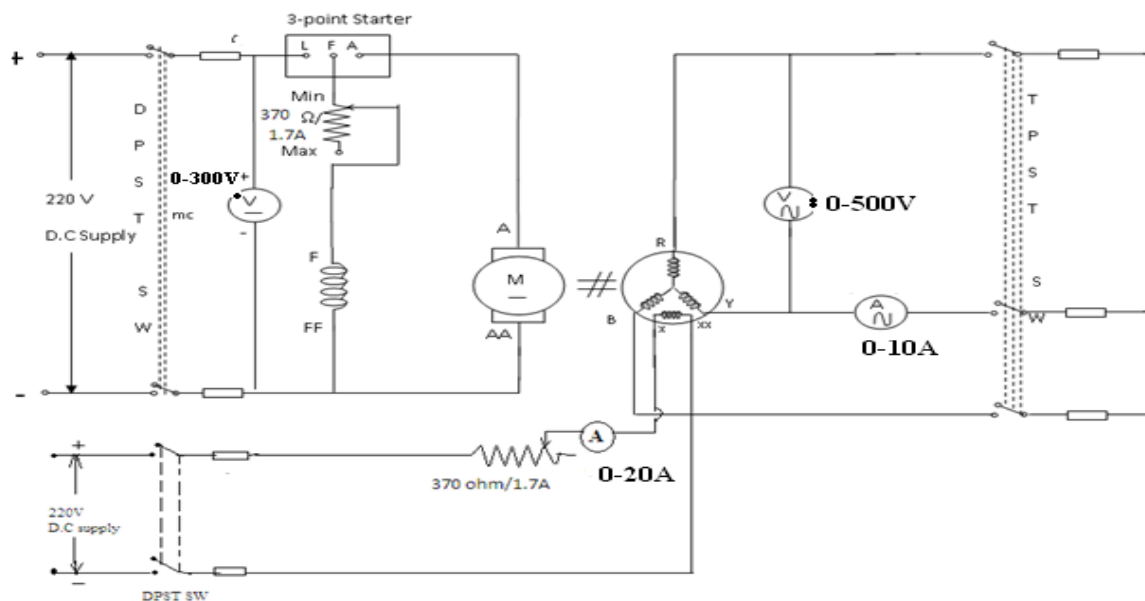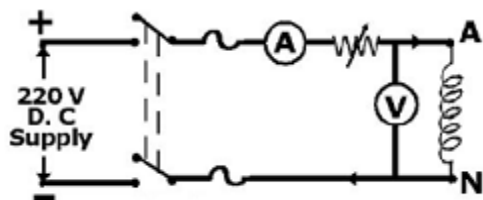CIRCUIT DIAGRAM;**OC & SC TEST:****TO FIND ARMATURE RESISTANCE:****Procedure:****1. OC test:**

- i) Connections are made as shown in the given circuit diagram for OC and SC test.
- ii) With the rheostat in the zero voltage position TPST switch open and the rheostat in their proper position, the dc supply to the motor is switched ON.
- iii) The dc motor is brought to rated speed of the alternator by properly varying the field rheostat by motor.
- iv) Now the alternator field is excited by applying the dc voltage through the rectifier in steps. At each step, note down the field current and corresponding generated voltage. This procedure is repeated till the voltage generated is much beyond rated value
- v) Reduce the alternator field excitation to zero level

2.SC test:

- i) With the rectifier in the minimum voltage position the TPST switch is closed.
- ii) Increase field excitation gradually till the SC current of the alternator reaches the rated current of alternator
- iii) Notedown all the meter readings

b) Armature Resistance:

S.No.	I (A)	V (volts)	$R_{dc} = V/I \ \Omega$

Percentage regulation at _____ load at different power factors

Power factor ($\cos\phi$)	E_o (V)		% Reg	
	Lagging	Leading	Lagging	Leading

RESULT:**EXERCISE QUESTIONS:**

1. A 1200KV, 6600V, 3phase star connected alternator has its armature resistance as 0.25Ω per phase and its synchronous reactance as 5Ω per phase. Calculate its regulation if it delivers a full load at i) 0.8 lagging and ii) 0.8 leading power factor.

VIVA QUESTIONS:

- 1) What is alternator and what is regulation?
- 2) How we can determine the regulation by using synchronous impedance method?

INTRODUCTION TO ELECTRONIC DEVICES

1. BASIC ELECTRONIC COMPONENTS

1.1. COLOUR CODING OF RESISTOR:

Colour Codes are used to identify the value of resistor. The numbers to the Colour are identified in the following sequence which is remembered as **BBROY GREAT BRITAN VERY GOOD WIFE (BBROYGBVGW)** and their assignment is listed in following table.

Black	Brown	Red	Orange	Yellow	Green	Blue	Violet	Grey	White
0	1	2	3	4	5	6	7	8	9

Table1: Colour codes of resistor

	First find the tolerance band, it will typically be gold (5%) and sometimes silver (10%).
	Starting from the other end, identify the first band - write down the number associated with that color
	Now read the next color, so write down a its vale next to the first value.
	Now read the third or 'multiplier exponent' band and write down that as the number of zeros.
	If the 'multiplier exponent' band is Gold move the decimal point one to the left. If the 'multiplier exponent' band is Silver move the decimal point two places to the left. If the resistor has one more band past the tolerance band it is a quality band.
	Read the number as the '% Failure rate per 1000 hour' This is rated assuming full wattage being applied to the resistors. (To get better failure rates, resistors are typically specified to have twice the needed wattage dissipation that the circuit produces). Some resistors use this band for temco information. 1% resistors have three bands to read digits to the left of the multiplier. They have a different temperature coefficient in order to provide the 1% tolerance. At 1% the temperature coefficient starts to become an important factor. at +/-200 ppm a change in temperature of 25 Deg C causes a value change of up to 1%

Table2: procedure to find the value of resistor using Colour codes

1.2. COLOUR CODING OF CAPACITORS

An electrical device capable of storing electrical energy. In general, a capacitor consists of two metal plates insulated from each other by a dielectric. The capacitance of a capacitor depends primarily upon its shape and size and upon the relative permittivity ϵ_r of the medium between the plates. In vacuum, in air, and in most gases, ϵ_r ranges from one to several hundred..

One classification of capacitors comes from the physical state of their dielectrics, which may be gas (or vacuum), liquid, solid, or a combination of these. Each of these classifications may be subdivided according to the specific dielectric used. Capacitors may be further classified by their ability to be used in alternating-current (ac) or direct-current (dc) circuits with various current levels.

- **Capacitor Identification Codes:** There are no international agreements in place to standardize capacitor identification. Most plastic film types (Figure1) have printed values and are normally in microfarads or if the symbol is n, Nanofarads. Working voltage is easily identified. Tolerances are upper case letters: M = 20%, K = 10%, J = 5%, H = 2.5% and F = $\pm 1\text{pF}$.

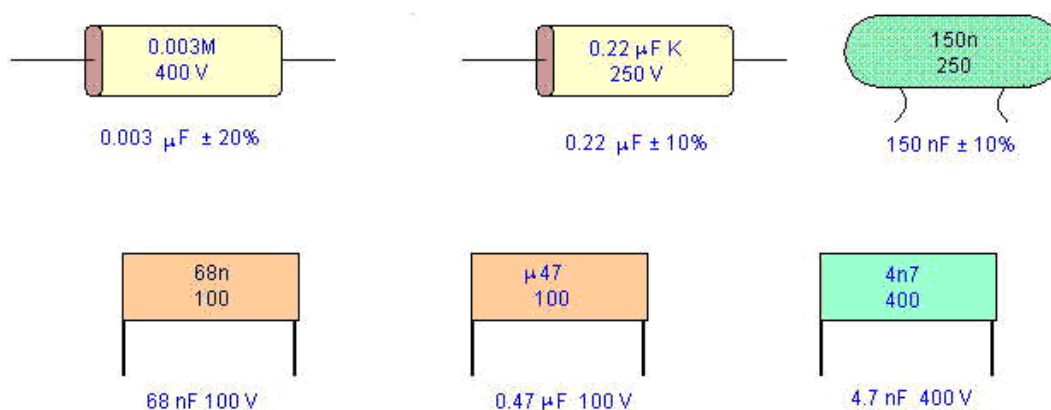


Figure 1: Plastic Film Types

A more difficult scheme is shown in Figure 2 where K is used for indicating Picofarads. The unit is picofarads and the third number is a multiplier. A capacitor coded 474K63 means $47 \times 10000 \text{ pF}$ which is equivalent to 470000 pF or 0.47 microfarads . K indicates 10% tolerance. 50, 63 and 100 are working volts.

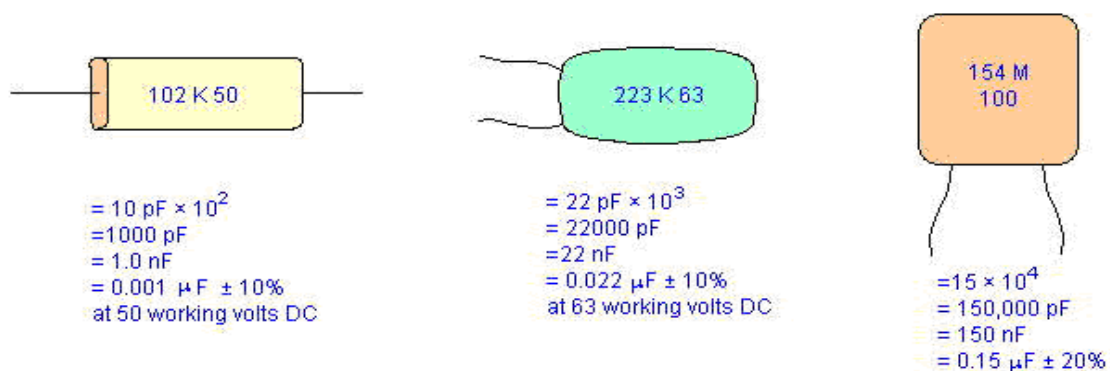


Figure 2: Pico farads Representation

Ceramic disk capacitors have many marking schemes. Capacitance, tolerance, working voltage and temperature coefficient may be found, which is as shown in figure 3. Capacitance values are given as number without any identification as to units. (uF, nF, pF) Whole numbers usually indicate pF and decimal numbers such as 0.1 or 0.47 are microfarads. Odd looking numbers such as 473 is the previously explained system and means 47 nF.

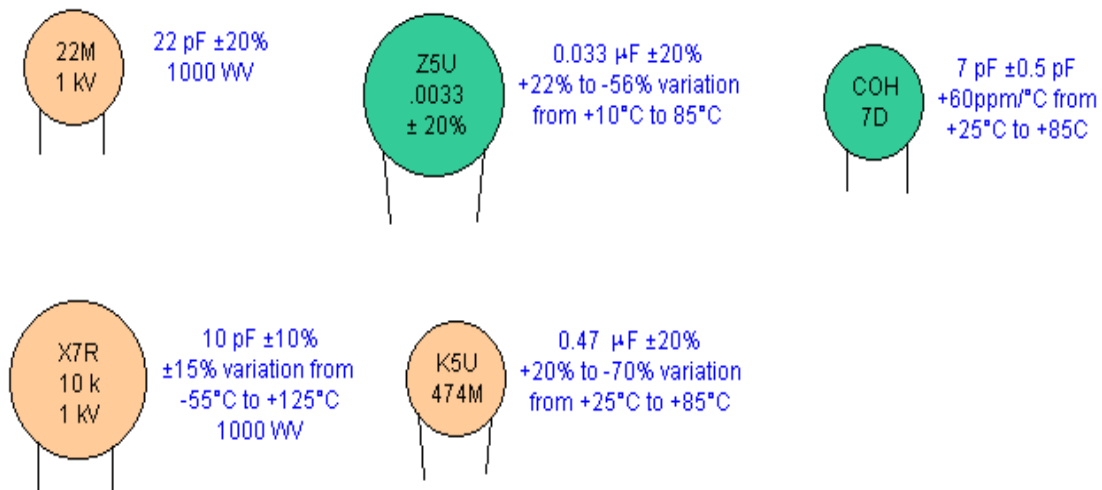


Figure3: ceramic Disk capacitor

Figure 4 shows some other miscellaneous schemes.

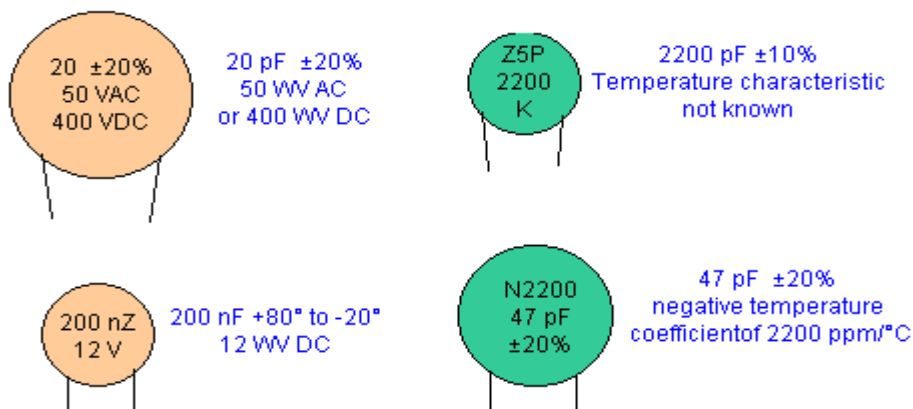


Figure 4: miscellaneous schemes.

➤ Electrolytic capacitor properties

There are a number of parameters of importance beyond the basic capacitance and capacitive reactance when using electrolytic capacitors. When designing circuits using electrolytic capacitors it is necessary to take these additional parameters into consideration for some designs, and to be aware of them when using electrolytic capacitors

- **ESR Equivalent series resistance:** Electrolytic capacitors are often used in circuits where current levels are relatively high. Also under some circumstances and current sourced from them needs to have low source impedance, for example when the capacitor is being used in a power supply circuit as a reservoir capacitor. Under these conditions it is necessary to consult the manufacturers' datasheets to discover whether the electrolytic capacitor chosen will meet the requirements for the circuit. If the ESR is high, then it will not be able to deliver the required amount of current in the circuit, without a voltage drop resulting from the ESR which will be seen as a source resistance.
- **Frequency response:** One of the problems with electrolytic capacitors is that they have a limited frequency response. It is found that their ESR rises with frequency and this generally limits their use to frequencies below about 100 kHz. This is particularly true for large capacitors, and even the smaller electrolytic capacitors should not be relied upon at high frequencies. To gain exact details it is necessary to consult the manufacturer's data for a given part.
- **Leakage:** Although electrolytic capacitors have much higher levels of capacitance for a given volume than most other capacitor technologies, they can also have a higher level of leakage. This is not a problem for most applications, such as when they are used in power supplies. However under some circumstances they are not suitable. For example they should not be used around the input circuitry of an operational amplifier. Here even a small amount of leakage can cause problems because of the high input impedance levels of the op-amp. It is also worth noting that the levels of leakage are considerably higher in the reverse direction.
- **Ripple current:** When using electrolytic capacitors in high current applications such as the reservoir capacitor of a power supply, it is necessary to consider the ripple current it is likely to experience. Capacitors have a maximum ripple current they can supply. Above this they can become too hot which will reduce their life. In extreme cases it can cause the capacitor to fail. Accordingly it is necessary to calculate the expected ripple current and check that it is within the manufacturer's maximum ratings.
- **Tolerance:** Electrolytic capacitors have a very wide tolerance. Typically this may be -50% + 100%. This is not normally a problem in applications such as decoupling or power supply smoothing, etc. However they should not be used in circuits where the exact value is of importance.
- **Polarization:** Unlike many other types of capacitor, electrolytic capacitors are polarized and must be connected within a circuit so that they only see a voltage across them in a particular way.

The physical appearance of electrolytic capacitor is as shown in Figure 5. The capacitors themselves are marked so that polarity can easily be seen. In addition to this it is common for the can of the capacitor to be connected to the negative terminal.




Figure 5: Electrolytic capacitor

It is absolutely necessary to ensure that any electrolytic capacitors are connected within a circuit with the correct polarity. A reverse bias voltage will cause the centre oxide layer forming the dielectric to be destroyed as a result of electrochemical reduction. If this occurs a short circuit will appear and excessive current can cause the capacitor to become very hot. If this occurs the component may leak the electrolyte, but under some circumstances they can explode. As this is not uncommon, it is very wise to take precautions and ensure the capacitor is fitted correctly, especially in applications where high current capability exists.

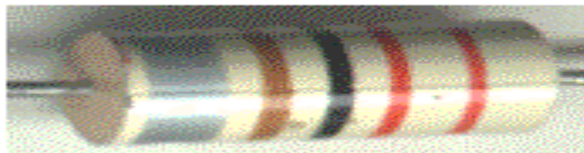
1.3. COLOUR CODING OF INDUCTORS

Inductor is just coil wound which provides more reactance for high frequencies and low reactance for low frequencies.

Molded inductors follow the same scheme except the units are usually micro henries. A brown-black-red inductor is most likely a 1000 μH . Sometimes a silver or gold band is used as a decimal point. So a red-gold-violet inductor would be a 2.7 μH . Also expect to see a wide silver or gold band before the first value band and a thin tolerance band at the end. The typical Colour codes and their values are shown in Figure 6.







1000 μH (1millihenry), 2%

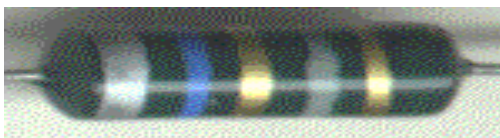


6.8 μH , 5%


Figure 6: Typical inductors Colour coding and their values.



2. CIRCUIT SYMBOLS

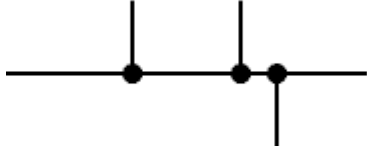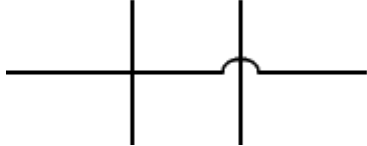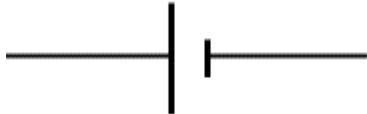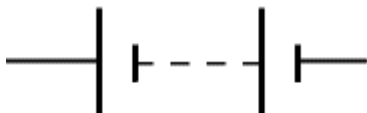WIRES AND CONNECTIONS			
S.NO.	COMPONENT NAME	CIRCUIT SYMBOL	FUNCTION
1	WIRE		To pass current very easily from one part of a circuit to another.
2	WIRES JOINED		A 'blob' should be drawn where wires are connected (joined), but it is sometimes omitted. Wires connected at 'crossroads' should be staggered slightly to form two T-junctions, as shown on the right.
3	WIRES NOT JOINED		In complex diagrams it is often necessary to draw wires crossing even though they are not connected. I prefer the 'bridge' symbol shown on the right because the simple crossing on the left may be misread as a join where you have forgotten to add a 'blob'.
POWER SUPPLIES			
S.NO	COMPONENT NAME	CIRCUIT SYMBOL	FUNCTION
1.	CELL		Supplies electrical energy. The larger terminal (on the left) is positive (+). A single cell is often called a battery, but strictly a battery is two or more cells joined together
2.	BATTERY		Supplies electrical energy. A battery is more than one cell. The larger terminal (on the left) is positive (+).
3.	DC SUPPLY		Supplies electrical energy. DC = Direct Current, always flowing in one direction.




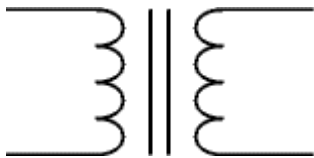
4.	AC SUPPLY		Supplies electrical energy. AC = Alternating Current, continually changing direction.
5.	FUSE		A safety device which will 'blow' (melt) if the current flowing through it exceeds a specified value.
6.	TRANSFORMER		Two coils of wire linked by an iron core. Transformers are used to step up (increase) and step down (decrease) AC voltages. Energy is transferred between the coils by the magnetic field in the core. There is no electrical connection between the coils.
7.	EARTH(GROUND)		A connection to earth. For many electronic circuits this is the 0V (zero volts) of the power supply, but for mains electricity and some radio circuits it really means the earth. It is also known as ground.





Output Devices: Lamps, Heater, Motor, etc.




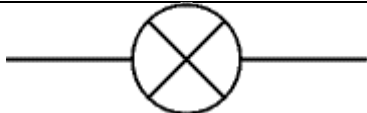
S.NO	COMPONENT NAME	CIRCUIT SYMBOL	FUNCTION
1.	LAMP(LIGHTING)		A transducer which converts electrical energy to light. This symbol is used for a lamp providing illumination, for example a car headlamp or torch bulb
2.	LAMP(INDICATOR)		A transducer which converts electrical energy to light. This symbol is used for a lamp which is an indicator, for example a warning light on a car dashboard.
3.	HEATER		A transducer which converts electrical energy to heat.
4.	MOTOR		A transducer which converts electrical energy to kinetic energy (motion).



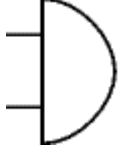
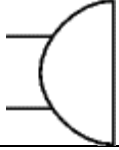
5.	BELL		A transducer which converts electrical energy to sound.
6.	BUZZER		A transducer which converts electrical energy to sound.
7.	INDUCTOR(SOLINOID, COIL)		A coil of wire which creates a magnetic field when current passes through it. It may have an iron core inside the coil. It can be used as a transducer converting electrical energy to mechanical energy by pulling on something.







Switches

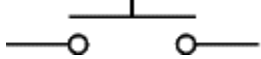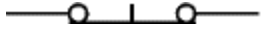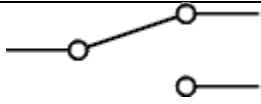
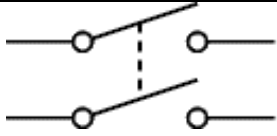
S.NO	COMPONENT NAME	CIRCUIT SYMBOL	FUNCTION
1.	PUSH SWITCH(PUSH TO MAKE)		A push switch allows current to flow only when the button is pressed. This is the switch used to operate a doorbell.
2.	PUSH TO BREAK SWITCH		This type of push switch is normally closed (on), it is open (off) only when the button is pressed.
3.	ON/OFF SWITCH(SPST)		SPST = Single Pole, Single Throw. An on-off switch allows current to flow only when it is in the closed (on) position.
4.	2 WAY SWITCH(SPDT)		SPDT = Single Pole, Double Throw. A 2-way changeover switch directs the flow of current to one of two routes according to its position. Some SPDT switches have a central off position and are described as 'on-off-on'.
5.	DUAL ON-OFF SWITCH(DPST)		DPST = Double Pole, Single Throw. A dual on-off switch which is often used to switch mains electricity because it can

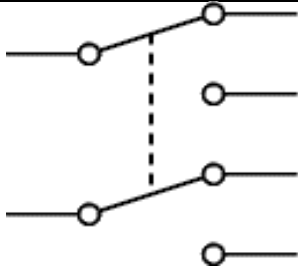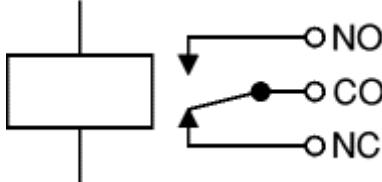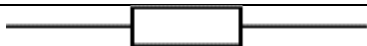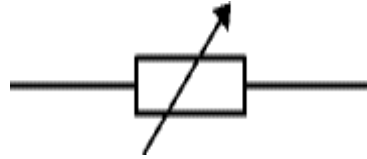			isolate both the live and neutral connections.
6.	REVERSING SWITCH(DPDT)		DPDT = Double Pole, Double Throw. This switch can be wired up as a reversing switch for a motor. Some DPDT switches have a central off position.
7.	RELAY		An electrically operated switch, for example a 9V battery circuit connected to the coil can switch a 230V AC mains circuit. NO = Normally Open, COM = Common, NC = Normally Closed.
RESISTORS			
S.NO	COMPONENT NAME	CIRCUIT SYMBOL	FUNCTION
1.	RESISTOR	 Or 	A resistor restricts the flow of current, for example to limit the current passing through an LED. A resistor is used with a capacitor in a timing circuit.
2.	VARIABLE RESISTOR(RHEOSTAT)		This type of variable resistor with 2 contacts (a rheostat) is usually used to control current. Examples include: adjusting lamp brightness, adjusting motor speed, and adjusting the rate of flow of charge into a capacitor in a timing circuit.
3.	VARIABLE RESISTOR(POTENTIOMETER)		This type of variable resistor with 3 contacts (a potentiometer) is usually used to control voltage. It can be used like this as a transducer converting position (angle of the control spindle) to an electrical signal

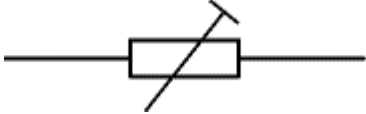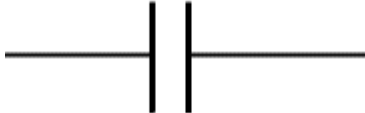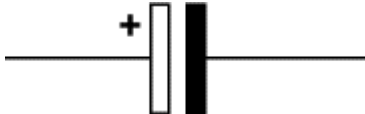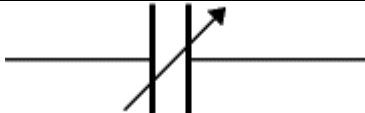4.	VARIABLE RESISTER(PRESET)		This type of variable resistor (a preset) is operated with a small screwdriver or similar tool. It is designed to be set when the circuit is made and then left without further adjustment. Presets are cheaper than normal variable resistors so they are often used in projects to reduce the cost
CAPACITORS			
S.NO	NAME OF THE COMPONENT	CIRCUIT SYMBOL	FUNCTION OF THE COMPONENT
1.	CAPACITOR		A capacitor stores electric charge. A capacitor is used with a resistor in a timing circuit. It can also be used as a filter, to block DC signals but pass AC signals.
2.	CAPACITOR POLARISED		A capacitor stores electric charge. This type must be connected the correct way round. A capacitor is used with a resistor in a timing circuit. It can also be used as a filter, to block DC signals but pass AC signals.
3.	VARIABLE CAPACITOR		A variable capacitor is used in a radio tuner.
3.	TRIMMER CAPACITOR		This type of variable capacitor (a trimmer) is operated with a small screwdriver or similar tool. It is designed to be set when the circuit is made and then left without further adjustment

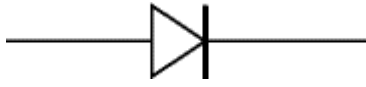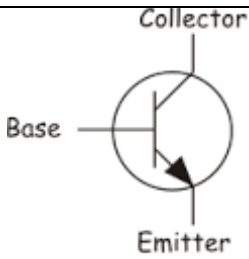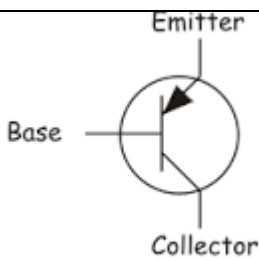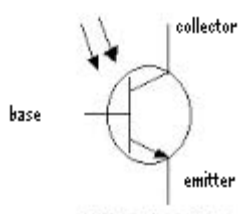DIODES			
S.NO	NAME OF THE COMPONENT	CIRCUIT SYMBOL	FUNCTION OF THE COMPONENT
1.	DIODE		A device which only allows current to flow in one direction
2.	LED(LIGHT EMITTING DIODE)		A transducer which converts electrical energy to light.
3.	ZENER DIODE		A special diode which is used to maintain a fixed voltage across its terminals
4.	Photodiode		A light-sensitive diode.
TRANSISTORS			
S.NO	NAME OF THE COMPONENT	CIRCUIT SYMBOL	FUNCTION OF THE COMPONENT
5.	TRANSISTOR NPN		A transistor amplifies current. It can be used with other components to make an amplifier or switching circuit.
6.	TRANSISTOR PNP		A transistor amplifies current. It can be used with other components to make an amplifier or switching circuit.
7.	PHOTO TRANSISTOR		A light-sensitive transistor.

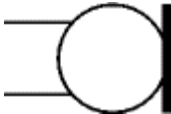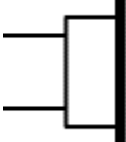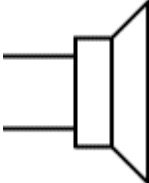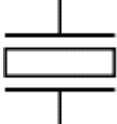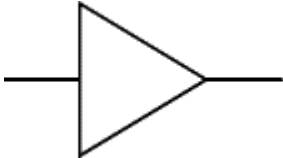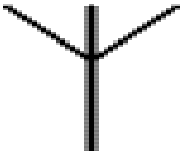AUDIO AND RADIO DEVICES			
S.NO	NAME OF THE COMPONENT	CIRCUIT SYMBOL	FUNCTION OF THE COMPONENT
1.	MICROPHONE		A transducer which converts sound to electrical energy.
2.	EARPHONE		A transducer which converts electrical energy to sound.
3.	LOUD SPEAKER		A transducer which converts electrical energy to sound.
4.	PIEZO TRANSDUCER		A transducer which converts electrical energy to sound.
5.	AMPLIFIER(GENERAL SYMBOL)		An amplifier circuit with one input. Really it is a block diagram symbol because it represents a circuit rather than just one component.
6.	ARIEL (ANTENNA)		A device which is designed to receive or transmit radio signals. It is also known as an antenna
Meters and Oscilloscope			
S.NO	NAME OF THE COMPONENT	CIRCUIT SYMBOL	FUNCTION OF THE COMPONENT
1.	VOLTMETER		A voltmeter is used to measure voltage. The Proper name for voltage is 'potential difference', but most people prefer to say voltage.
2.	AMMETER		An ammeter is used to measure current
3.	GALVANOMETER		A galvanometer is a very sensitive meter which is used to measure tiny currents, usually 1mA or

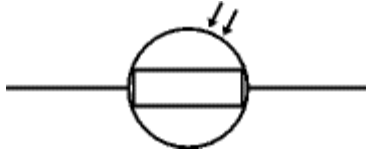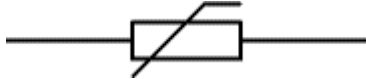			less
4.	OHEMMETER		An ohmmeter is used to measure resistance. Most multimeters have an ohmmeter setting.
5.	OSCILLOSCOPE		An oscilloscope is used to display the shape of electrical signals and it can be used to measure their voltage and time period.
Sensors (input devices)			
S.NO	NAME OF THE COMPONENT	CIRCUIT SYMBOL	FUNCTION OF THE COMPONENT
1.	LDR		A transducer which converts brightness (light) to resistance (an electrical property). LDR = Light Dependent Resistor
2.	THERMISTOR		A transducer which converts temperature (heat) to resistance (an electrical property).

3. STUDY OF CRO

An oscilloscope is a test instrument which allows us to look at the 'shape' of electrical signals by displaying a graph of voltage against time on its screen. It is like a voltmeter with the valuable extra function of showing how the voltage varies with time. A graticule with a 1cm grid enables us to take measurements of voltage and time from the screen.

The graph, usually called the trace, is drawn by a beam of electrons striking the phosphor coating of the screen making it emit light, usually green or blue. This is similar to the way a television picture is produced.

Oscilloscopes contain a vacuum tube with a cathode (negative electrode) at one end to emit electrons and an anode (positive electrode) to accelerate them so they move rapidly down the tube to the screen. This arrangement is called an electron gun. The tube also contains electrodes to deflect the electron beam up/down and left/right.

The electrons are called cathode rays because they are emitted by the cathode and this gives the oscilloscope its full name of cathode ray oscilloscope or CRO.

A dual trace oscilloscope can display two traces on the screen, allowing us to easily compare the input and output of an amplifier for example. It is well worth paying the modest extra cost to have this facility.

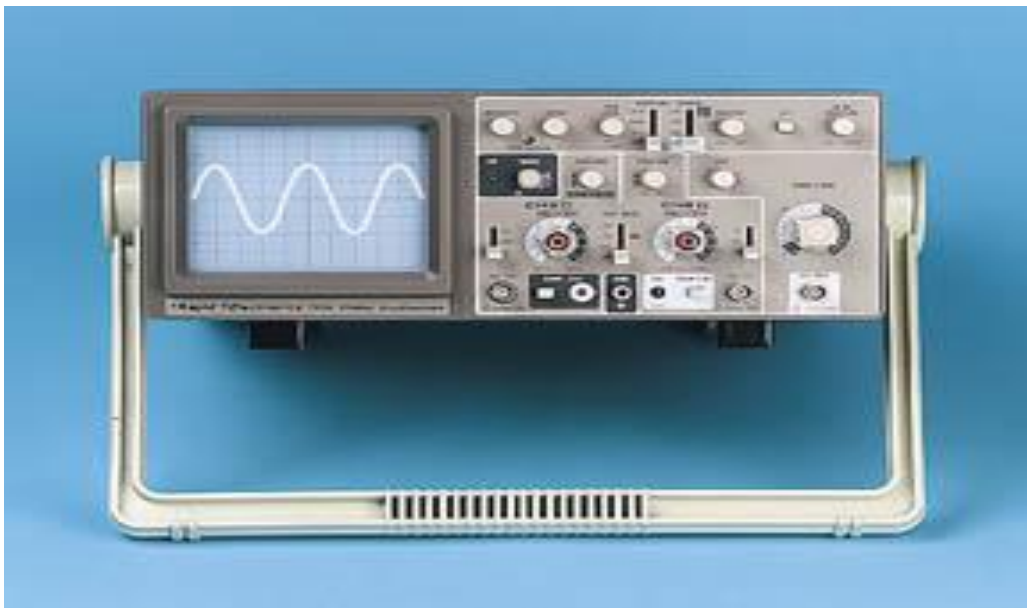


Figure1: Front Panel of CRO

▪ BASIC OPERATION:

Figure2: Internal Blocks of CRO

Setting up an oscilloscope:

Oscilloscopes are complex instruments with many controls and they require some care to set up and use successfully. It is quite easy to 'lose' the trace off the screen if controls are set wrongly.

There is some variation in the arrangement and labeling of the many controls so the following instructions may need to be adapted for this instrument.

1. Switch on the oscilloscope to warm up (it takes a minute or two).
2. Do not connect the input lead at this stage.
3. Set the AC/GND/DC switch (by the Y INPUT) to DC.
4. Set the SWP/X-Y switch to SWP (sweep).
5. Set Trigger Level to AUTO.
6. Set Trigger Source to INT (internal, the y input).
7. Set the Y AMPLIFIER to 5V/cm (a moderate value).
8. Set the TIMEBASE to 10ms/cm (a moderate speed).
9. Turn the time base VARIABLE control to 1 or CAL.
10. Adjust Y SHIFT (up/down) and X SHIFT (left/right) to give a trace across the middle of the screen, like the picture.
11. Adjust INTENSITY (brightness) and FOCUS to give a bright, sharp trace.

The following type of trace is observed on CRO after setting up, when there is no input signal connected.



Figure 3: Absence of input signal

Connecting an oscilloscope:

The Y INPUT lead to an oscilloscope should be a co-axial lead and the figure 4 shows its construction. The central wire carries the signal and the screen is connected to earth (0V) to shield the signal from electrical interference (usually called noise).

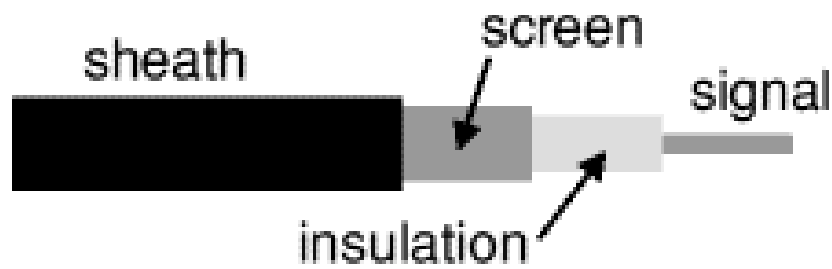


Figure4: Construction of a co-axial lead

Most oscilloscopes have a BNC socket for the y input and the lead is connected with a push and twist action, to disconnect we need to twist and pull. Professionals use a specially designed lead and probes kit for best results with high frequency signals and when testing high resistance circuits, but this is not essential for simpler work at audio frequencies (up to 20 kHz).



Figure 5: Oscilloscope lead and probes kit

Obtaining a clear and stable trace:

Once if we connect the oscilloscope to the circuit, it is necessary to adjust the controls to obtain a clear and stable trace on the screen in order to test it.

- The Y AMPLIFIER (VOLTS/CM) control determines the height of the trace. Choose a setting so the trace occupies at least half the screen height, but does not disappear off the screen.
- The TIMEBASE (TIME/CM) control determines the rate at which the dot sweeps across the screen. Choose a setting so the trace shows at least one cycle of the signal across the screen. Note that a steady DC input signal gives a horizontal line trace for which the time base setting is not critical.
- The TRIGGER control is usually best left set to AUTO.

The trace of an AC signal with the oscilloscope controls correctly set is as shown in Figure 6.

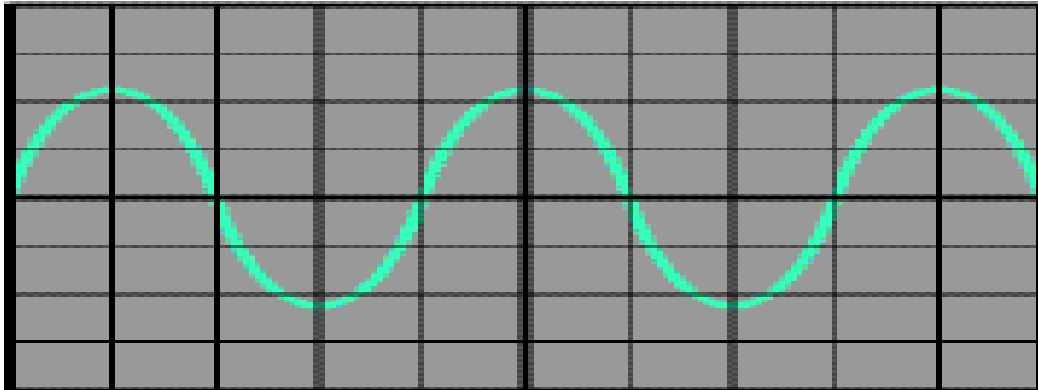


Figure 6 : Stable waveform

Measuring voltage and time period

The trace on an oscilloscope screen is a graph of voltage against time. The shape of this graph is determined by the nature of the input signal. In addition to the properties labeled on the graph, there is frequency which is the number of cycles per second. The diagram shows a sine wave but these properties apply to any signal with a constant shape

Figure7: Properties of trace

- **Amplitude** is the maximum voltage reached by the signal. It is measured in volts.
- **Peak voltage** is another name for amplitude.
- **Peak-peak voltage** is twice the peak voltage (amplitude). When reading an oscilloscope trace it is usual to measure peak-peak voltage.
- **Time period** is the time taken for the signal to complete one cycle. It is measured in seconds (s), but time periods tend to be short so milliseconds (ms) and microseconds (μ s) are often used. $1\text{ms} = 0.001\text{s}$ and $1\mu\text{s} = 0.000001\text{s}$.
- **Frequency** is the number of cycles per second. It is measured in hertz (Hz), but frequencies tend to be high so kilohertz (kHz) and megahertz (MHz) are often used. $1\text{kHz} = 1000\text{Hz}$ and $1\text{MHz} = 1000000\text{Hz}$.

$$\text{Frequency} = \frac{1}{\text{Time period}}$$

$$\text{Time period} = \frac{1}{\text{Frequency}}$$

A) Voltage: Voltage is shown on the vertical y-axis and the scale is determined by the Y AMPLIFIER (VOLTS/CM) control. Usually peak-peak voltage is measured because it

can be read correctly even if the position of 0V is not known. The amplitude is half the peak-peak voltage.

$$\text{Voltage} = \text{distance in cm} \times \text{volts/cm}$$

B) Time period: Time is shown on the horizontal x-axis and the scale is determined by the TIMEBASE (TIME/CM) control. The time period (often just called period) is the time for one cycle of the signal. The frequency is the number of cycles per second, frequency = 1/time period.

$$\text{Time} = \text{distance in cm} \times \text{time/cm}$$

4. STUDY OF FUNCTION GENERATOR

A function generator is a device that can produce various patterns of voltage at a variety of frequencies and amplitudes. It is used to test the response of circuits to common input signals. The electrical leads from the device are attached to the ground and signal input terminals of the device under test.



Figure 1: A typical low-cost function generator.

➤ **Features and controls :**

Most function generators allow the user to choose the shape of the output from a small number of options.

- Square wave - The signal goes directly from high to low voltage.

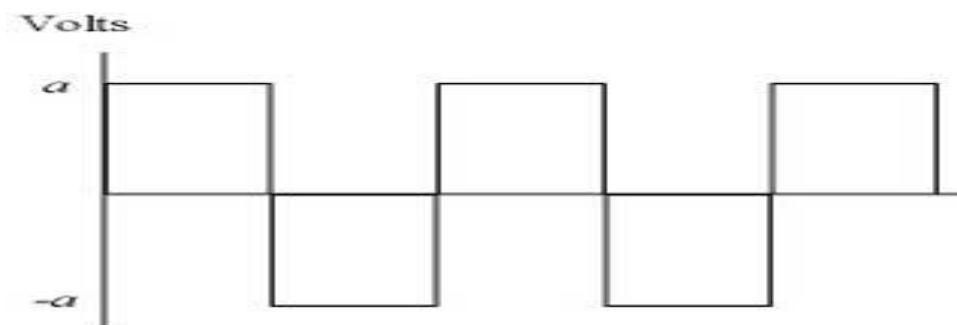


Figure 2: Square wave

The duty cycle of a signal refers to the ratio of high voltage to low voltage time in a square wave signal.

- Sine wave - The signal curves like a sinusoid from high to low voltage.

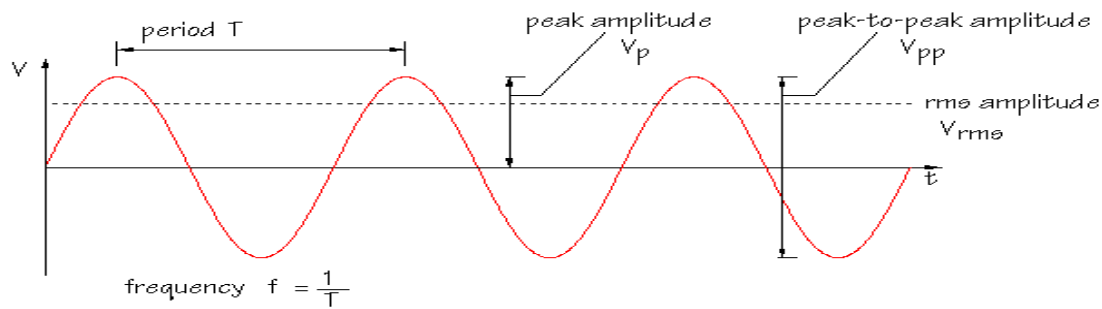


Figure3: Sine Wave

- Triangle wave - The signal goes from high to low voltage at a fixed rate.

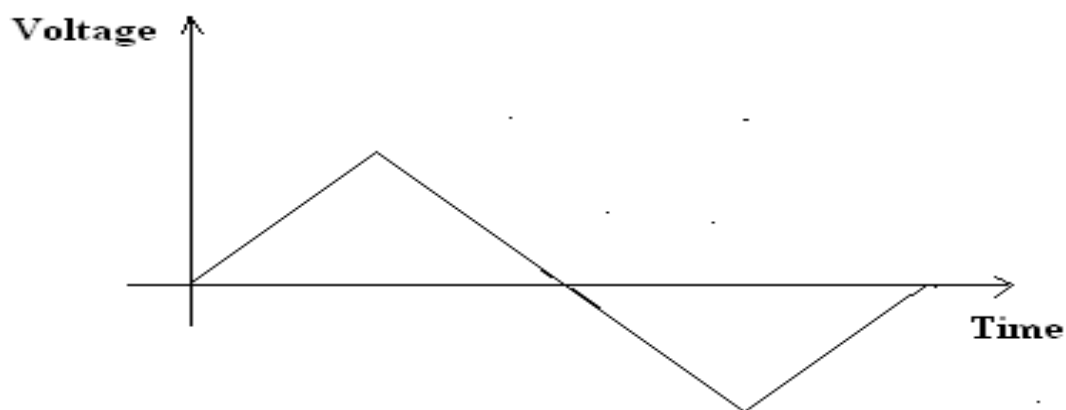


Figure4: Triangular Wave

The amplitude control on a function generator varies the voltage difference between the high and low voltage of the output signal. The direct current (DC) offset control on a function generator varies the average voltage of a signal relative to the ground. The frequency control of a function generator controls the rate at which output signal oscillates. On some function generators, the frequency control is a combination of different controls. One set of controls chooses the broad frequency range (order of magnitude) and the other selects the precise frequency. This allows the function generator to handle the enormous variation in frequency scale needed for signals.

➤ How to use a function generator

After powering on the function generator, the output signal needs to be configured to the desired shape. Typically, this means connecting the signal and ground leads to an oscilloscope to check the controls. Adjust the function generator until the output signal is correct, then attach the signal and ground leads from the function generator to the input and ground of the device under test. For some applications, the negative lead of the function generator should attach to a negative input of the device, but usually attaching to ground is sufficient.

5. STUDY OF REGULATED POWER SUPPLY

There are many types of power supply. Most are designed to convert high voltage AC mains electricity to a suitable low voltage supply for electronic circuits and other devices. A power supply can be broken down into a series of blocks, each of which performs a particular function. For example a 5V regulated supply:

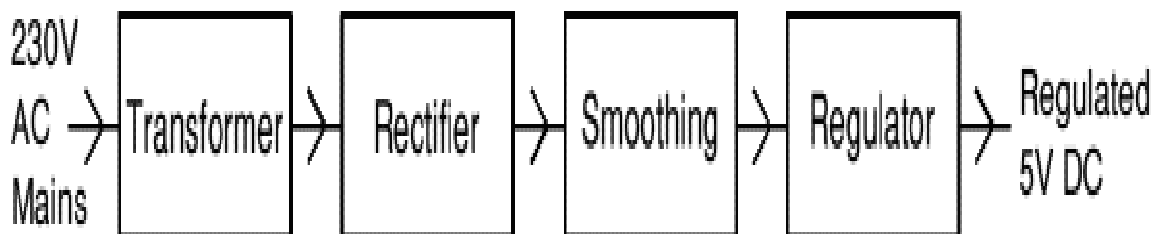


Figure1: Block Diagram of Regulated power supply

Each of the blocks is described in more detail below:

- **Transformer:** Steps down high voltage AC mains to low voltage AC.
 - **Rectifier:** Converts AC to DC, but the DC output is varying.
 - **Smoothing:** Smooths the DC from varying greatly to a small ripple.
 - **Regulator:** Eliminates ripple by setting DC output to a fixed voltage.
- **Dual Supplies:** Some electronic circuits require a power supply with positive and negative outputs as well as zero volts (0V). This is called a 'dual supply' because it is like two ordinary supplies connected together as shown in the diagram. Dual supplies have three outputs, for example a $\pm 9V$ supply has +9V, 0V and -9V outputs.

Figure 2: Dual Supply

6. TYPES OF CIRCUIT BOARD

- **Breadboard:** This is a way of making a temporary circuit, for testing purposes or to try out an idea. No soldering is required and all the components can be re-used afterwards. It is easy to change connections and replace components. Almost all the Electronics Club projects started life on a breadboard to check that the circuit

worked as intended. The following figure depicts the appearance of Bread board in which the holes in top and bottom stripes are connected horizontally that are used for power supply and ground connection conventionally and holes on middle stripes connected vertically. And that are used for circuit connections conventionally.

Figure 1: Bread board

- **Strip board:**

Figure 2: Strip board

Strip board has parallel strips of copper track on one side. The strips are 0.1" (2.54mm) apart and there are holes every 0.1" (2.54mm). Strip board requires no special preparation other than cutting to size. It can be cut with a junior hacksaw, or simply snap it along the lines of holes by putting it over the edge of a bench or table and pushing hard.

Printed Circuit Board: A printed circuit board, or PCB, is used to mechanically support and electrically connect electronic components using conductive pathways, tracks or traces etched from copper sheets laminated onto a non-conductive substrate. It is also referred to as printed wiring board (PWB) or etched wiring board. A PCB populated with electronic components is a printed circuit assembly (PCA), also known as a printed circuit board assembly (PCBA).

Printed circuit boards have copper tracks connecting the holes where the components are placed. They are designed specially for each circuit and make construction very easy. However, producing the PCB requires special equipment so this method is not recommended if you are a beginner unless the PCB is provided for you.

Figure 3: Printed circuit board

PCBs are inexpensive, and can be highly reliable. They require much more layout effort and higher initial cost than either wire-wrapped or point-to-point constructed circuits, but are much cheaper and faster for high-volume production. Much of the electronics industry's PCB design, assembly, and quality control needs are set by standards that are published by the IPC organization.

SECTION-B

1. P-N JUNCTION DIODE CHARACTERISTICS

- AIM:**
1. To observe and draw the Forward and Reverse bias V-I Characteristics of a P-N Junction diode.
 2. To calculate static and dynamic resistance in both forward and Reverse Bias Conditions.

APPARATUS:

- | | |
|-----------------------------------|--------|
| 1. P-N Diode IN4007 | - 1No. |
| 2. Regulated Power supply (0-30V) | - 1No. |
| 3. Resistor 1K Ω | - 1No. |
| 4. Ammeter (0-20 mA) | - 1No. |
| 5. Ammeter (0-200 μ A) | - 1No. |
| 6. Voltmeter (0-20V) | - 2No. |
| 7. Bread board | |
| 8. Connecting wires | |


THEORY:



A P-N junction diode conducts only in one direction. The V-I characteristics of the diode are curve between voltage across the diode and current flowing through the diode. When external voltage is zero, circuit is open and the potential barrier does not allow the current to flow. Therefore, the circuit current is zero. When P-type (Anode) is connected to +ve terminal and n- type (cathode) is connected to -ve terminal of the supply voltage is known as forward bias. The potential barrier is reduced when diode is in the forward biased condition. At some forward voltage, the potential barrier altogether eliminated and current starts flowing through the diode and also in the circuit. Then diode is said to be in ON state. The current increases with increasing forward voltage.

When N-type (cathode) is connected to +ve terminal and P-type (Anode) is connected to -ve terminal of the supply voltage is known as reverse bias and the potential barrier across the junction increases. Therefore, the junction resistance becomes very high and a very small current (reverse saturation current) flows in the circuit. Then diode is said to be in OFF state. The reverse bias current is due to minority charge carriers.

CIRCUIT DIAGRAM:

A) Forward bias:

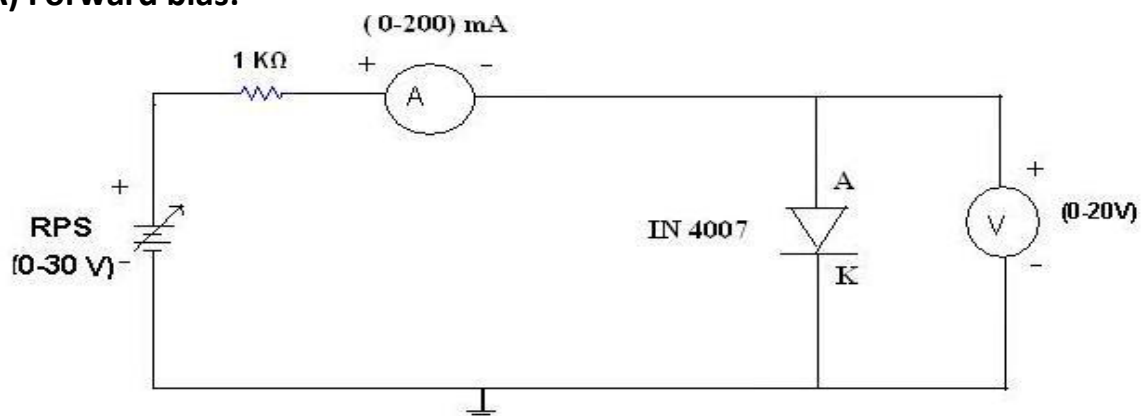

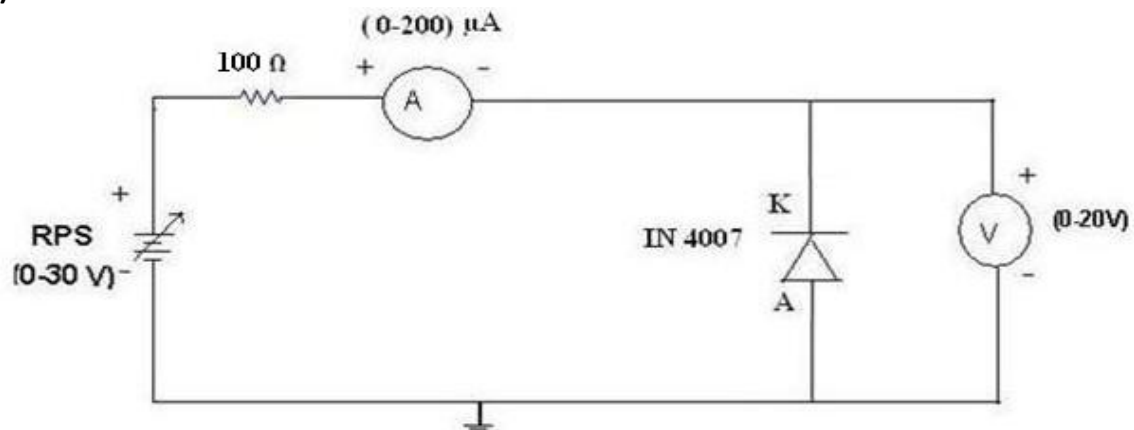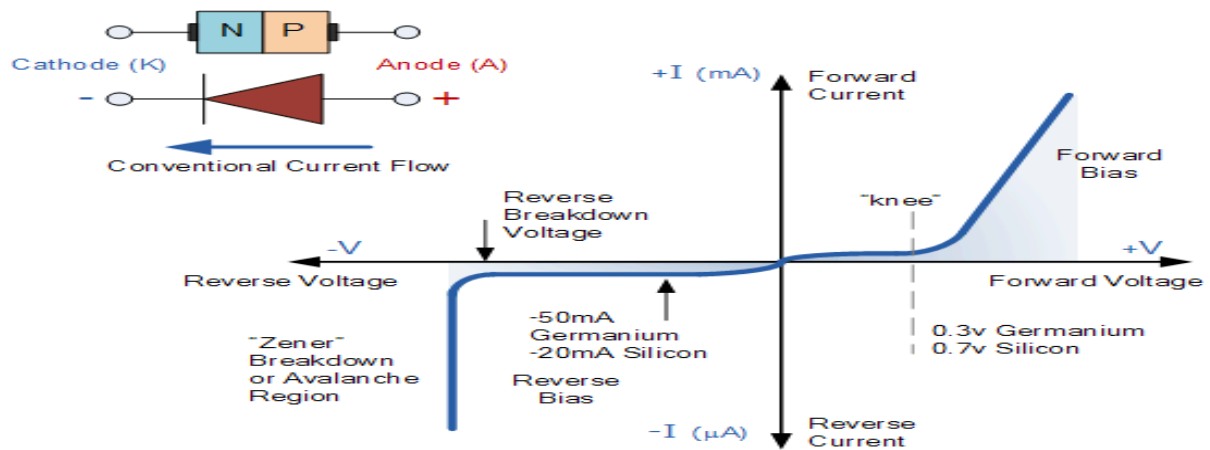B) Reverse Bias:**MODEL GRAPH:****OBSERVATIONS:****A) FORWARD BIAS:**

S.NO	Applied Voltage(V)	Forward Voltage(V_f)	Forward Current(I_f (mA))

B) REVERSE BIAS:

S.NO	Applied Voltage(V)	Reverse Voltage(V_R)	Reverse Current($I_R(\mu A)$)

Calculations:

Calculation of Static and Dynamic Resistance for a given diode.

In forward bias condition:

$$\text{Static Resistance } R_s = V_f / I_f =$$

$$\text{Dynamic Resistance, } R_D = \Delta V_f / \Delta I_f =$$

In Reverse bias condition:

$$\text{Static Resistance } R_s = V_R / I_R =$$

$$\text{Dynamic Resistance, } R_D = \Delta V_R / \Delta I_R =$$

PROCEDURE:**A) FORWARD BIAS:**

1. Connections are made as per the circuit diagram.
2. For forward bias, the RPS +ve is connected to the anode of the diode and RPS -ve is connected to the cathode of the diode
3. Switch on the power supply and increases the input voltage (supply voltage) in Steps of 0.1V
4. Note down the corresponding current flowing through the diode and voltage across the diode for each and every step of the input voltage.
5. The reading of voltage and current are tabulated.
6. Graph is plotted between voltage (V_f) on X-axis and current (I_f) on Y-axis.

B) REVERSE BIAS:

1. Connections are made as per the circuit diagram
2. for reverse bias, the RPS +ve is connected to the cathode of the diode and RPS -ve is connected to the anode of the diode.
3. Switch on the power supply and increase the input voltage (supply voltage) in Steps of 1V.

4. Note down the corresponding current flowing through the diode voltage across the diode for each and every step of the input voltage.
5. The readings of voltage and current are tabulated
6. Graph is plotted between voltage (V_R) on X-axis and current (I_R) on Y-axis.

PRECAUTIONS:

1. All the connections should be correct.
2. Parallax error should be avoided while taking the readings from the Analog meters.

RESULT:**EXERCISE QUESTIONS:**

1. The reverse saturation current of a silicon p – n junction diode at an operating temperature of 27°C is 50 nA. Compute the dynamic forward and reverse resistances of the diode for applied voltages of 0.8 V and -0.4 V respectively
2. Find the value of D.C. resistance and A.C resistance of a Germanium junction diode at 25°C with reverse saturation current, $I_o = 25\mu\text{A}$ and at an applied voltage of 0.2V across the diode

VIVA QUESTIONS:

1. Define depletion region of a diode?
2. What is meant by transition & space charge capacitance of a diode?
3. Is the V-I relationship of a diode Linear or Exponential?
4. Define cut-in voltage of a diode and specify the values for Si and Ge diodes?
5. What are the applications of a p-n diode?
6. Draw the ideal characteristics of P-N junction diode?
7. What is the diode equation?
8. What is PIV?
9. What is the break down voltage?
10. What is the effect of temperature on PN junction diodes?

2. ZENER DIODE CHARACTERISTICS AND ZENER AS VOLTAGE REGULATOR

AIM:

- To observe and draw the static characteristics of a zener diode
- To find the voltage regulation of a given zener diode

APPARATUS:

- | | |
|-----------------------------------|--------|
| 1. Zener diode | - 1No. |
| 2. Regulated Power Supply (0-30v) | - 1No. |
| 3. Voltmeter (0-20v) | - 1No. |
| 4. Ammeter (0-20mA) | - 1No. |
| 5. Resistor (1K ohm) | |
| 6. Bread Board | |
| 7. Connecting wires | |


THEORY:



A zener diode is heavily doped p-n junction diode, specially made to operate in the break down region. A p-n junction diode normally does not conduct when reverse biased. But if the reverse bias is increased, at a particular voltage it starts conducting heavily. This voltage is called Break down Voltage. High current through the diode can permanently damage the device


To avoid high current, we connect a resistor in series with zener diode. Once the diode starts conducting it maintains almost constant voltage across the terminals whatever may be the current through it, i.e., it has very low dynamic resistance. It is used in voltage regulators.

CIRCUIT DIAGRAM

A) STATIC CHARACTERISTICS :

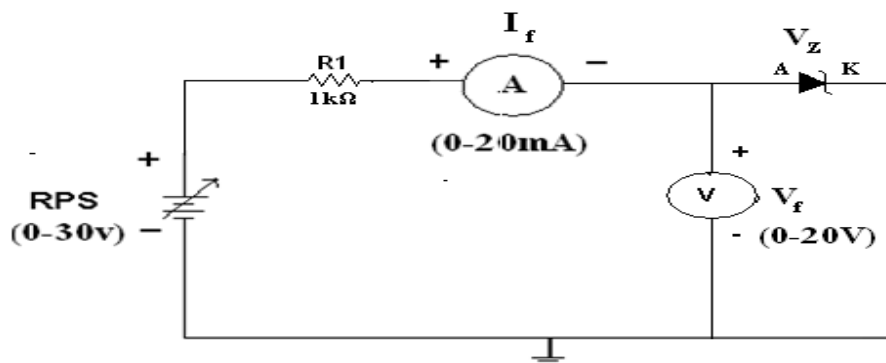

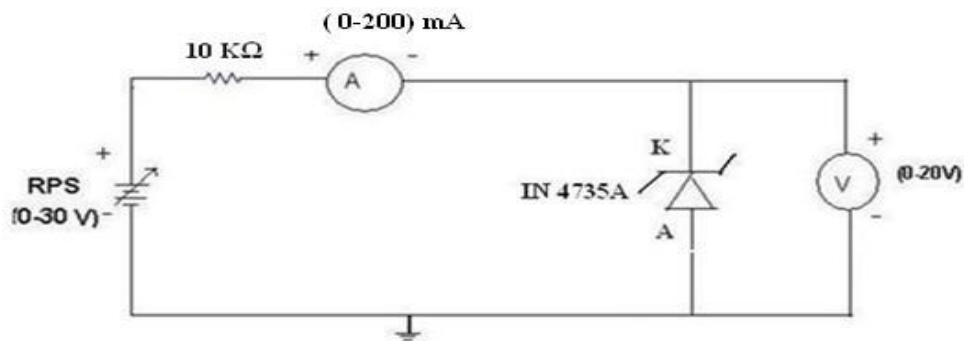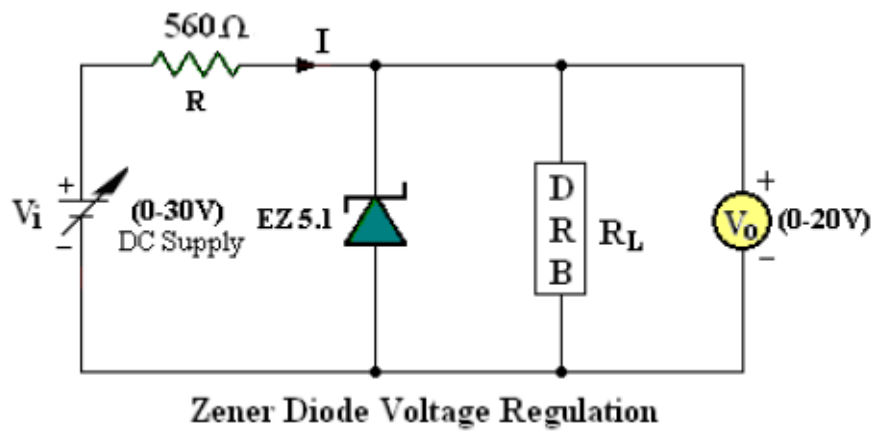b) REVERSE BIAS CHARACTERISTICS:**VOLTAGE REGULATION:**

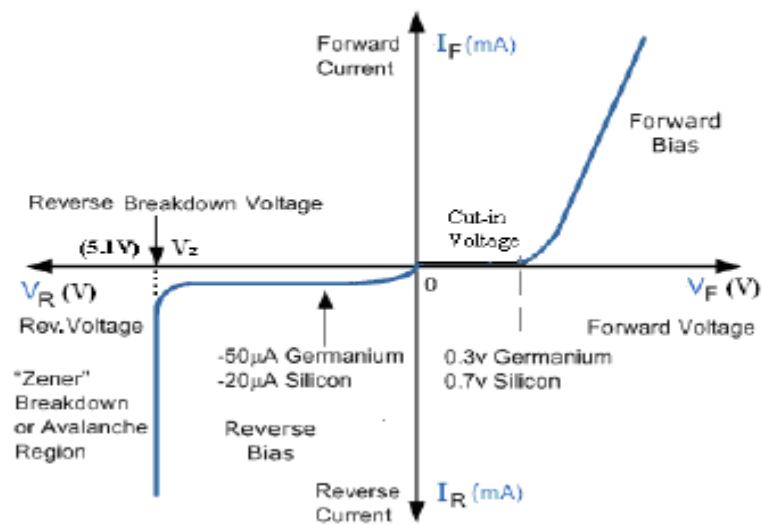MODEL GRAPHS:**ZENER DIODE CHARACTERISTICS:**

V-I Characteristics of Zener Diode

OBSERVATIONS:**A) FORWARD BIAS characteristics:**

S.NO	Applied Voltage(V)	Forward Voltage(V_f)	Forward Current(I_f (mA))

B) REVERSE BIAS Characteristics:

S.NO	Applied Voltage(V)	Reverse Voltage(V_R)	Reverse Current(I_R (mA))

PROCEDURE:**A) Static characteristics:**

1. Connections are made as per the circuit diagram.
2. The Regulated power supply voltage is increased in steps.
3. The Forward current (I_f), and the forward voltage (V_f) are observed and then noted in the tabular form.
4. A graph is plotted between Forward current (I_f) on X-axis and the forward voltage (V_f) on Y-axis.

B) Regulation characteristics:**LOAD REGULATION CHARACTERISTICS:**

1. Connect the Circuit as per the Circuit Diagram on the bread board.
2. By changing the load Resistance, kept constant I/P Voltage at 5V, 10 V, 15 V as Per table given below. Take the readings of O/P Voltmeter ($V_o=V_z$).
3. Now by changing the I/P Voltage, kept constant load Resistance at 1K, 2K, 3K as per table given below. Take the readings of O/P Voltmeter ($V_o=V_z$).

LOAD REGULATION

S.No	$R_L (\Omega)$	$V_{i1}=5V$ $V_o (V)$	$V_{i2}=10V$ $V_o (V)$	$V_{i3}=15V$ $V_o (V)$
1	100			
2	300			
3	500			
4	700			
5	900			
6	1K			
7	3K			
8	5K			
9	7K			
10	10K			

LINE REGULATION

$V_i (V)$	$R_{L1}=1K\Omega$ $V_o (V)$	$R_{L2}=2K\Omega$ $V_o (V)$	$R_{L3}=3K\Omega$ $V_o (V)$
0			
1			
3			
5			
7			
9			
11			
13			
15			
20			

PRECAUTIONS:

1. The terminals of the zener diode should be properly identified
2. While determined the load regulation, load should not be immediately shorted.
3. Should be ensured that the applied voltages & currents do not exceed the ratings of the diode.

RESULT:

EXERCISE QUESTIONS:

1. A Zener voltage regulator circuit is to maintain constant voltage at 60 V, over a current range from 5 to 50 mA. The input supply voltage is 200 V. Determine the value of resistance R to be connected in the circuit, for voltage regulation from load current $I_L = 0$ mA to I_L max, the maximum possible value of I_L . What is the value I_L max?

VIVAQUESTIONS:

1. What type of temp coefficient does the zener diode have?
2. If the impurity concentration is increased, how the depletion width effected?
3. Does the dynamic impedance of a zener diode vary?
4. Explain briefly about avalanche and zener breakdowns?
5. Draw the zener equivalent circuit?
6. Differentiate between line regulation & load regulation?
7. In which region zener diode can be used as a regulator?
8. How the breakdown voltage of a particular diode can be controlled?
9. What type of temperature coefficient does the Avalanche breakdown has?
10. By what type of charge carriers the current flows in zener and avalanche breakdown diodes?

3. HALF -WAVE RECTIFIER WITH AND WITHOUT FILTER

AIM: To examine the input and output waveforms of half wave Rectifier and also calculate its load regulation and ripple factor.

1. with Filter
2. without Filter

APPARATUS:

Digital multimetersMultimeter	- 1No.
Transformer (6V-0-6V)	- 1No.
Diode, 1N4007	- 1No.
Capacitor 100 μ f/470 μ f	- 1No.
Decade Resistance Box	- 1No.
Breadboard	
CRO and CRO probes	
Connecting wires	

THEORY:

In Half Wave Rectification, When AC supply is applied at the input, only Positive Half Cycle appears across the load whereas, the negative Half Cycle is suppressed. How this can be explained as follows:

During positive half-cycle of the input voltage, the diode D1 is in forward bias and conducts through the load resistor R_L . Hence the current produces an output voltage across the load resistor R_L , which has the same shape as the +ve half cycle of the input voltage.

During the negative half-cycle of the input voltage, the diode is reverse biased and there is no current through the circuit. i.e., the voltage across R_L is zero. The net result is that only the +ve half cycle of the input voltage appears across the load. The average value of the half wave rectified o/p voltage is the value measured on dc voltmeter.

For practical circuits, transformer coupling is usually provided for two reasons.

1. The voltage can be stepped-up or stepped-down, as needed.
2. The ac source is electrically isolated from the rectifier. Thus preventing shock hazards in the secondary circuit.

The efficiency of the Half Wave Rectifier is 40.6%

Theoretical calculations for Ripple factor:**Without Filter:**

$$V_{rms} = V_m / 2$$



$$V_m = 2V_{rms}$$


$$V_{dc} = V_m / \pi$$

$$\text{Ripple factor } r = \sqrt{(V_{rms} / V_{dc})^2 - 1} = 1.21$$

With Filter:

$$\text{Ripple factor, } r = 1 / (2\sqrt{3} f C R)$$

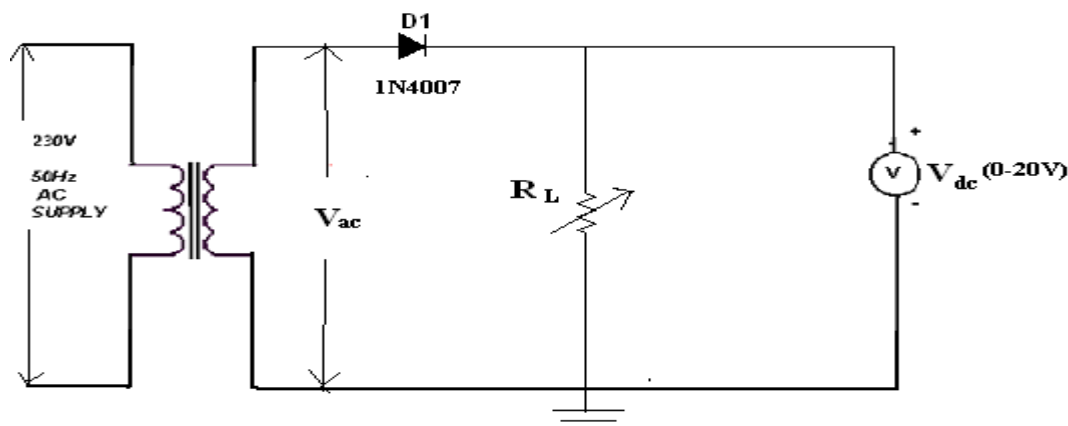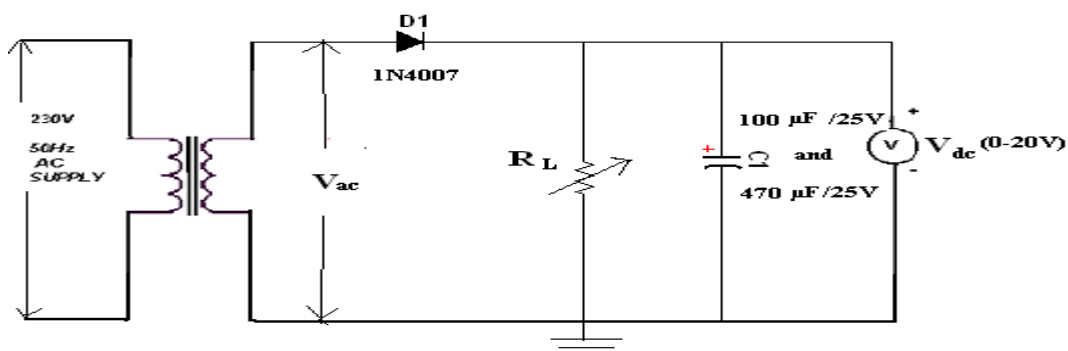CIRCUIT DIAGRAM:**A) Half wave Rectifier without filter:****B) Half wave Rectifier with filter**

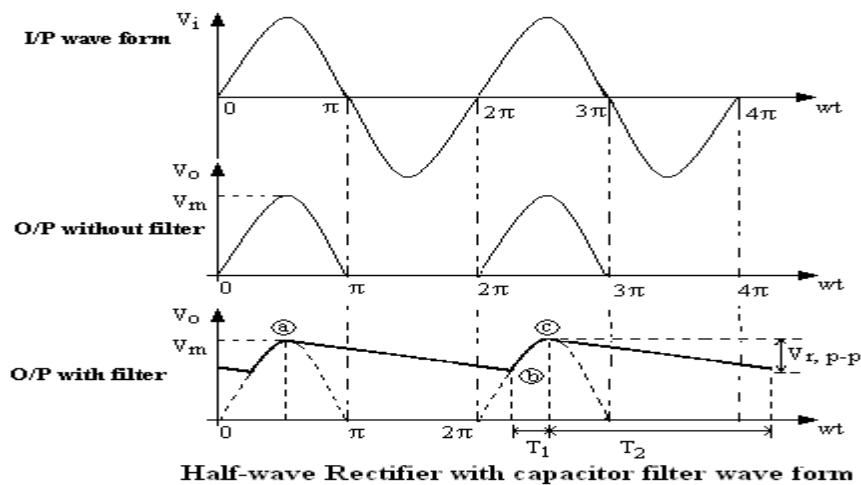MODEL WAVEFORMS:**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. Connect the primary side of the transformer to ac mains and the secondary side to the rectifier input.
3. By the multimeter, measure the ac input voltage of the rectifier and, ac and dc voltage at the output of the rectifier.
4. Find the theoretical of dc voltage by using the formula,

$$V_{dc} = V_m / \pi$$

Where, $V_m = 2V_{rms}$, (V_{rms} =output ac voltage.)

5. The Ripple factor is calculated by using the formula

$$r = \text{ac output voltage} / \text{dc output voltage.}$$

WITHOUT FILTER:

S.No	Load Resistance R_L kilo-ohm	O/P Voltage (V_o)		Ripple factor $\left(\gamma = \frac{V_{ac}}{V_{dc}}\right)$	% of Regulation $\left(\frac{V_{NL} - V_{FL}}{V_{NL}} \times 100\%\right)$
		V_{ac} (V)	V_{dc} (V)		
1	1 ^S				
2	2				
3	3				
4	4				
5	5				
6	6				
7	7				
8	8				

WITH CAPACITOR FILTER:

S.No	Load Resistance R_L kilo-ohm	O/P Voltage (V_o)		Ripple factor $\left(\gamma = \frac{V_{ac}}{V_{dc}}\right)$	% of Regulation $\left(\frac{V_{NL} - V_{FL}}{V_{NL}} \times 100\%\right)$
		V_{ac} (V)	V_{dc} (V)		
1	1				
2	2				
3	3				
4	4				
5	5				
6	6				
7	7				
8	8				

REGULATION CHARACTERISTICS:

1. Connections are made as per the circuit diagram.
2. By increasing the value of the rheostat, the voltage across the load and current flowing through the load are measured.
3. The reading is tabulated.
4. From the value of no-load voltages, the %regulation is calculated using the formula,

$$\% \text{Regulation} = [(V_{NL} - V_{FL}) / V_{FL}] \times 100$$

PRECAUTIONS:

1. The primary and secondary side of the transformer should be carefully identified
2. The polarities of all the diodes should be carefully identified.
3. While determining the % regulation, first Full load should be applied and then it should be decremented in steps.

RESULT:**EXERCISE QUESTIONS:**

1. A half wave rectifier having a resistor load of 1000 ohms rectifier an alternating of 325V peak value and the diode has a forward resistance of 100 ohms calculate a) peak ,average and RMS value of current) dc power output c) A.C input power and d) efficiency of the rectifier

VIVA QUESTIONS:

1. What is the PIV of Half wave rectifier?
2. What is the efficiency of half wave rectifier?
3. What is the rectifier?
4. What is the difference between the half wave rectifier and full wave Rectifier?
5. What is the o/p frequency of Bridge Rectifier?
6. What are the ripples?
7. What is the function of the filters?
8. What is TUF?
9. What is the average value of o/p voltage for HWR?
10. What is the peak factor?

4. FULL-WAVE RECTIFIER WITH AND WITHOUT FILTER

AIM: To Examine the input and output waveforms of Full Wave Rectifier and also calculate its load regulation and ripple factor.

1. with Filter
2. without Filter

APPARATUS:

Digital multimeters	Multimeter	- 1No.
Transformer (6V-0-6V)		- 1No.
Diode, 1N4007		- 2No.
Capacitor 100 μ f/470 μ f		- 1No.
Decade Resistance Box		- 1No.
Breadboard		
CRO and CRO probes		
Connecting wires		

THEORY:

The circuit of a center-tapped full wave rectifier uses two diodes D1&D2. During positive half cycle of secondary voltage (input voltage), the diode D1 is forward biased and D2 is reverse biased. So the diode D1 conducts and current flows through load resistor R_L .

During negative half cycle, diode D2 becomes forward biased and D1 reverse biased. Now, D2 conducts and current flows through the load resistor R_L in the same direction. There is a continuous current flow through the load resistor R_L during both the half cycles and will get unidirectional current as shown in the model graph. The difference between full wave and half wave rectification is that a full wave rectifier allows unidirectional (one way) current to the load during the entire 360 degrees of the input signal and half-wave rectifier allows this only during one half cycle (180 degree).

THEORETICAL CALCULATIONS:

$$V_{rms} = V_m / \sqrt{2}$$

$$V_m = V_{rms} \sqrt{2}$$



$$V_{dc} = 2V_m / \pi$$


(i) Without filter:

$$\text{Ripple factor, } r = \sqrt{(V_{rms} / V_{dc})^2 - 1} = 0.812$$

(ii) With filter:

$$\text{Ripple factor, } r = 1 / (4\sqrt{3} f C R_L)$$

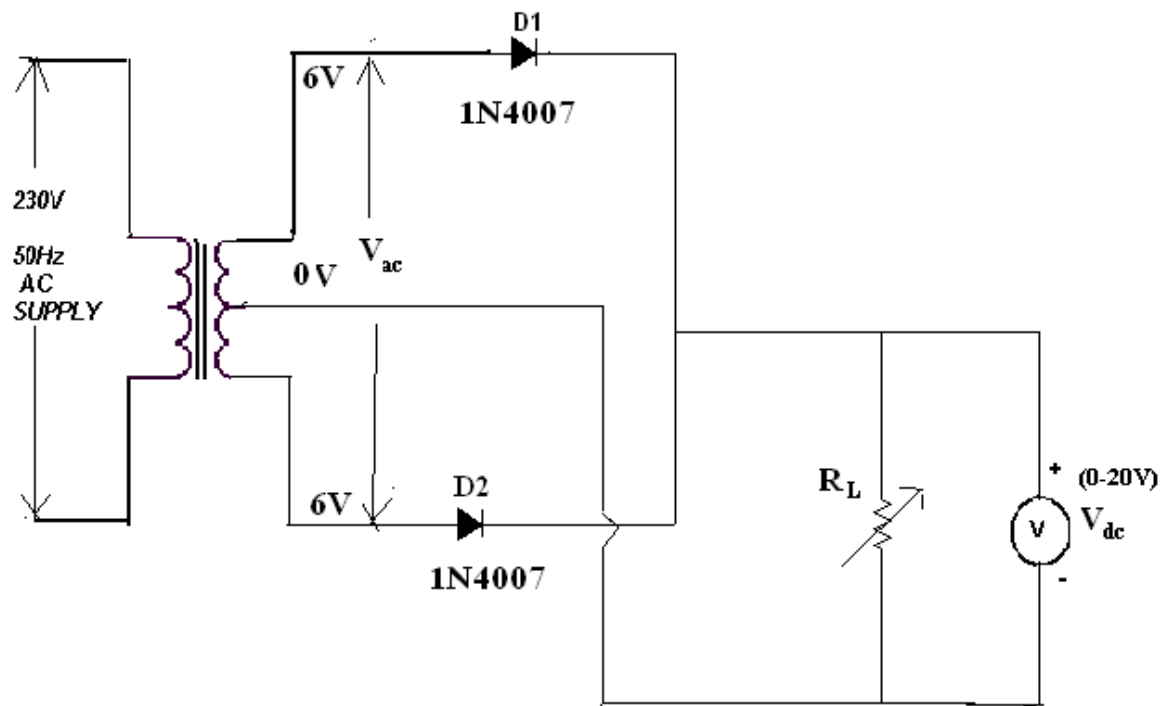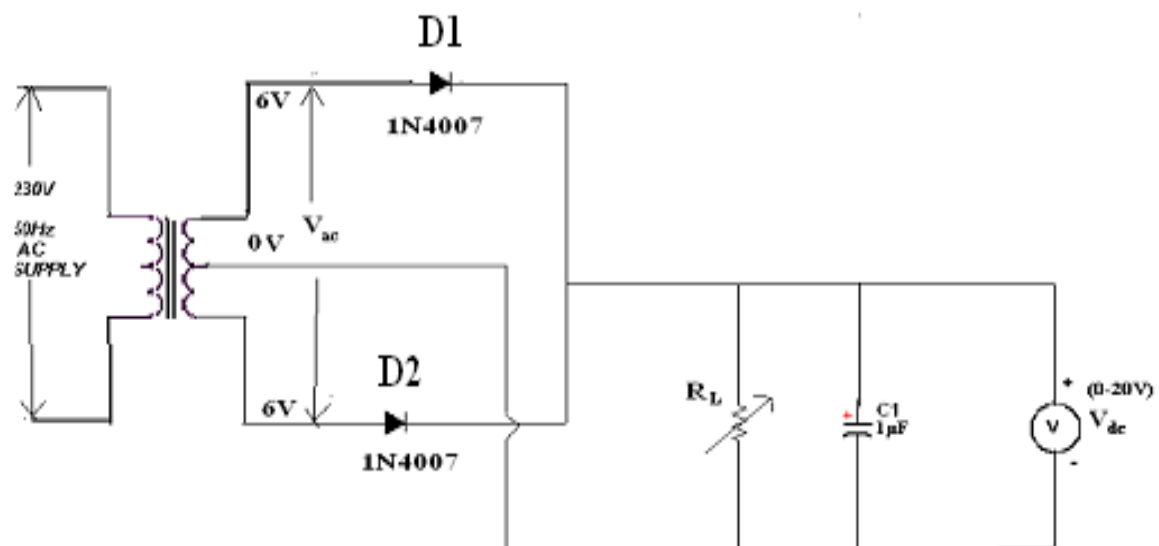CIRCUIT DIAGRAM:**A) FULL WAVE RECTIFIER WITHOUT FILTER:****B) FULL WAVE RECTIFIER WITH FILTER:**

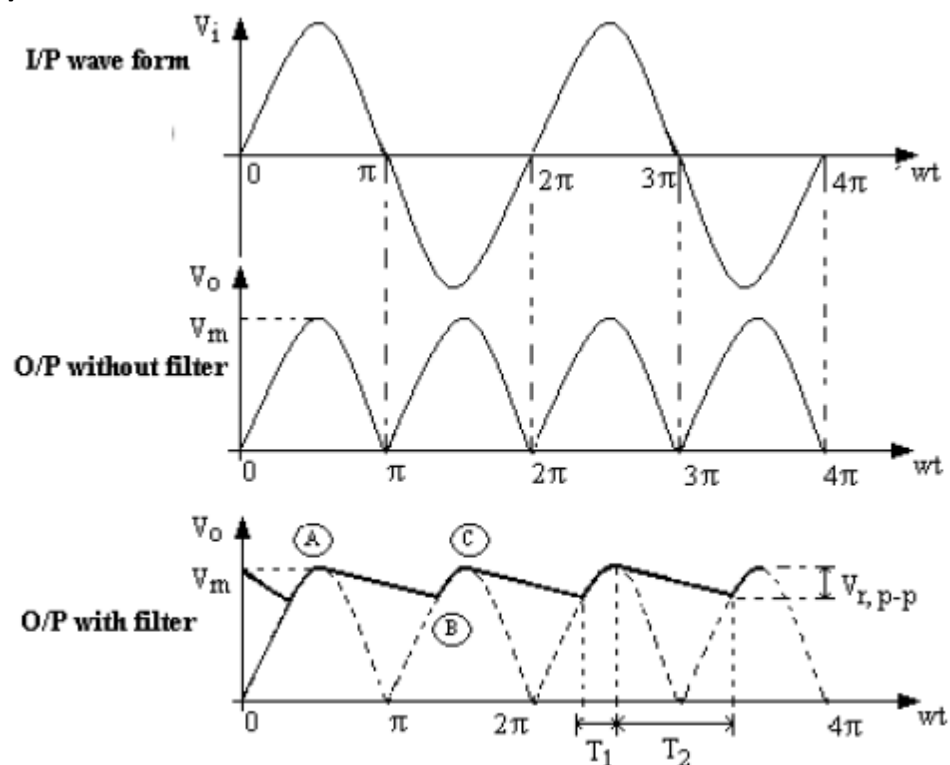MODEL WAVEFORMS:**A) WAVEFORMS:****Full-wave Rectifier with capacitor filter wave form****WITHOUT FILTER:**

S.No	Load Resistance R_L kilo-ohm	O/P Voltage (V_o)		Ripple factor $\left(\gamma = \frac{V_{ac}}{V_{dc}}\right)$	% of Regulation $\left(\frac{V_{NL} - V_{FL}}{V_{NL}} \times 100\%\right)$
		V_{ac} (V)	V_{dc} (V)		
1	1				
2	2				
3	3				
4	4				
5	5				
6	6				
7	7				
8	8				

WITH CAPACITOR FILTER:

$V_{\text{no load Voltage (Vdc)}} = V$

S.No	Load Resistance R_L kilo-ohm S	O/P Voltage (Vo)		Ripple factor $\left(\gamma = \frac{V_{ac}}{V_{dc}}\right)$	% of Regulation $\left(\frac{V_{NL} - V_{FL}}{V_{NL}} \times 100\%\right)$
		V_{ac} (V)	V_{dc} (V)		
1	1				
2	2				
3	3				
4	4				
5	5				
6	6				
7	7				
8	8				

PROCEDURE:

1. Connections are made as per the circuit diagram.
2. Connect the ac mains to the primary side of the transformer and the secondary side to the rectifier.
3. Measure the ac voltage at the input side of the rectifier.
4. Measure both ac and dc voltages at the output side the rectifier.
5. Find the theoretical value of the dc voltage by using the formula $V_{dc} = 2V_m/\pi$
6. Connect the filter capacitor across the load resistor and measure the values of V_{ac} and V_{dc} at the output.
7. The theoretical values of Ripple factors with and without capacitor are calculated.
8. From the values of V_{ac} and V_{dc} practical values of Ripple factors are calculated. The practical values are compared with theoretical values.

PRECAUTIONS:

1. The primary and secondary side of the transformer should be carefully identified.
2. The polarities of all the diodes should be carefully identified.

RESULT:

EXERCISE QUESTIONS:

1. A Full wave single phase rectifier makes use of 2 diodes, the internal forward resistance of each is considered to be constant and equal to 30Ω . The load resistance is $1K\Omega$. The transformer secondary voltage is 200-0-200V (rms). Calculate V_{DC} , I_{DC} , and Ripple factor efficiency.

VIVA QUESTIONS:

1. Define regulation of the full wave rectifier?
2. Define peak inverse voltage (PIV)? And write its value for Full-wave rectifier?
3. If one of the diode is changed in its polarities what wave form would you get?
4. Does the process of rectification alter the frequency of the waveform?
5. What is ripple factor of the Full-wave rectifier?
6. What is the necessity of the transformer in the rectifier circuit?
7. What are the applications of a rectifier?
8. What is meant by ripple and define Ripple factor?
9. Explain how capacitor helps to improve the ripple factor?
10. Can a rectifier made in INDIA ($V=230v$, $f=50Hz$) be used in USA ($V=110v$, $f=60Hz$)?

5. INPUT AND OUTPUT CHARACTERISTICS OF TRANSISTOR CB CONFIGURATION

- AIM:** 1.To observe and draw the input and output characteristics of a transistor connected in common base configuration.
2. To find α of the given transistor and also its input and output Resistances.

APPARATUS:

Transistor, BC107	-1No.
Regulated power supply (0-30V)	-1No.
Voltmeter (0-20V)	- 2No.
Ammeters (0-10mA)	-2No.
Resistor, 1K Ω	-2No
Bread board	
Connecting wires	

THEORY:

A transistor is a three terminal active device. The terminals are emitter, base, collector. In CB configuration, the base is common to both input (emitter) and output (collector). For normal operation, the E-B junction is forward biased and C-B junction is reverse biased. In CB configuration, I_E is +ve, I_C is -ve and I_B is -ve. So,

$$V_{EB} = F_1(V_{CB}, I_E) \text{ and}$$

$$I_C = F_2(V_{EB}, I_B)$$




With an increasing the reverse collector voltage, the space-charge width at the output junction increases and the effective base width 'W' decreases. This phenomenon is known as "Early effect". Then, there will be less chance for recombination within the base region. With increase of charge gradient with in the base region, the current of minority carriers injected across the emitter junction increases.

The current amplification factor of CB configuration is given by,

$$\alpha = \Delta I_C / \Delta I_E$$

$$\text{Input Resistance, } r_i = \Delta V_{BE} / \Delta I_E \quad \text{at Constant } V_{CB}$$

$$\text{Output Résistance, } r_o = \Delta V_{CB} / \Delta I_C \quad \text{at Constant } I_E$$

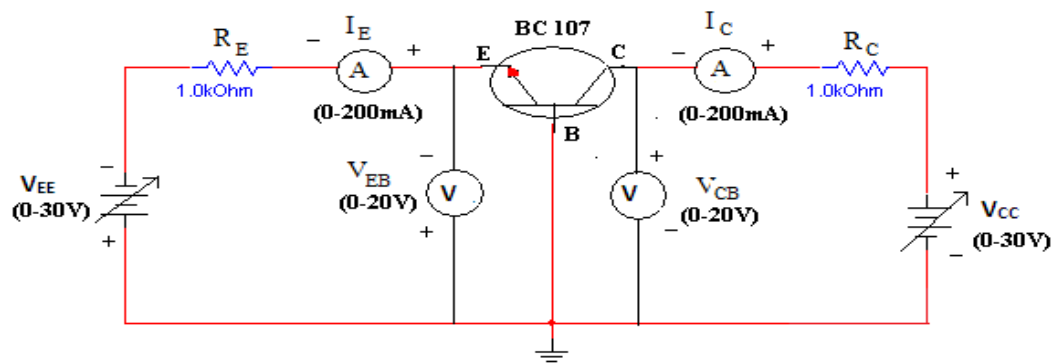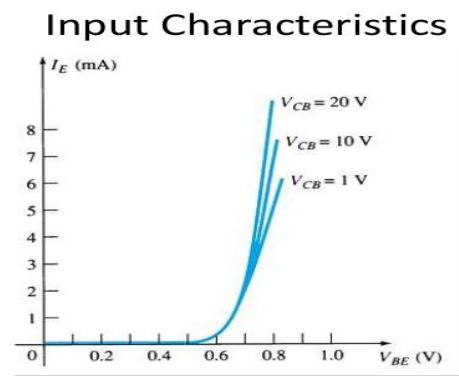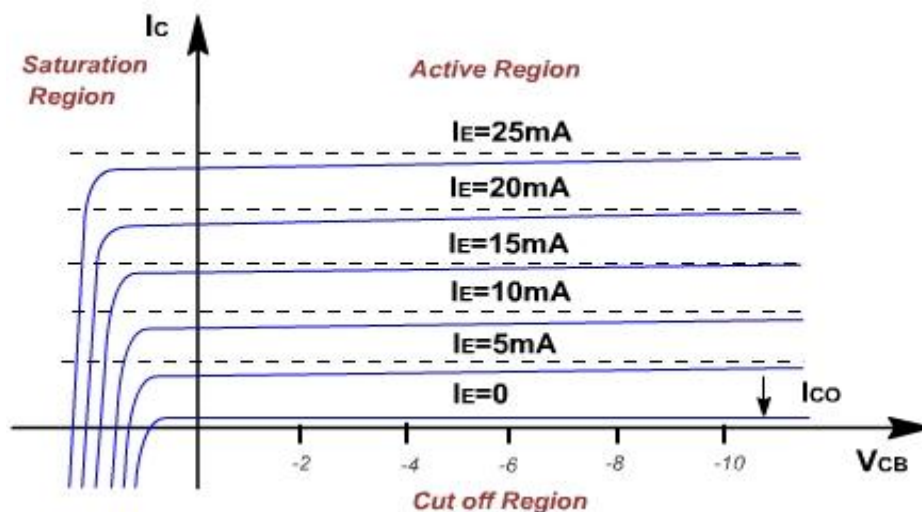CIRCUIT:**MODEL GRAPHS:****A) INPUT CHARACTERISTICS****B) OUTPUT CHARACTERISTICS**

OBSERVATIONS:**A) INPUT CHARACTERISTICS:**

$V_{EE}(V)$	$V_{CB}=1V$		$V_{CB}= 2V$		$V_{CB}= 4V$	
	$V_{EB}(V)$	$I_E(mA)$	$V_{EB}(V)$	$I_E(mA)$	$V_{EB}(V)$	$I_E(mA)$

B) OUTPUT CHARACTERISTICS:

$V_{CC}(V)$	$I_E=10mA$		$I_E=20mA$		$I_E=30mA$	
	$V_{CB}(V)$	$I_C(mA)$	$V_{CB}(V)$	$I_C(mA)$	$V_{CB}(V)$	$I_C(mA)$

PROCEDURE:**A) INPUT CHARACTERISTICS:**

1. Connections are made as per the circuit diagram.
2. For plotting the input characteristics, the output voltage V_{CE} is kept constant at 0V and for different values of V_{EE} , note down the values of I_E and V_{BE} .
3. Repeat the above step keeping V_{CB} at 2V, 4V, and 6V and all the readings are tabulated.
4. A graph is drawn between V_{EB} and I_E for constant V_{CB} .

B) OUTPUT CHARACTERISTICS:

1. Connections are made as per the circuit diagram.
2. For plotting the output characteristics, the input I_E is kept constant at 0.5mA and for different values of V_{CC} , note down the values of I_C and V_{CB} .
3. Repeat the above step for the values of I_E at 1mA, 5mA and all the readings are tabulated.
4. A graph is drawn between V_{CB} and I_C for constant I_E .

PRECAUTIONS:

1. The supply voltages should not exceed the rating of the transistor.
2. Meters should be connected properly according to their polarities.

RESULT:**EXERCISE QUESTIONS:**

1. Calculate the collector current and emitter current for a transistor with $\alpha_{D.C.} = 0.99$ and $I_{CBO} = 20 \mu A$ when the base current is $50 \mu A$.

VIVA QUESTIONS:

1. What is the range of α for the transistor?
2. Draw the input and output characteristics of the transistor in CB configuration?
3. Identify various regions in output characteristics?
4. What is the relation between α and β ?
5. What are the applications of CB configuration?
6. What are the input and output impedances of CB configuration?
7. Define α (alpha)?
8. What is early effect?
9. Draw Circuit diagram of CB configuration for PNP transistor?
10. What is the power gain of CB configuration?

6. INPUT AND OUTPUT CHARACTERISTICS OF TRANSISTOR CE CONFIGURATION

AIM:

1. To draw the input and output characteristics of transistor connected in CE configuration
2. To find β of the given transistor and also its input and output Resistances

APPARATUS:

Transistor, BC107	-1No.
Regulated power supply (0-30V)	-1No.
Voltmeter (0-20V)	-2No.
Ammeters (0-20mA)	-1No.
Ammeters (0-200 μ A)	-1No.
Resistor, 100 Ω	-1No.
Resistor, 1K Ω	-1No.
Bread board	
Connecting wires	

THEORY:




In common emitter configuration, input voltage is applied between base and emitter terminals and out put is taken across the collector and emitter terminals. Therefore the emitter terminal is common to both input and output.

The input characteristics resemble that of a forward biased diode curve. This is expected since the Base-Emitter junction of the transistor is forward biased. As compared to CB arrangement I_B increases less rapidly with V_{BE} . Therefore input resistance of CE circuit is higher than that of CB circuit.

The output characteristics are drawn between I_C and V_{CE} at constant I_B . the collector current varies with V_{CE} upto few volts only. After this the collector current becomes almost constant, and independent of V_{CE} . The value of V_{CE} up to which the collector current changes with V_{CE} is known as Knee voltage. The transistor always operated in the region above Knee voltage, I_C is always constant and is approximately equal to I_B . The current amplification factor of CE configuration is given by

$$\beta = \Delta I_C / \Delta I_B$$

$$\begin{aligned} \text{Input Resistance, } r_i &= \Delta V_{BE} / \Delta I_B (\mu A) \text{ at Constant } V_{CE} \\ \text{Output Resistance, } r_o &= \Delta V_{CE} / \Delta I_C \text{ at Constant } I_B (\mu A) \end{aligned}$$

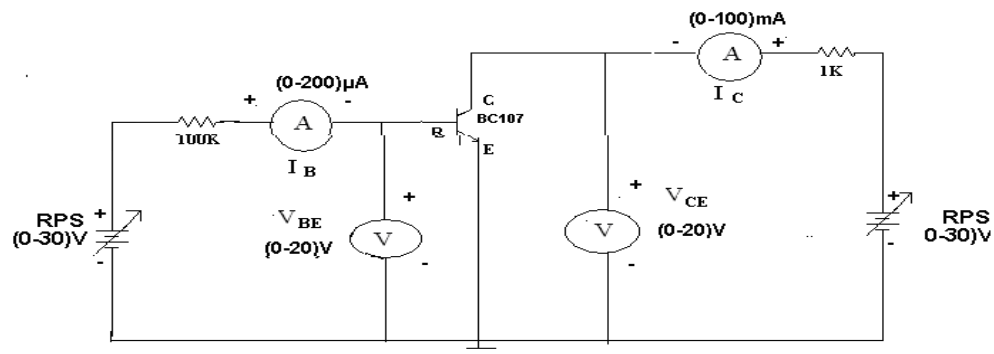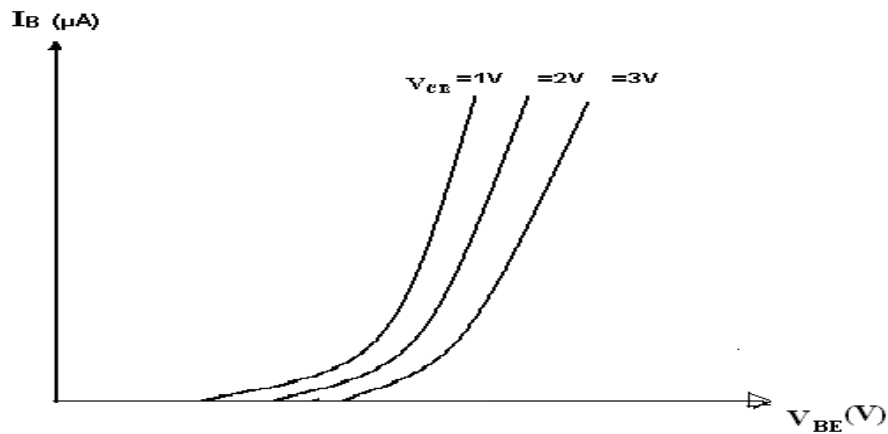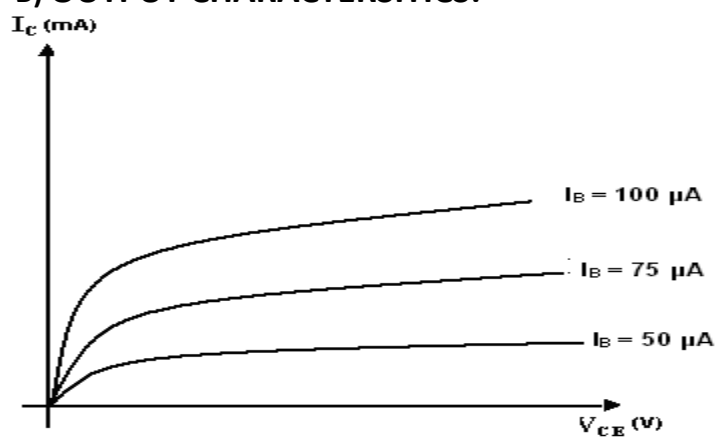CIRCUIT DIAGRAM:**MODEL GRAPHS:****A) INPUT CHARACTERISTICS:****B) OUTPUT CHARACTERISTICS:**

OBSERVATIONS:**A) INPUT CHARACTERISTICS:**

V_{BB}	$V_{CE} = 1V$		$V_{CE} = 2V$		$V_{CE} = 4V$	
	$V_{BE}(V)$	$I_B(\mu A)$	$V_{BE}(V)$	$I_B(\mu A)$	$V_{BE}(V)$	$I_B(\mu A)$

B) OUTPUT CHARACTERISTICS:

S.NO	$I_B = 50 \mu A$		$I_B = 75 \mu A$		$I_B = 100 \mu A$	
	$V_{CE}(V)$	$I_C(mA)$	$V_{CE}(V)$	$I_C(mA)$	$V_{CE}(V)$	$I_C(mA)$

PROCEDURE:**INPUT CHARACTERISTICS:**

1. Connect the circuit as per the circuit diagram.
2. For plotting the input characteristics the output voltage V_{CE} is kept constant at 1V and for different values of V_{BB} , note down the values of I_B and V_{BE}
3. Repeat the above step by keeping V_{CE} at 2V and 4V and tabulate all the readings.
4. plot the graph between V_{BE} and I_B for constant V_{CE}

OUTPUT CHARACTERISTICS:

1. Connect the circuit as per the circuit diagram
2. For plotting the output characteristics the input current I_B is kept constant at 50 μA and for different values of V_{CC} note down the values of I_C and V_{CE}

3. Repeat the above step by keeping I_B at 75 μA and 100 μA and tabulate the all the readings
4. Plot the graph between V_{CE} and I_C for constant I_B

PRECAUTIONS:

1. The supply voltage should not exceed the rating of the transistor
2. Meters should be connected properly according to their polarities

RESULT:**EXERCISE QUESTIONS:**

1. For an NPN transistor with $\alpha_N = 0.98$, $I_{CO} = 2\mu\text{A}$ and $I_{EO} = 1.6\mu\text{A}$ connected in Common Emitter Configuration, calculate the minimum base current for which the transistor enters into saturation region. V_{CC} and load resistance are given as 12 V and 4.0 K Ω respectively.
2. Calculate the values of I_E , α_{dc} and β_{dc} for a transistor with $I_B = 13\mu\text{A}$, $I_C = 200\text{mA}$, $I_{CBO} = 6\mu\text{A}$. Also determine the new level of I_C which will result from reducing I_B to 100 mA.

VIVA QUESTIONS:

1. What is the range of β for the transistor?
2. What are the input and output impedances of CE configuration?
3. Identify various regions in the output characteristics?
4. What is the relation between α and β ?
5. Define current gain in CE configuration?
6. Why CE configuration is preferred for amplification?
7. What is the phase relation between input and output?
8. Draw diagram of CE configuration for PNP transistor?
9. What is the power gain of CE configuration?
10. What are the applications of CE configuration?